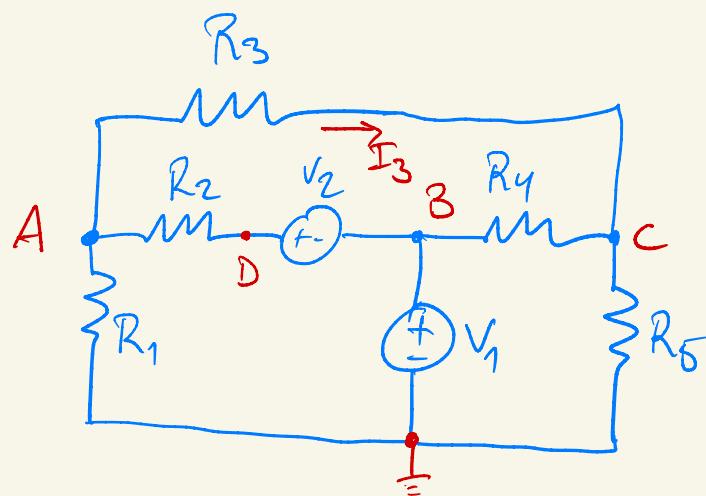


A1


 Q: Find  $I_3$ .

Using the node voltage method:

$$V_B = V_1 = 6V ; V_D = V_2 + V_1 = 9V$$

$V_A = ?$  ;  $V_C = ?$  (2 equations)

KCL at A:  $\frac{V_A}{R_1} + \frac{V_A - V_D}{R_2} + \frac{V_A - V_C}{R_3} = 0$

KCL at C:  $\frac{V_C}{R_5} + \frac{V_C - V_B}{R_4} + \frac{V_C - V_A}{R_3} = 0$


$$(1) \begin{cases} \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) V_A - \frac{1}{R_3} V_C = \frac{9}{R_2} \\ -\frac{1}{R_3} V_A + \left( \frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5} \right) V_C = \frac{6}{R_4} \end{cases}$$

(Solve (1) for  $V_A$  &  $V_C$ )

$$I_3 = \frac{V_A - V_C}{R_3}$$

(with the direction depicted  
in the figure)

A2

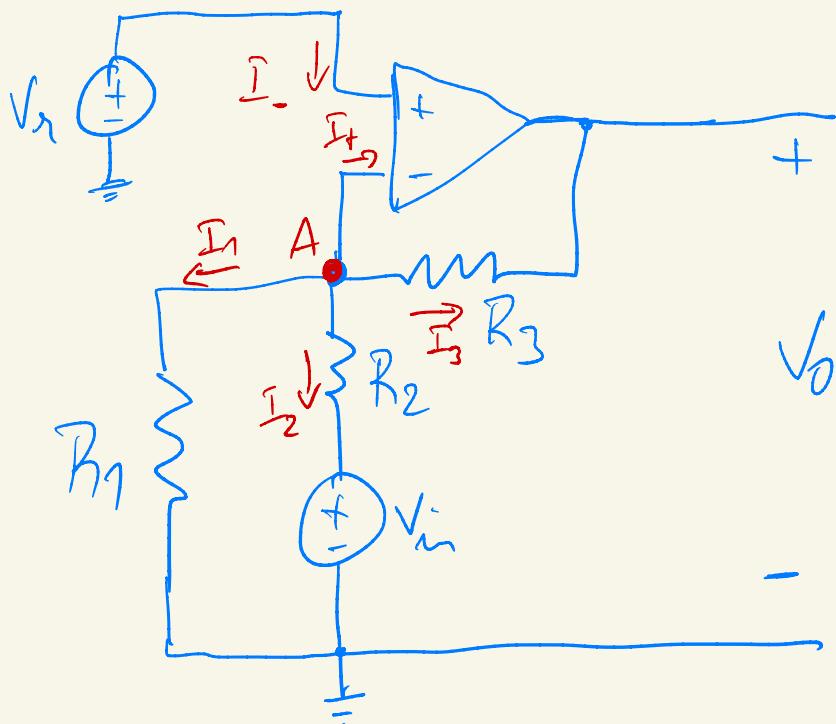

- Find  $V_o$  as a function of  $V_{in}$ ,  $V_2$
- Find  $I_3$ .

$\Rightarrow$  (ideal OpAmp)

$$\text{KCL at } A: \frac{V_A}{R_1} + \frac{V_A - V_{in}}{R_2} + \frac{V_A - V_o}{R_3} + \cancel{I_+} = 0$$

$$V_A = V_- = V_+ = V_2 \quad (\text{ideal OpAmp in negative feedback}) \Rightarrow \frac{V_o}{R_3} = -\frac{V_{in}}{R_2} + \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) V_2$$


$$V_o = -\frac{R_3}{R_2} V_{in} + \left( 1 + \frac{R_3(R_1+R_2)}{R_1 R_2} \right) V_2$$

$$\therefore V_o = -0.25 V_{in} + 1.75 V_2$$

$$I_3 = \frac{V_A - V_o}{R_3} = \frac{V_2 - V_o}{R_3} = \frac{1 - (-1.25 + 1.75)}{100} = \frac{0.5}{100} = 5 \text{ mA}$$

A<sub>3</sub>

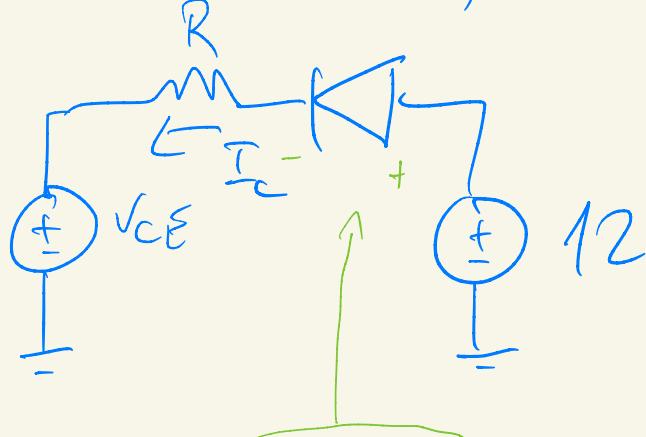Switch :  $V_{CE} = V_{CE, SAT} = 0.2 \checkmark$



$$V_D = 1.5V$$

KVL:  $12 - V_D - R_b I_c - R I_c = V_{CE} = 0 \text{ V} (=)$


$$12 - 1.5 - 0.2 = (R + R_b) I_c (=)$$

$$I_c = \frac{10.3}{R + R_b}; \quad I_c \leq 20 \text{ mA} (=)$$

$$\frac{10.3}{R + 20} \leq 20 \cdot 10^{-3} (=)$$

$$R + 20 \geq \frac{10.3}{20 \cdot 10^{-3}} = 515 \Omega$$

$$R \geq 495 \Omega$$

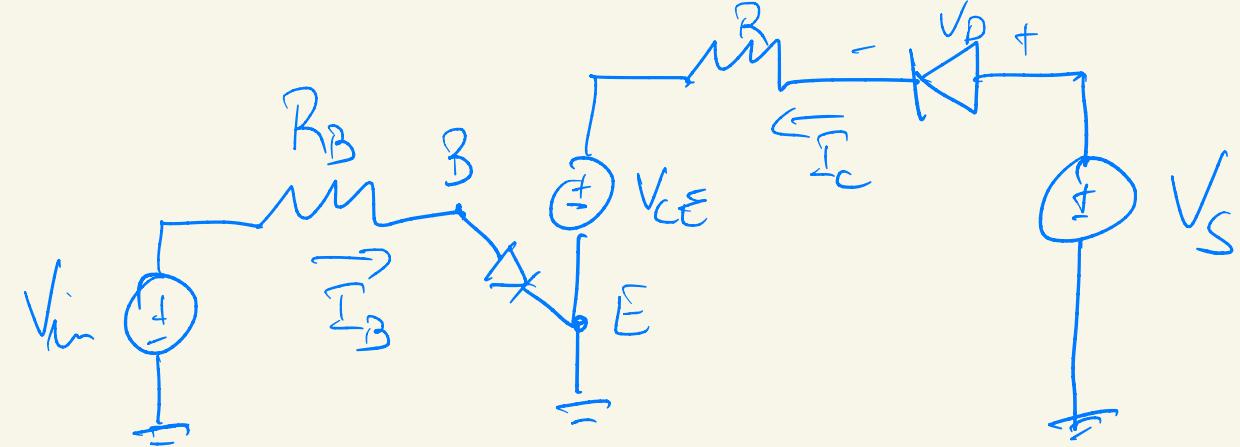

choose  $R_B$  so that  $I_B \in \left[ \frac{I_c}{\beta}, 1 \text{mA} \right]$

$$I_B = \frac{V_{in} - V_B}{R_B} = \frac{5 - 0.6}{R_B} = \frac{4.4}{R_B}$$

$$I_B \leq 1 \text{mA} \Rightarrow \frac{4.4}{R_B} \leq 10^{-3} \Rightarrow R_B \geq 4.4 \text{k}\Omega$$

$$I_B \geq \frac{I_c}{\beta} \Rightarrow \beta I_B \geq \frac{10.3}{R + R_D} \quad (I_c \text{ when } V_{CE} = V_{CE,SAT})$$


$$\Rightarrow \frac{\beta \cdot 4.4}{R_B} \geq \frac{10.3}{R + R_D} \Rightarrow R_B \leq \frac{\beta \cdot 4.4 (R + R_D)}{10.3}$$

$$\text{Supposing } R \approx 500 \Omega ; R_B \leq \frac{300 \times 4.4 \times 520}{10.3} \approx$$

$$R_B \leq \frac{6.6 \times 10^5}{10.3} \approx 64 \text{ k}\Omega$$

$\therefore R_B = 5 \text{ k}\Omega$  would do.

A4. a)

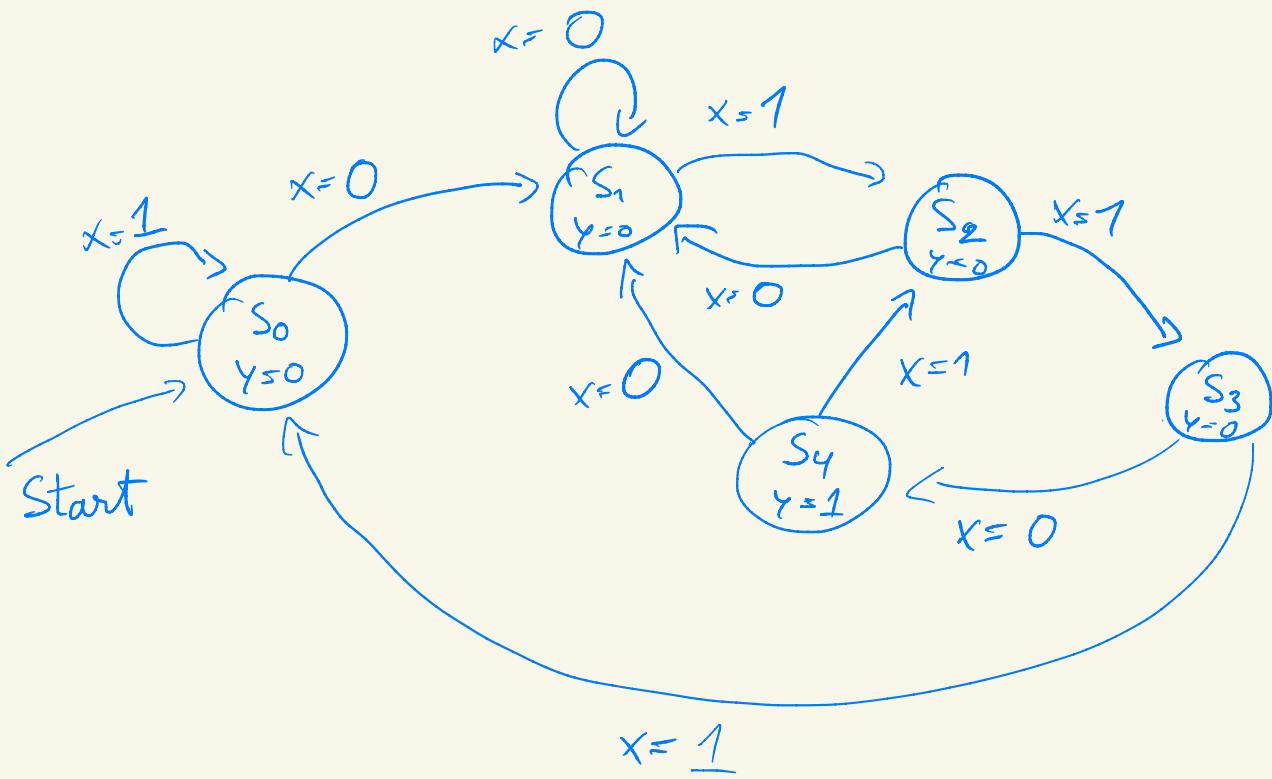

State Coding			Output (for Moore circuit)	
	$q_2$	$q_1$	$q_0$	$Y$
$S_0$	0	0	0	0
$S_1$	0	0	1	0
$S_2$	0	1	0	0
$S_3$	0	1	1	0
$S_4$	1	0	0	1

# Transition Truth Table



$q_2$	$q_1$	$q_0$	$x_i$		$q_2^+$	$q_1^+$	$q_0^+$
0	0	0	0		0	0	1
0	0	0	1		0	0	0
0	0	1	0		0	0	1
0	0	1	1		0	1	0
0	1	0	0		0	0	1
0	1	0	1		0	1	1
0	1	1	0		1	0	0
0	1	1	1		0	0	0
1	0	0	0		0	0	1
1	0	0	1		0	1	0
-	-	-	-				

3 flip-flops are needed


A 4 b)

		q <sub>0</sub> ×			
		00	01	11	10
q <sub>2</sub> q <sub>1</sub>	00	-		1	1
	01	1			-
	11	1			
	10		-	1	
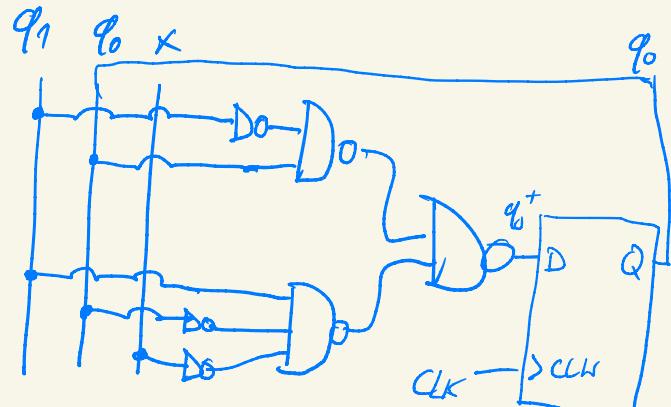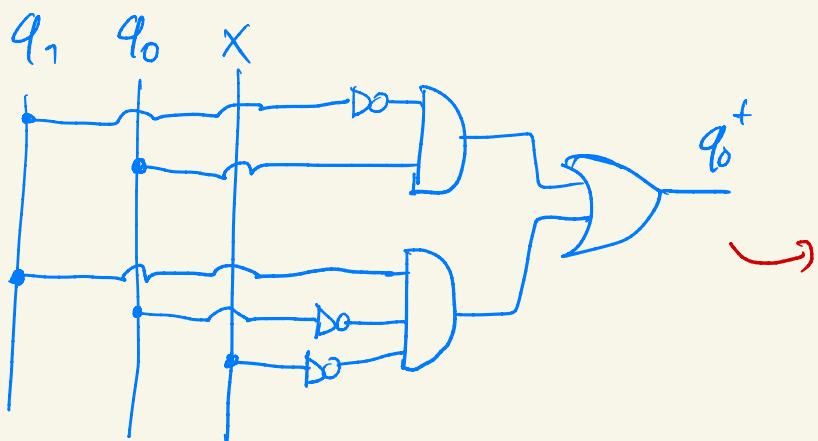
$$q_0^+ = \bar{q}_1 \cdot q_0 + q_1 \cdot \bar{q}_0 \cdot x$$



A5

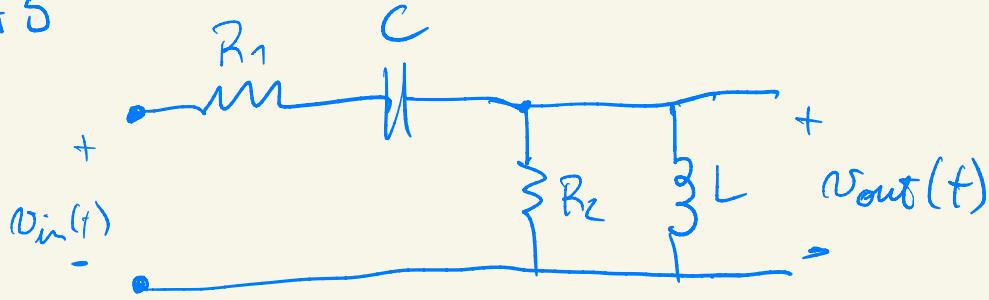

$$V_{in}(t) = 2 \sin(10^5 t - \frac{\pi}{3})$$


- Find  $V_{out}(t)$
- classify the type of filter

① Convert all voltages to phasors.

$$V_{in}(t) = I_m (\sqrt{c_{in}}(t)) ; \sqrt{c_{in}}(t) = 2 e^{j\omega t} e^{j(-\frac{\pi}{3})}$$

Phasor:  $\bar{V}_{in} = 2 e^{-j\frac{\pi}{3}}$  (so  $\sqrt{c_{in}}(t) = \bar{V}_{in} e^{j\omega t}$ )  
 $\omega = 10^5 \pi \text{ rad/s.}$

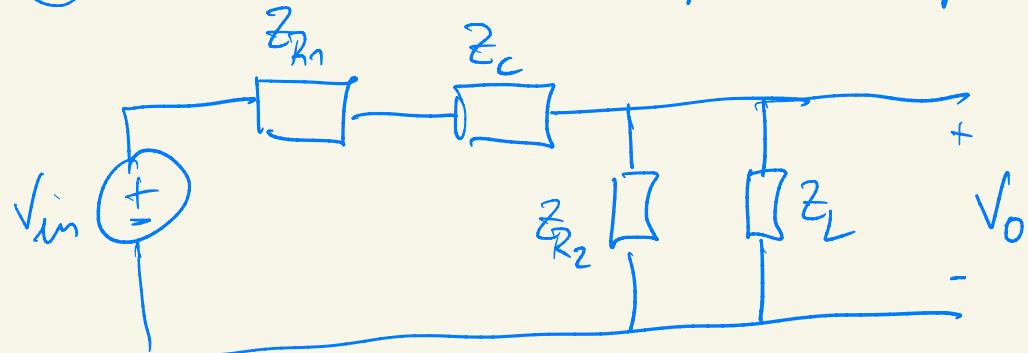② Convert to complex impedances and phasors




$$Z_{R1} = R_1, Z_{R2} = R_2$$

$$Z_C = \frac{1}{j\omega c}$$

$$Z_L = j\omega L$$

③ (Simplify and) Analyze the circuit

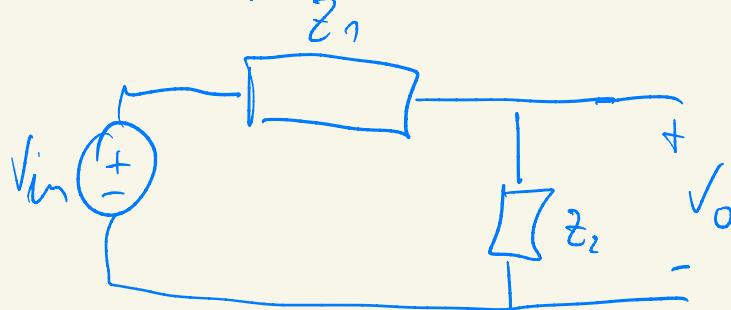

$$Z_1 = Z_{R_1} + Z_C = R + \frac{1}{j\omega C}$$

$$Z_2 = Z_{R_2} // Z_L = \frac{Z_{R_2} Z_L}{Z_{R_2} + Z_L}$$

$$V_o = \frac{Z_2}{Z_1 + Z_2} V_{in} \quad (\text{It is a voltage divider})$$

Or to stop ③ here & go to ④

$$H(j\omega) = \frac{V_o}{V_{in}} = \frac{Z_2}{Z_1 + Z_2} = \frac{1}{\frac{Z_1}{Z_2} + 1} = \frac{1}{\frac{(Z_{R_2} + Z_L)(Z_{R_1} + Z_C)}{Z_{R_2} Z_L} + 1}$$

$$= \frac{Z_{R_2} Z_L}{(Z_{R_1} + Z_C)(Z_{R_2} + Z_L) + Z_{R_2} Z_L} = \frac{j\omega R_2 L}{Z_{R_1} Z_{R_2} + Z_{R_1} Z_L + Z_C Z_{R_2} + Z_C Z_L + Z_{R_2} Z_L} =$$

$$= \frac{j\omega R_2 L}{R_1 R_2 + j\omega R_1 L + \frac{R_2}{j\omega C} + \frac{L}{C} + j\omega R_2 L} = \quad (R_1 = R_2 = R)$$

$$= \frac{-\omega^2 R L C}{j\omega C R^2 - \omega^2 R L C + R + j\omega L - \omega^2 R L C} =$$

$$= \frac{-\omega^2 R L C}{R - 2\omega^2 R L C + j\omega(R^2 C + L)} = \frac{-10^{10} \pi^2 \cdot 50 \cdot 10^{-10}}{50 - 2 \cdot 10^{10} \cdot \pi^2 \cdot 50 \cdot 10^{-10} + j \cdot 10^5 \left( 50 \cdot 10^{-7} + \frac{1}{10} \right)}$$

$$= \frac{-\pi^2 \cdot 50}{(1 - 2\pi^2) \cdot 50 + j\pi \cdot 10^5 (1.25 \times 10^{-3})} = \frac{-50\pi^2}{(1 - 2\pi^2) \cdot 50 + j\pi \cdot 125}$$

$$H(j10^5\pi) = \frac{-2\pi^2}{(1-2\pi^2).2 + j5\pi} = |H(j10^5\pi)| \cdot e^{j\angle H(j10^5\pi)}$$

④ Compute the phasor  $V_0$

$$V_0 = H(j10^5\pi) \cdot V_{in} = |H(j10^5\pi)| \cdot |V_{in}| \cdot e^{j(\angle V_{in} + \angle H(j10^5\pi))}$$

⑤ Convert back from phasor to sinusoidal voltages


$$\Rightarrow v_{out}(t) = I_m(V_0 e^{j\omega t}) = 2 \cdot |H(j10^5\pi)| \cdot \sin(10^5\pi t - \frac{\pi}{3} + \angle H(j10^5\pi))$$

- Filter type:


$$|H(j0)| = \lim_{w \rightarrow 0} |H(jw)| = \frac{0}{R} = 0$$

$$|H(j\infty)| = \lim_{w \rightarrow \infty} |H(jw)| = \lim_{w \rightarrow \infty} \left| \frac{-w^2 RLC}{R - 2w^2 RLC + jw(R^2 C + L)} \right| =$$

$$= \lim_{w \rightarrow \infty} \left| \frac{-RLC}{\frac{R}{w^2} - 2RLC + j\frac{1}{w}(R^2 C + L)} \right| = \frac{1}{2}$$

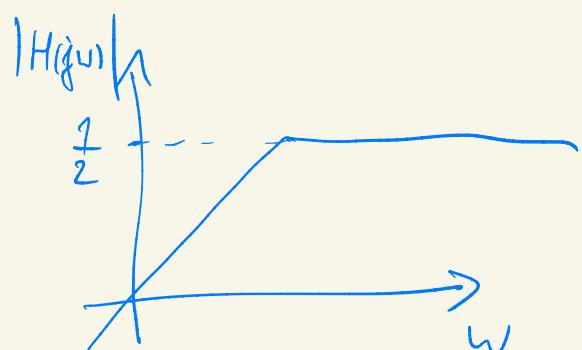

It is a high-pass filter

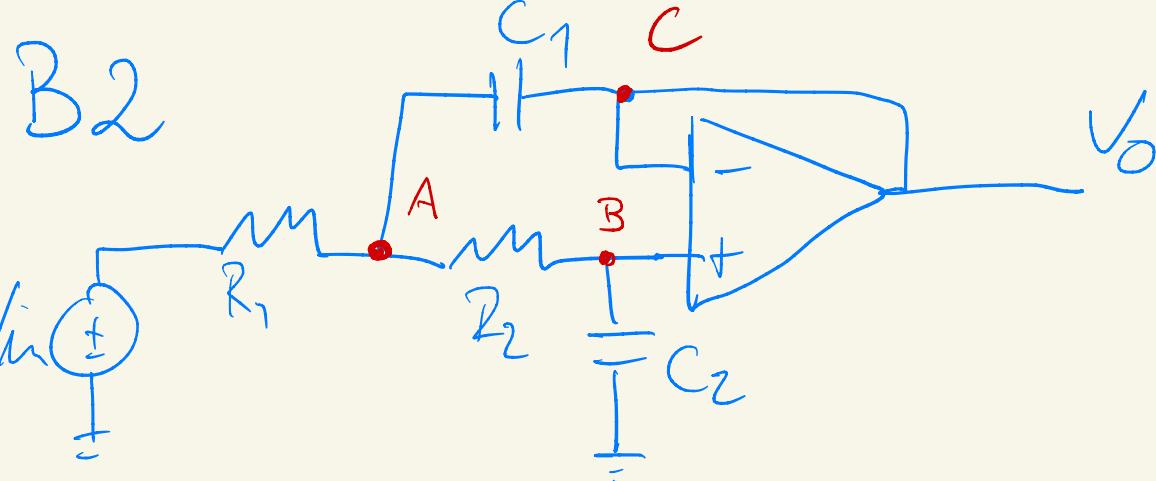

$$V_A = ? \quad V_B = V_C = V_o$$

↳ OPAmpl in neg. feedback

KCL:

$$\left\{ \frac{V_{in} - V_A}{Z_{R_1}} + \frac{V_B - V_A}{Z_{R_2}} + \frac{V_o - V_A}{Z_{C_1}} = 0 \quad (i) \right.$$

$$\frac{V_A - V_B}{Z_{R_2}} + \frac{0 - V_B}{Z_{C_2}} = 0$$

$$V_o = V_B$$

$$\left\{ \begin{aligned} & \left( \frac{V_{in}}{Z_{R_1}} + \left( \frac{1}{Z_{R_2}} + \frac{1}{Z_{C_1}} \right) V_o - \left( \frac{1}{Z_{R_1}} + \frac{1}{Z_{R_2}} + \frac{1}{Z_{C_1}} \right) V_A \right) = 0 \\ & \frac{1}{Z_{R_2}} V_A = \left( \frac{1}{Z_{R_2}} + \frac{1}{Z_{C_2}} \right) V_o \Leftrightarrow V_A = \left( 1 + \frac{Z_{R_2}}{Z_{C_2}} \right) V_o \end{aligned} \right. \quad (=)$$

$$\frac{V_{in}}{Z_{R_1}} = - \frac{Z_{R_2} + Z_{C_1}}{Z_{R_2} Z_{C_1}} V_o + \left( \frac{1}{Z_{R_1}} + \frac{1}{Z_{R_2}} + \frac{1}{Z_{C_1}} \right) \left( 1 + \frac{Z_{R_2}}{Z_{C_2}} \right) V_o$$

$$R_1 = R_2 = Z_{R_1} = Z_{R_2} = Z_R$$

$$Z_{C_1} = \frac{1}{j\omega C_1} = \frac{1}{2j\omega C_2} = \frac{1}{2} Z_{C_2}$$

$$Z_{C_1} = Z_C, Z_{C_2} = 2 Z_C$$

$$\frac{V_{in}}{Z_R} = - \frac{Z_R + Z_C}{Z_R \cdot Z_C} V_o + \left( \frac{2}{Z_R} + \frac{1}{Z_C} \right) \left( 1 + \frac{Z_R}{2Z_C} \right) V_o$$

$$V_{in} = - \frac{Z_R + Z_C}{Z_C} V_o + \left( 2 + \frac{Z_R}{Z_C} \right) \left( 1 + \frac{Z_R}{2Z_C} \right) V_o$$

$$V_{in} = \left( - \frac{Z_R + Z_C}{Z_C} + \left( 2 + \frac{Z_R}{Z_C} + \frac{Z_R^2}{2Z_C^2} + \frac{Z_R^2}{2Z_C^2} \right) \right) V_o$$

$$= \left( 1 + \frac{Z_R}{Z_C} + \frac{Z_R^2}{2Z_C^2} \right) V_o$$

$$= \left( \frac{2Z_C^2 + 2Z_R Z_C + Z_R^2}{2Z_C^2} \right) V_o$$

$$\Rightarrow V_o = \frac{2Z_C^2}{2Z_C^2 + 2Z_R Z_C + Z_R^2} V_{in}$$

$$H(j\omega) = \frac{V_o}{V_{in}} = \frac{2 \left( \frac{1}{j\omega C} \right)^2}{2 \left( \frac{1}{j\omega C} \right)^2 + \frac{2R}{j\omega C} + R^2} = \frac{1}{1 + j\omega RC + \frac{1}{2} (j\omega RC)^2} =$$

$$= \frac{1}{1 - \frac{1}{2} \omega^2 R^2 C^2 + j\omega RC}$$

$$; |H(j\omega)| = \frac{1}{\sqrt{\left(1 - \frac{1}{2} \omega^2 R^2 C^2\right)^2 + \omega^2 R^2 C^2}} =$$

$$= \frac{1}{\sqrt{1^2 - \omega^2 R^2 C^2 + \frac{1}{4} \omega^4 R^4 C^4 + \omega^2 R^2 C^2}} \\ = \frac{1}{\sqrt{1^2 + \frac{1}{4} \omega^4 R^4 C^4}}$$

$$\lim_{\omega \rightarrow 0} |H(j\omega)| = 1$$

$$\lim_{\omega \rightarrow \infty} |H(j\omega)| = 0$$

$$RC = 10^4 \times 20 \times 10^{-9} = 2 \times 10^{-4}$$
$$H(j1.4 \times 10^4) = \frac{1}{\sqrt{1^2 - \frac{1}{4} \cdot 1.4^4 \times 10^{16} \times (R \cdot C)^4}} =$$

$$= \frac{1}{\sqrt{1^2 + \frac{1.4^4}{4} \times 10^{16} \times 16 \times 10^{-16}}} = \frac{1}{\sqrt{1^2 + 4 \times 1.4^4}} \approx \frac{1}{\sqrt{1^2 + 15.4}} =$$

$$= \frac{1}{\sqrt{16.4}} \approx \frac{1}{4.05} \approx 0.247.$$