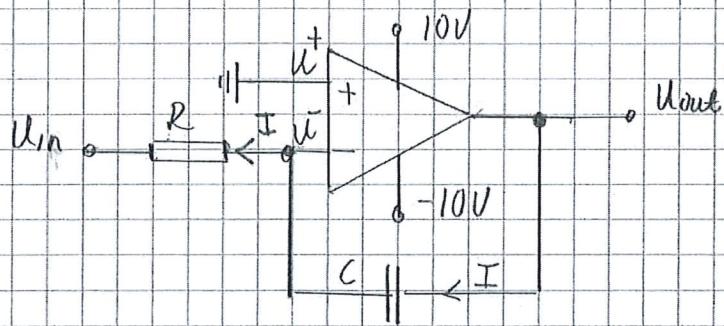


1



• Ideal OpAmp + Negative feedback  $\rightarrow u^+ \approx u^-$

1(a) Answer:  $|u_{out}| < 10 [V]$

1(b)

$$u_{in} + RI = 0$$

$$u_{out} - \frac{1}{C} \int_{s=0}^t I(s) ds$$

$$u_{out} = -\frac{1}{RC} \int_{s=0}^t u_{in}(s) ds = |u_{in}(s) = \alpha, s > 0| =$$

$$= -\frac{\alpha t}{RC} [V], \quad t \geq 0$$

1(c) Answer: Integration


1(d)

$$\alpha = -t \implies u_{out}(t) = -\frac{1}{RC} \int_{s=0}^t -s ds = \frac{t^2}{2RC}$$

$$u_{out}(2) = \frac{4}{2RC} = 4 \implies RC = \frac{1}{2} \rightarrow C = \frac{1}{2} \mu F.$$

Answer:  $C = \frac{1}{2} \mu F$

2a

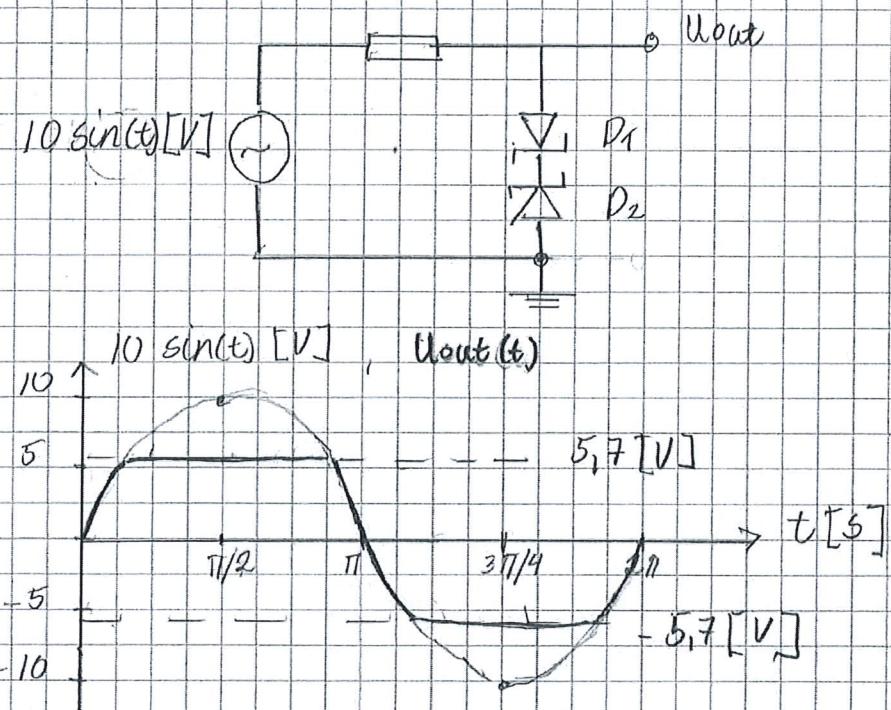


Negative part of cycle: D<sub>2</sub> - forward biased  
D<sub>1</sub> - backward biased

2b

NOR-gate

| A | B | Y |
|---|---|---|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 0 |

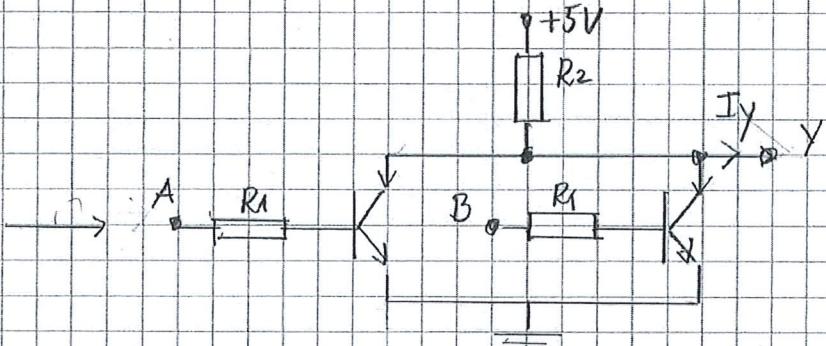

$$h_{FE} = 100$$

$$V_{BEK} = 0.7 [V]$$

$$V_{CEsat} = 0.1 [V]$$

$$I_{max} = 10 [mA]$$

$$\text{Logical 1} \Rightarrow \geq 4 [V]$$

$$\text{Logical 0} \Rightarrow \leq 1 [V]$$

Max input & output current of gate: 1 [mA]

### Selection of $R_2$ .

$$Y = 1 \rightarrow U_Y = 5 - I_Y \cdot R_2 > 4 \xrightarrow{\text{max}} R_2 < \frac{5-4}{1 \cdot 10^{-3}} = 1 [k\Omega]$$

$$Y = 0 \rightarrow U_Y = 5 - (I_C + I_Y) R_2 < 1 \xrightarrow{\substack{\text{min} \\ I_Y=0}} R_2 = \frac{4}{10^{-2}} > 400 [\Omega]$$

$\Rightarrow$  Select:  $R_2 = 820 [\Omega]$

### Selection of $R_1$

$$R_2 = 820 [\Omega] \rightarrow I_C < \frac{5 - V_{CE(\text{sat})}}{R_2} = 6 [\text{mA}]$$

$$\rightarrow I_B > I_C / h_{FE} = 6 \cdot 10^{-3} / 10^2 = 60 [\mu\text{A}]$$

$$\rightarrow R_1 < \frac{U_A - V_{BE}}{I_B} \xleftarrow{4V} \frac{4 - 0.7}{60 \cdot 10^{-6}} = 55 [\text{k}\Omega]$$

$$I_B = \frac{U_A - V_{BE}}{R_1} < 1 [\text{mA}] \rightarrow R_1 > 4,3 [\text{k}\Omega]$$

$\Rightarrow$  Select:  $R_1 = 4,7 [\text{k}\Omega]$


3

a) Answer: Mealy machine. The output depends both on the state & current input.

b) Answer: 4 states, Nr. of. states  $\leq 2^n$ , where n is the number of bits in the memory.


c)

| S | State |                |                |                             |                             |                | Y |
|---|-------|----------------|----------------|-----------------------------|-----------------------------|----------------|---|
|   | X     | Q <sub>1</sub> | Q <sub>2</sub> | Q <sub>1</sub> <sup>+</sup> | Q <sub>2</sub> <sup>+</sup> | S <sup>+</sup> |   |
| 0 | 0     | 0              | 0              | 0                           | 0                           | 0              | 0 |
| 1 | 0     | 0              | 1              | 0                           | 0                           | 0              | 0 |
| 2 | 0     | 1              | 0              | 0                           | 1                           | 1              | 0 |
| 3 | 1     | 1              | 1              | 0                           | 1                           | 1              | 0 |
| 0 | 1     | 0              | 0              | 1                           | 0                           | 2              | 0 |
| 1 | 1     | 0              | 1              | 0                           | 0                           | 0              | 1 |
| 2 | 1     | 1              | 0              | 1                           | 0                           | 2              | 0 |
| 3 | 1     | 1              | 1              | 0                           | 0                           | 0              | 1 |

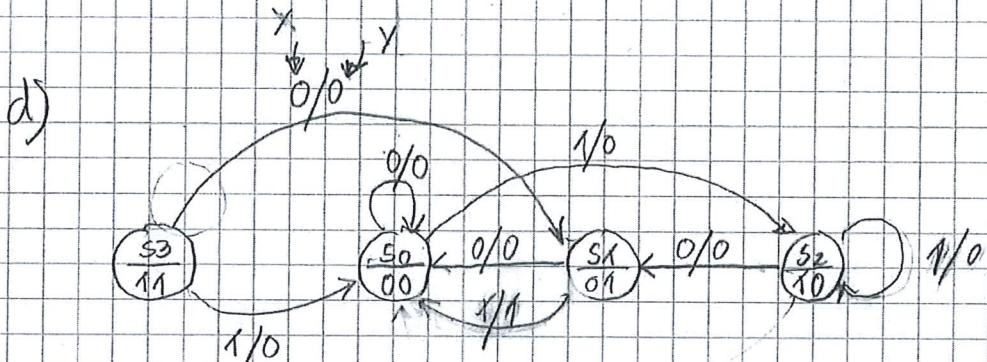

e) Answer: 101.

4 a)

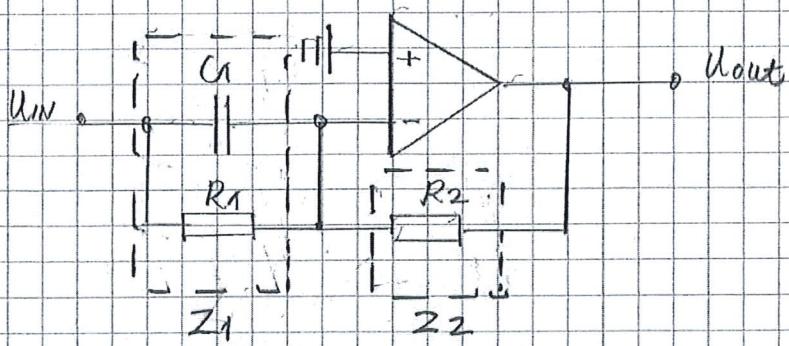

$$H(j\omega) = -z_2/z_1 \quad , \quad z_i - \text{complex impedance}$$

$$z_2 = R_2$$

$$z_1 = \frac{(1/j\omega C_1) \cdot R_1}{1/j\omega C_1 + R_1} = \frac{R_1}{1 + j\omega R_1 C_1}$$

$$\rightarrow H(j\omega) = -\frac{R_2}{R_1} \cdot \frac{1 + j\omega R_1 C_1}{1 + j\omega R_1 C_1}$$

b)  $R_1 = 10 \text{ [k}\Omega\text{]}, \quad R_2 = 1 \text{ [k}\Omega\text{]}, \quad C_1 = 1 \text{ [\mu F]}$

$$\rightarrow H(j\omega) = -0.1 (1 + 0.1j\omega)$$


$$|H(0)| = 0.1$$

$$\lim_{\omega \rightarrow \infty} |H(j\omega)| = \infty$$


Answer: HP-filter

c) Answer: Cut-off freq:  $1/R_1 C_1 - \cancel{100} \text{ [rad/s]}$

d)  $\uparrow 20 \log_{10} |H(j\omega)|$

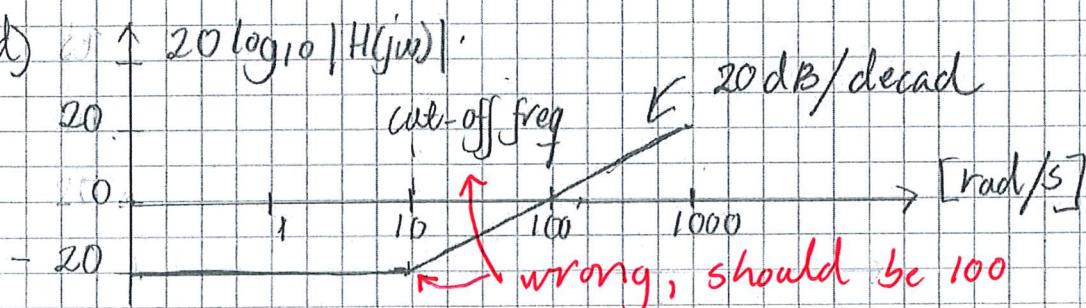

5a)

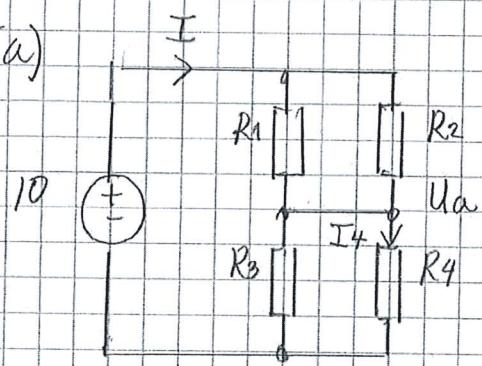

$$I_4 = U_a / R_4$$

$$U_a = R_3 // R_4 \cdot 10$$


$$R_1 // R_2 + R_3 // R_4$$

$$\Rightarrow I_4 = \frac{10}{R_4} \cdot \frac{R_3 \cdot R_4}{R_3 + R_4} = \frac{\frac{R_3 \cdot R_4}{R_1 \cdot R_2}}{R_1 + R_2} + \frac{R_3 \cdot R_4}{R_3 + R_4}$$

$$= \frac{10}{4 \cdot 10^3} \cdot \frac{4/3 \cdot 10^3}{2/3 \cdot 10^3 + 4/3 \cdot 10^3} = \frac{10}{4 \cdot 10^3} \cdot \frac{2}{3} = \frac{5}{3} \cdot 10^{-3} \text{ [A]}$$


Answer:  $5/3$  [mA]

5b)

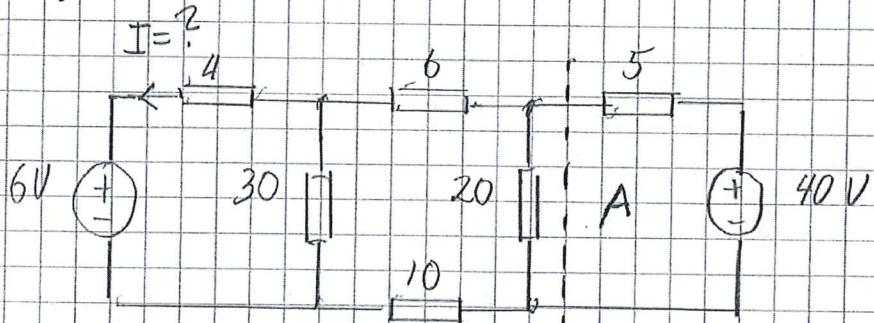


The current I can be found in multiple ways. Here source transformation is used.


Step 1: Convert A to current source

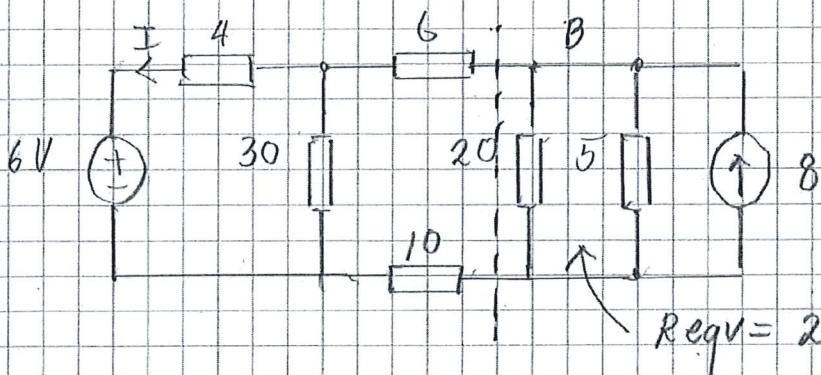


Step 2: Convert B to voltage source

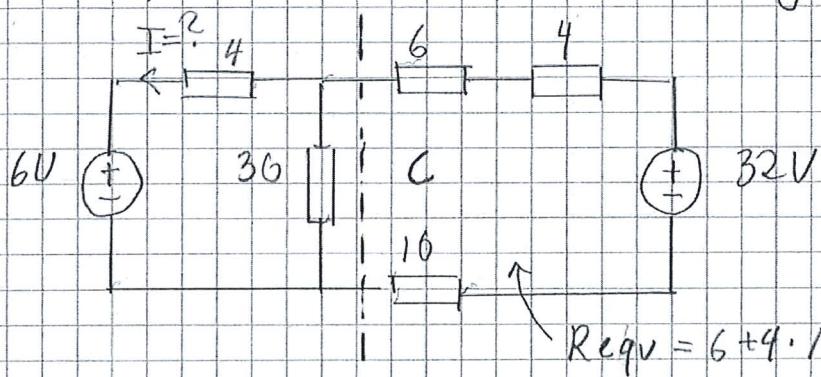

Step 3: Convert C to current source

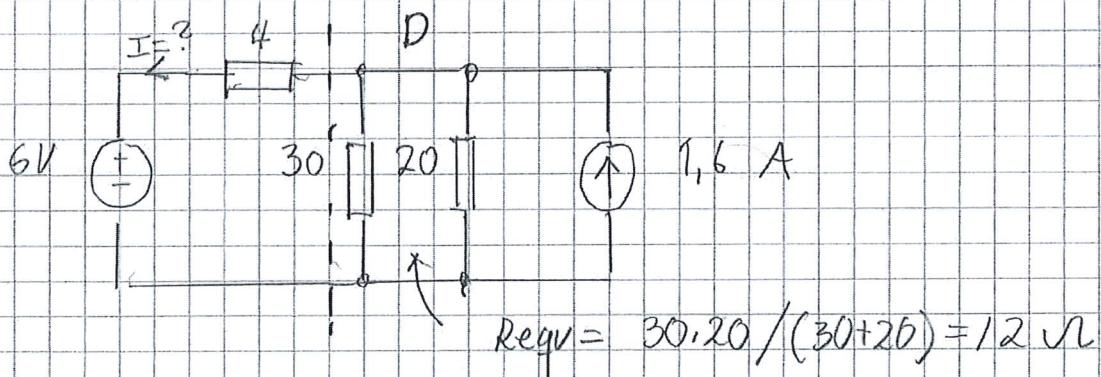

Step 4: Convert D to voltage source

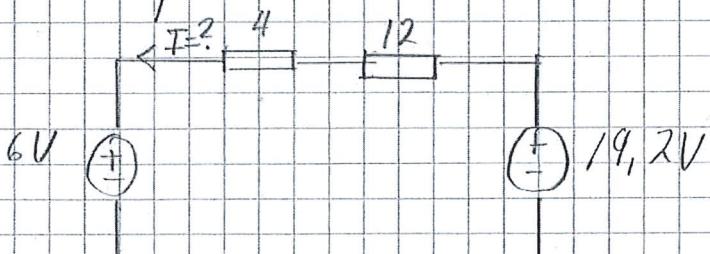

Answer:  $I = (19.2 - 6) / (4 + 12) = 0.825 [A]$

