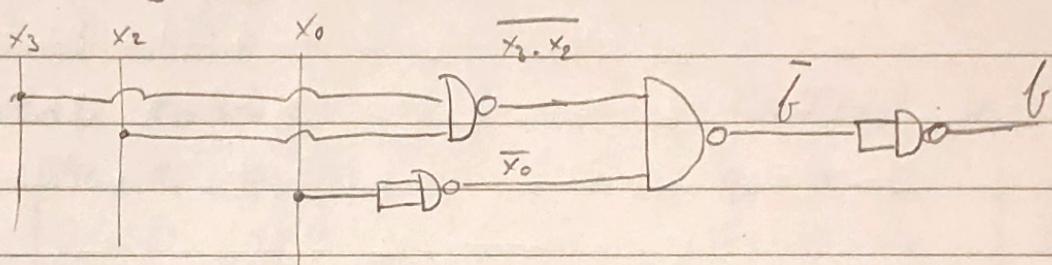


A₁


x₁ x₀

		00	01	11	10
		00	1	-	1
		01	1	-	-
x ₃ x ₂		11	-	-	
		10	1		1

$$f = \overline{x}_3 \cdot \overline{x}_0 + \overline{x}_2 \cdot \overline{x}_0 = (\overline{x}_3 + \overline{x}_2) \cdot \overline{x}_0$$
$$= \overline{x_3 \cdot x_2} \cdot \overline{x_0}$$



A_2

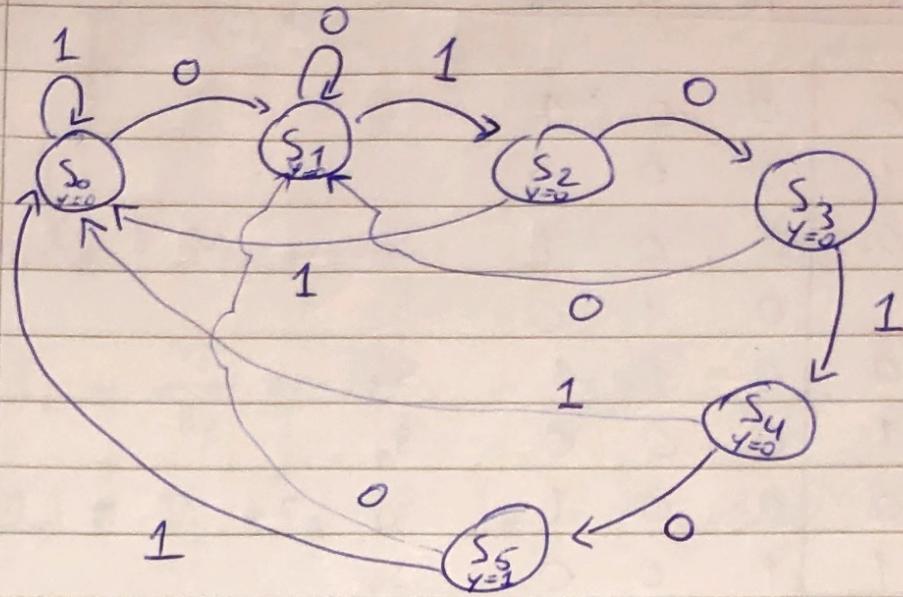

State coding:

	q_2	q_1	q_0
S_0	0	0	0
S_1	0	0	1
S_2	0	1	0
S_3	0	1	1
S_4	1	0	0
S_5	1	0	1

Output y

	q_2	q_1	q_0	y
	0	0	0	0
	0	0	1	0
	0	1	0	0
	0	1	1	0
	1	0	0	0
	1	0	1	1

(missing rows are treated as "don't care")


State Transitions

<u>q_2</u> <u>q_1</u> <u>q_0</u> <u>x</u>	<u>q_2^+</u>	<u>q_1^+</u>	<u>q_0^+</u>	
0 0 0 0	0	0	1	s_1
0 0 0 1	0	0	0	s_0
0 0 1 0	0	0	1	s_1
0 0 1 1	0	1	0	s_2
0 1 0 0	0	1	1	s_3
0 1 0 1	0	0	0	s_0
0 1 1 0	0	0	1	s_1
0 1 1 1	1	0	0	s_4
1 0 0 0	1	0	1	s_5
1 0 0 1	0	0	0	s_0
1 0 1 0	0	0	1	s_1
1 0 1 1	0	0	0	s_0

Moore type, because output y only depends on the states.

3 memory bits are used, so 3 flip-flops are needed.

A3 a)

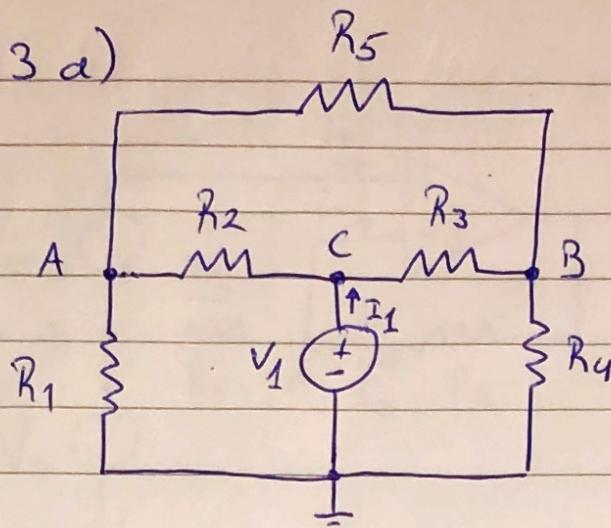

Using the method of potentials, we label each node as A, B, C, and each voltage with respect to ground is V_A , V_B , V_C .

$$V_C = V_1, \quad V_A = ?, \quad V_B = ?$$

KCL at each node with unknown voltage

$$A: -\frac{V_A}{R_1} - \frac{V_A - V_C}{R_2} - \frac{V_A - V_B}{R_5} = 0$$

$$B: -\frac{V_B}{R_4} - \frac{V_B - V_C}{R_3} - \frac{V_B - V_A}{R_5} = 0$$

$$(=) \begin{cases} -\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_5}\right)V_A + \frac{1}{R_5}V_B = -\frac{V_1}{R_2} \\ \frac{1}{R_5}V_A - \left(\frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5}\right)V_B = -\frac{V_1}{R_3} \end{cases}$$


(inserting the values for R 's and V_1 , we get:)

$$V_A = V_B = \frac{R_4}{R_3 + R_4} V_1 = \frac{5}{4} V.$$

KCL on C:

$$I_1 = \frac{V_1 - V_A}{R_2} + \frac{V_1 - V_B}{R_3} = 250 \text{ mA}$$

A3.b)

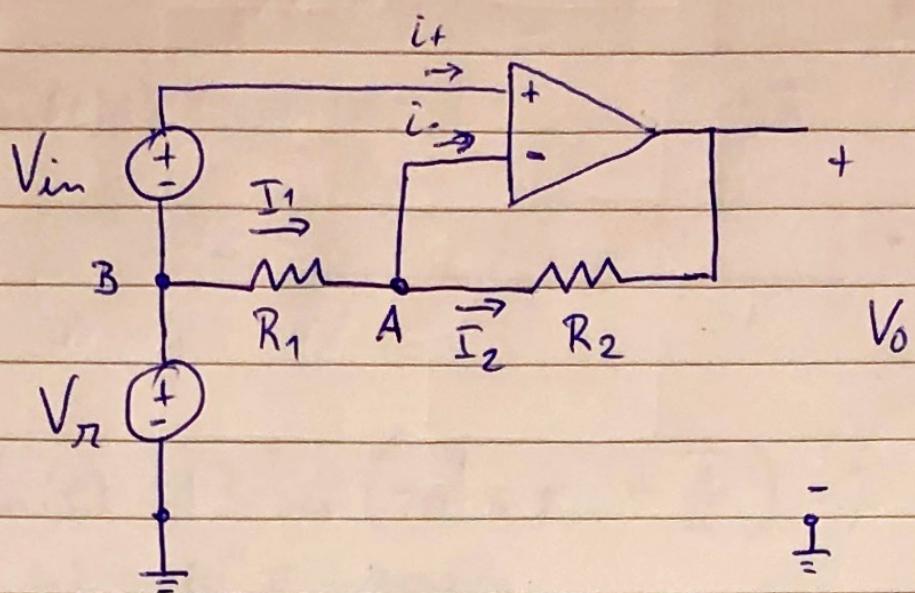

OPAMP with negative feedback :

$$i_+ = i_- = 0 \quad ; \quad v_+ = v_-$$

$$v_A = v_- = v_+ = V_{in} + V_r \quad ; \quad v_B = V_r$$


$$\text{KCL at node } A : \underbrace{\frac{v_B - v_A}{R_1}}_{= I_1} - i_- - \underbrace{\frac{v_A - v_o}{R_2}}_{= I_2} = 0$$

$$(=) \frac{V_r - V_{in} - V_r}{R_1} - \frac{V_{in} + V_r - V_o}{R_2} = 0 \quad (=)$$

$$\frac{V_o}{R_2} = \frac{V_{in}}{R_1} + \frac{V_{in}}{R_2} + \frac{V_r}{R_2} \quad (=) \quad V_o = \left(1 + \frac{R_2}{R_1}\right) V_{in} + V_r$$

$$V_o = 3V_{in} + V_r = 11 \text{ V}$$
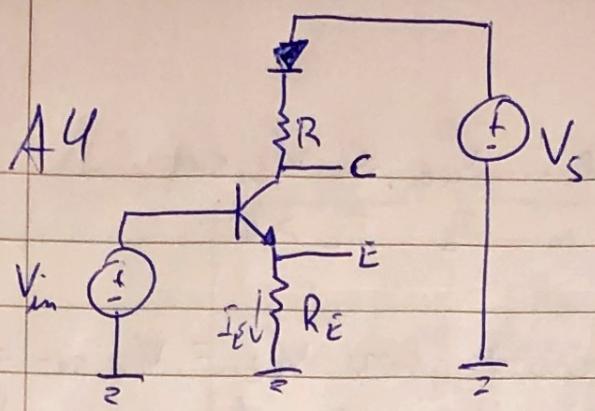
$$I_2 = \frac{V_A - V_o}{R_2} = \frac{V_{in} + V_r - V_o}{R_2} = \frac{V_{in} + V_r - 3V_{in} - V_r}{R_2} = -\frac{2V_{in}}{R_2}$$



a)

$$V_{in} - V_E = V_{BE,SAT} \quad (=) \quad V_E = V_{in} - V_{BE,SAT} = 5V$$

$$I_E = \frac{V_E}{R_E} = \frac{5}{50} = 100 \text{ mA}$$

$$I_C \approx I_E - I_B \approx I_E = 100 \text{ mA}$$

~~K.V.L.~~: $V_s - V_D - R I_C - V_{CE} - V_E = 0$

$$\Rightarrow V_{CE} = V_s - V_D - V_E - \frac{R}{R_E} V_E$$

$$= 24 - 2 + 5 - \frac{100}{50} \times 5 = 24 - 17 = 7V$$

$$I_B = \frac{1}{\beta} I_C = \frac{100 \text{ mA}}{300} = \frac{1}{3} \text{ mA} = 333 \mu\text{A}$$

$\therefore I_B > 0, I_C > 0, V_{CE} > V_{CE,SAT} \Rightarrow \text{Active region}$

$$R_E = ?$$

A 4.b). Saturation mode: $V_{CE} \leq V_{CE,SAT}$
 $I_B, I_C > 0$.

Let us analyze the circuit for $V_{CE} = V_{CE,SAT} = 0.2 \text{ V}$
(border between the saturation and active regions)


From A 4.a): $I_C \approx I_E = \frac{5}{R_E}$

KVL: $V_S - V_D - R I_C - V_{CE} - V_E = 0 \quad (=)$

$$\frac{5R}{R_E} = 24 - 2 - 0.2 - 5 \quad (=) \quad R_E = \frac{500}{16.8} \approx 29.7 \Omega$$

$R_E = 29.7 \Omega$ is the largest value for which the BJT is in saturation.

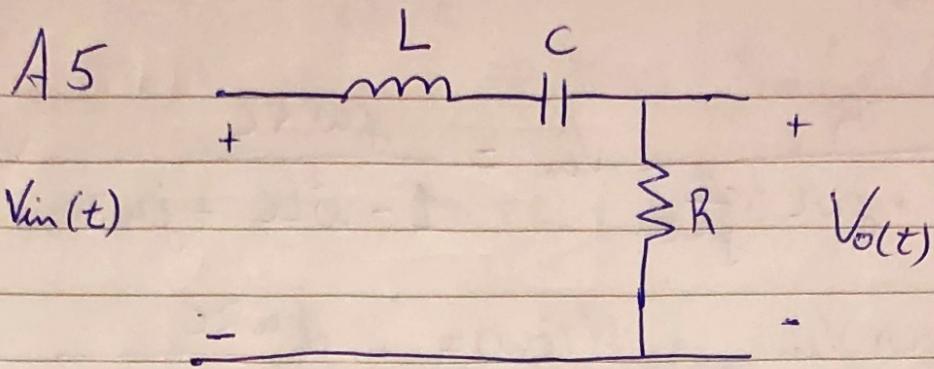+ A larger R_E than 29.7Ω will decrease $I_E = \frac{B_5}{R_E}$, decrease $I_C \approx I_E$, which will make V_{CE} increase above $V_{CE,SAT}$ so that the KVL holds (note that, in the KVL, V_S , V_D , and V_E are constant, so only I_C and V_{CE} can vary).



$$V_{in}(t) = 3 \sin(10^4 \pi t + \frac{\pi}{2}) ; V_o(t) = ?$$


$\omega = 10^4 \pi \text{ rad/s}$

i) Associate $V_{in}(t)$ to a varying complex voltage
 $V_{in}(t) = \text{Im}(V_{cin}(t)) ; V_{cin}(t) = 3 \cos(10^4 \pi t + \frac{\pi}{2}) + j3 \sin(10^4 \pi t + \frac{\pi}{2})$

In polar form: $V_{cin}(t) = 3 e^{j(10^4 \pi t + \frac{\pi}{2})}$

$$= \underbrace{3 e^{j\frac{\pi}{2}}}_{= V_{in}} \times e^{j\omega t} = V_{in} \times e^{j\omega t}$$

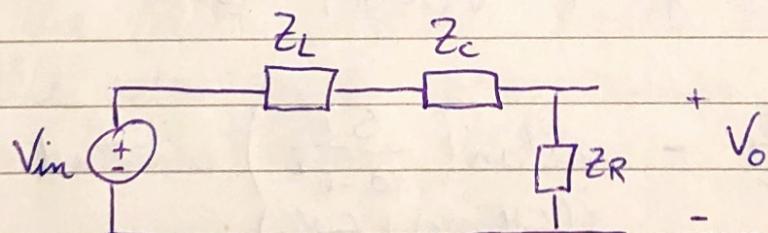For AC analysis, we convert the AC circuit to a DC circuit with constant complex voltage and complex impedances:



Where $V_{in} = 3 e^{j\frac{\pi}{2}}$, $V_o = ?$, $Z_R = R$, $Z_L = j\omega L$, $Z_C = \frac{1}{j\omega C}$
 From KVL, we get:

$$V_o = \frac{Z_R}{Z_R + Z_L + Z_C} V_{in}$$

A5 (cont.)

$$V_o = \frac{R}{R + j\omega L + \frac{1}{j\omega C}} V_{in} = \frac{j\omega R C}{1 - \omega^2 LC + j\omega R C} V_{in}$$

$$V_o = H(j\omega) V_{in} ; H(j\omega) = \frac{j\omega R C}{1 - \omega^2 LC + j\omega R C}$$

$$\omega = 10^4 \pi \text{ rad/s}$$

$$R = 50 \Omega , C = 10^{-6} F , L = 10^{-3} H$$

$$H(j10^4 \pi) = \frac{j10^4 \pi \cdot 50 \cdot 10^{-6}}{1 - 10^8 \pi^2 \cdot 10^{-9} + j10^4 \pi \cdot 50 \cdot 10^{-6}} = \\ = \frac{j5\pi \times 10^{-1}}{1 - 10^{-1}\pi^2 + j5\pi \times 10^{-1}} = \frac{j5\pi}{10^{-1}\pi^2 + j5\pi}$$

To solve $V_o = H(j\omega) V_{in}$, we need to convert $H(j\omega)$ into polar form: $H(j\omega) = |H(j\omega)| e^{j\angle H(j\omega)}$

$$|H(j10^4 \pi)| = \frac{|j5\pi|}{\sqrt{(10^{-1}\pi^2)^2 + (5\pi)^2}} = \frac{5\pi}{\sqrt{(10^{-1}\pi^2)^2 + (5\pi)^2}}$$

$$\angle H(j10^4 \pi) = \frac{\pi}{2} - \arctan\left(\frac{5\pi}{10^{-1}\pi^2}\right) \text{ rad}$$

$j(\angle H(j10^4 \pi) + \angle V_{in})$

$$V_o = |H(j10^4 \pi)| \cdot |V_{in}| \times e^{j(\pi - \arctan(\frac{5\pi}{10^{-1}\pi^2}))}$$

(A5 cont. 2)

$$V_{co}(t) = V_0 \times e^{j10^4\pi t} \Rightarrow V_o(t) = \text{Im}(V_{co}(t))$$

$$V_o(t) = |V_0| \sin(10^4\pi t + \angle V_0)$$

$$= \frac{15\pi}{\sqrt{(10^{-\pi^2})^2 + 25\pi^2}} \sin(10^4\pi t + \pi - \arctan(\frac{5\pi}{10^{-\pi^2}}))$$

To determine the type of filter, we look at $H(jw)$ and how it varies with w .

$$|H(j0)| = \frac{0}{1} = 0$$

$$\lim_{w \rightarrow \infty} |H(jw)| = \lim_{w \rightarrow \infty} \left| \frac{jwRC}{1 - w^2LC + jwRC} \right| \leq$$

$$\approx \lim_{w \rightarrow \infty} \left| \frac{jwRC}{-w^2LC} \right| = \lim_{w \rightarrow \infty} \frac{|jR|}{|wL|} = 0$$

The filter blocks both the very low and the very high frequencies, so it is a Band-Pass filter.