

1

1.a In the circuit shown below, determine the current flowing through the 10V voltage source.

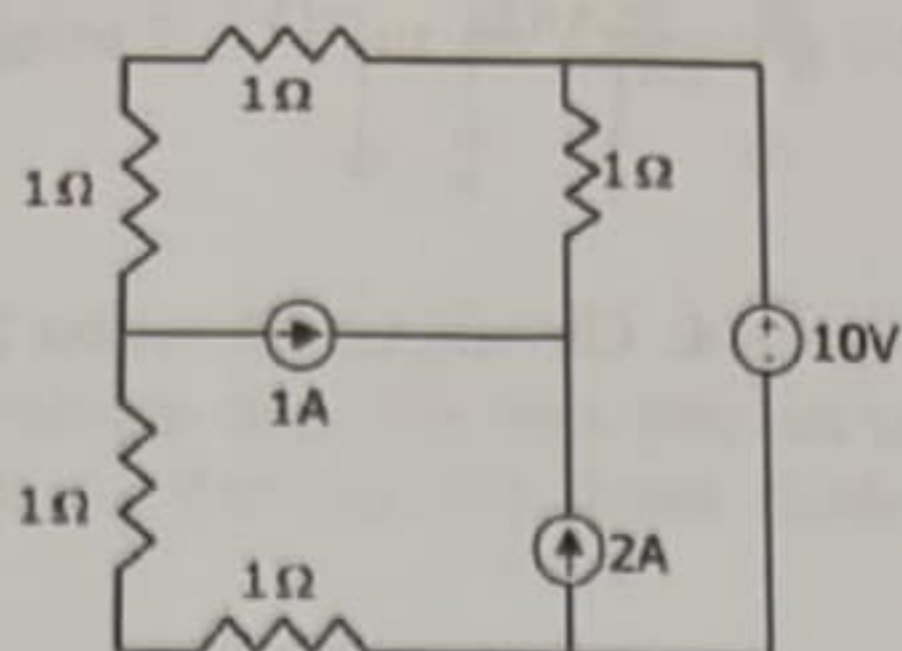


Figure 1: Circuit for Question 1.a.

(1.a: 4pt)

1.b The switch in the following circuit was on position 'a' for a long time, and then moved to position 'b' at time $t = 0$. Determine the current $i(t)$ at $t > 0$.

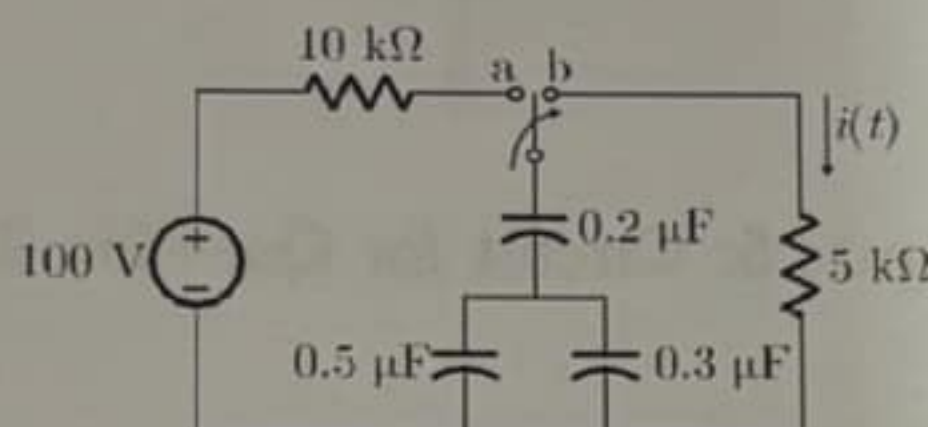


Figure 2: Circuit for Question 1.b.

(1.b: 3 pt)

1.c For the circuit shown below, $R_1 = R_2 = R_4 = 1\Omega$ and $R_3 = 1.1\Omega$. Determine the value of the voltage drop V_{ab} .

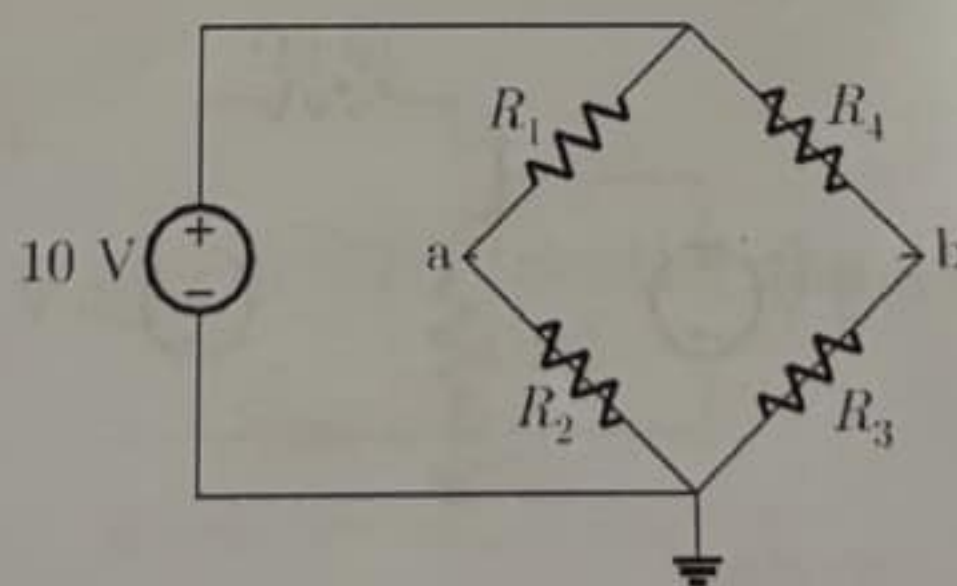


Figure 3: Circuit for Question 1.c.

(1.c: 3 pt)

(Sub-Total Question 1: 10 pt)

2

- 2.a Determine the value of current I through the resistance r in the following circuit.

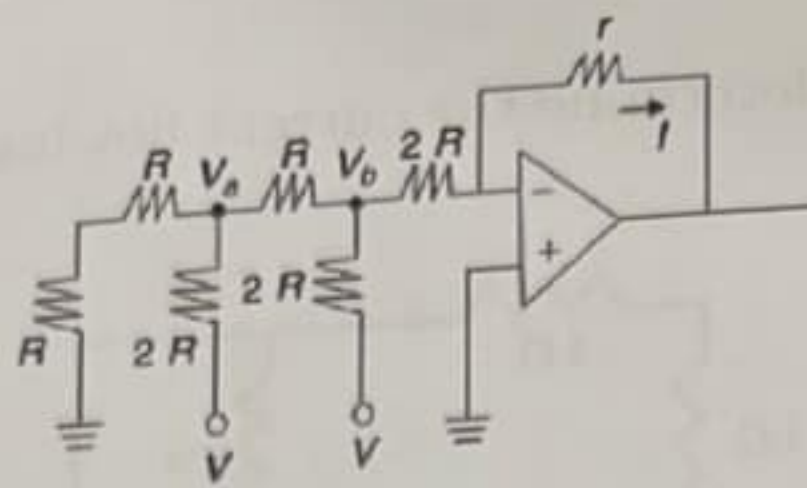


Figure 4: Circuit for Question 2.a.

(2.a: 5 pt)

- 2.b Determine the value of the output voltage in the following circuit.

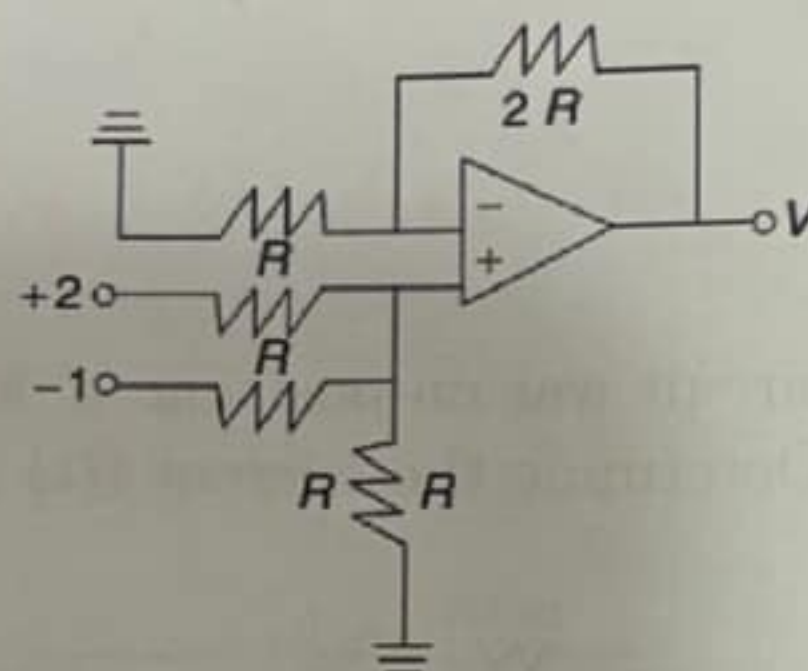


Figure 5: Circuit for Question 2.b.

(2.b: 5 pt)

(Sub-Total Question 2: 10 pt)

3

- 3.a In the following circuit, assume that β is very large and $V_{BE} = 0.7V$. Determine the mode of operation of the BJT.

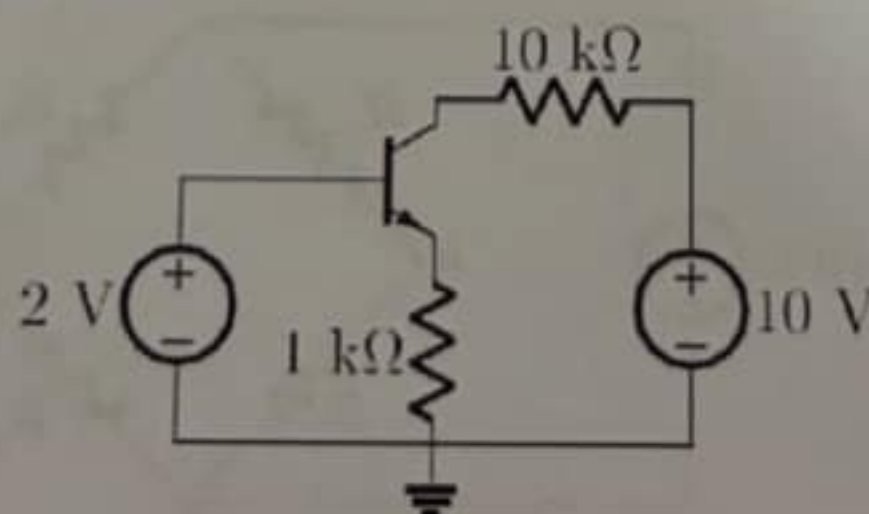


Figure 6: Circuit for Question 3.a.

(3.a: 4 pt)

- 3.b In the following circuit, determine the current through the ideal diode ($V_{BE} = 0V$).

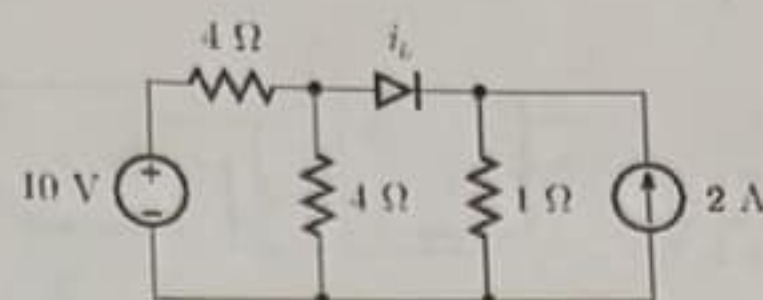


Figure 7: Circuit for Question 3.b.

(3.b: 4 pt)

- 3.c Draw a hand sketch of the voltage drop V_R with respect to time. Show the voltage values and the required calculations. Assume the Zener diode to be ideal with a breakdown voltage of 6V.

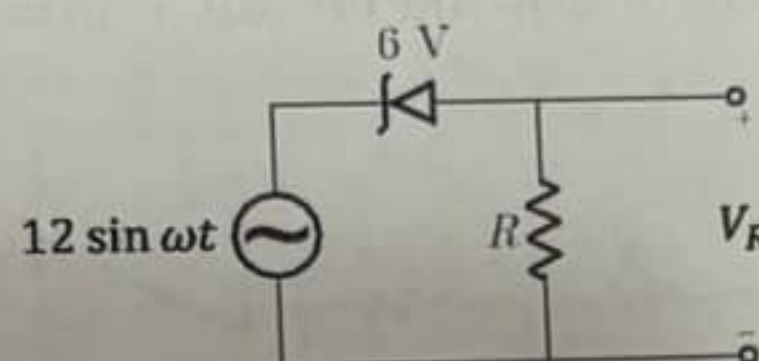


Figure 8: Circuit for Question 3.c.

(3.c: 2 pt)

(Sub-Total Question 3: 10 pt)

4

- 4.a If $X = 1$ in the following logic equation, determine $Y = ?$ and $Z = ?$.
 $[X + Z\{\bar{Y} + (\bar{Z} + XY)\}]\{\bar{X} + \bar{Z}(X + Y)\} = 1$.

(4.a: 2 pt)

- 4.b Simplify the following Boolean expression using K-map and design the circuit using NAND gates only.

$$F(w, x, y, z) = wy + xy + \bar{w}xyz + \bar{w}\bar{x}y + xz + \bar{x}\bar{y}\bar{z}.$$

(4.b: 3 pt)

- 4.c For the following circuit, $Y = AB + \bar{C}\bar{D}$. Identify the gates G1 and G2.

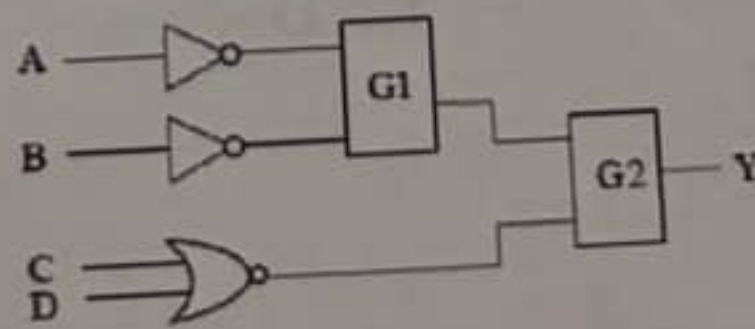


Figure 9: Circuit for Question 4.c.

(4.c: 2 pt)

- 4.d For following circuit, $t < t_0$, $Q_1 = Q_2 = 0$. The input X is shown in the figure. Draw a hand sketch of the output Y .

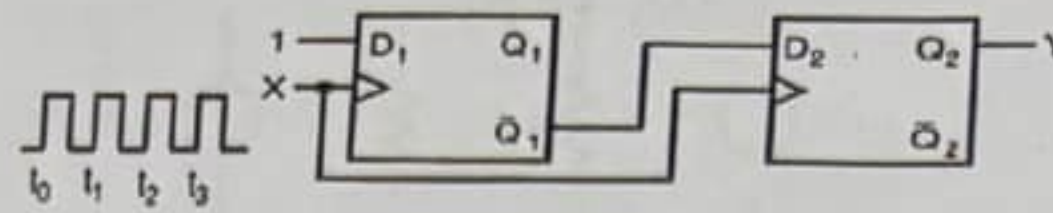


Figure 10: Circuit for Question 4.d.

(4.d: 3 pt)

(Sub-Total Question 4: 10 pt)

5

- 5.a Determine the type of filter the following circuit represents. Motivate your answer.

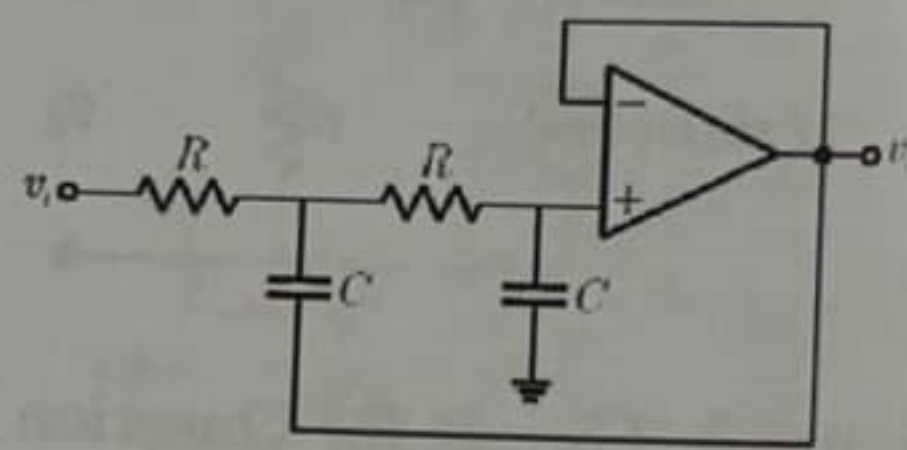


Figure 11: Circuit for Question 5.a.

(5.a: 5 pt)

- 5.b In the following circuit, input $v_i = V_p \cos(t/RC)$. Determine the steady-state output v_o .

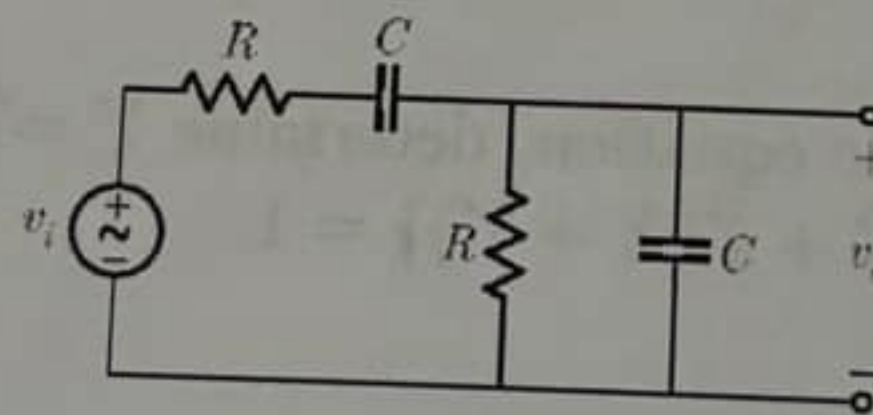


Figure 12: Circuit for Question 5.b.

(5.b: 5 pt)

(Sub-Total Question 5: 10 pt)

— END —