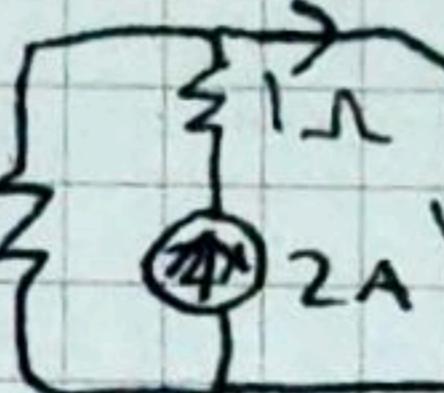


1a) Superposition

① nollställ Övriga: 2Ω

Bidrag: $0,5A$ riktnings nedåt (spänningsskälles)

② nollställ Övriga: 4Ω



$\Sigma 32$

* 4


19F3D-0084-YUH

Ark 1.

Get $I = 0,5A$

Bidrag: $2A$ riktnings nedåt (spänningsskälles)

③ $10V$ nollställ Övriga: 4Ω

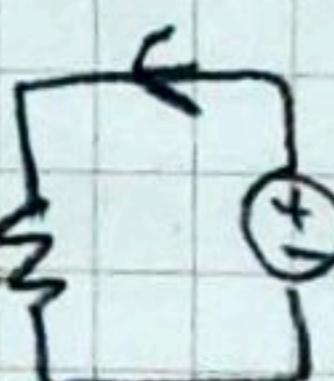

$$I = \frac{U}{R} = \frac{10}{4} = 2,5A$$

Bidrag: $2,5A$ riktnings uppåt (spänningsskälles)

Summa bidrags: $2A + 0,5A - 2,5A = 0A$

SVAR: Strömmen genom spänningsskällan är $0A$

4 ✓

* Miss i svaret på 4c väger upp!

1b) The capacitors are fully charged

after "long time" - combined voltage drop: 100V

Capacitors in parallel: $C_E = C_1 + C_2 \rightarrow 0,5\text{NF} + 0,3\text{NF} = 0,8\text{NF}$

Capacitors in series: $C_E = \frac{C_1 \cdot C_2}{C_1 + C_2} \rightarrow \frac{0,2\text{NF} \cdot 0,8\text{NF}}{0,2\text{NF} + 0,8\text{NF}} = 0,16\text{NF}$

$V_B = 100\text{V}$ (combined voltage drop) $R = 5\text{k}\Omega$ $C = 0,16\text{NF}$ ✓

$$I_C = \frac{V_B}{R} \cdot e^{\left(\frac{-t}{RC}\right)} \quad I_C = 0,02 \cdot e^{-800t} \text{ A}$$


2

ANSWER: $I_C = 0,02 \cdot e^{-800t} \text{ A}$ ✗

1c) RHE circuit is made up of
two voltage dividers. $R_1 = R_2 = R_4 = 1\Omega$ $R_3 = 1,1\Omega$

19F3D-0084-YUH

Ark 3

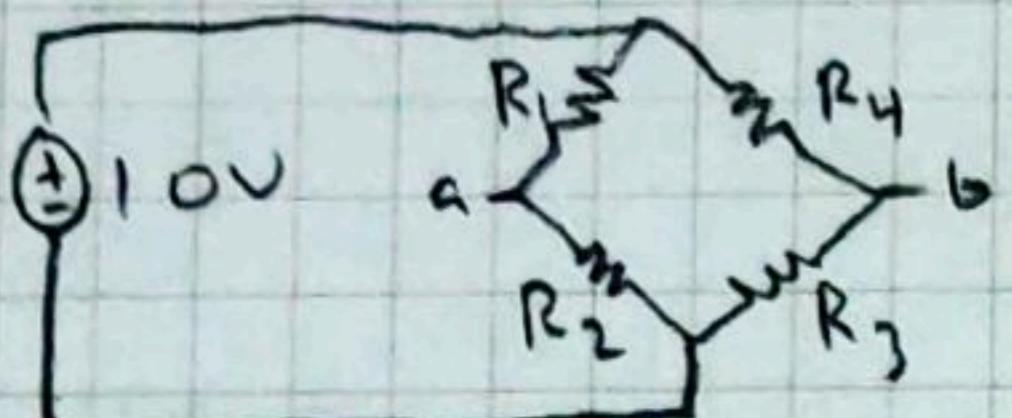


$$V_a = 10 \cdot \frac{1}{2} = 5V \quad V_b = 10 \cdot \frac{1,1}{2} = 5,5V$$

$$V_{ab} = V_a - V_b = 5V - 5,5V = -0,5V \quad \text{Voltage drop } V_{ab} = 0,5V$$

ANSWER: $V_{ab} = 0,5V$ X

①

7
Q1

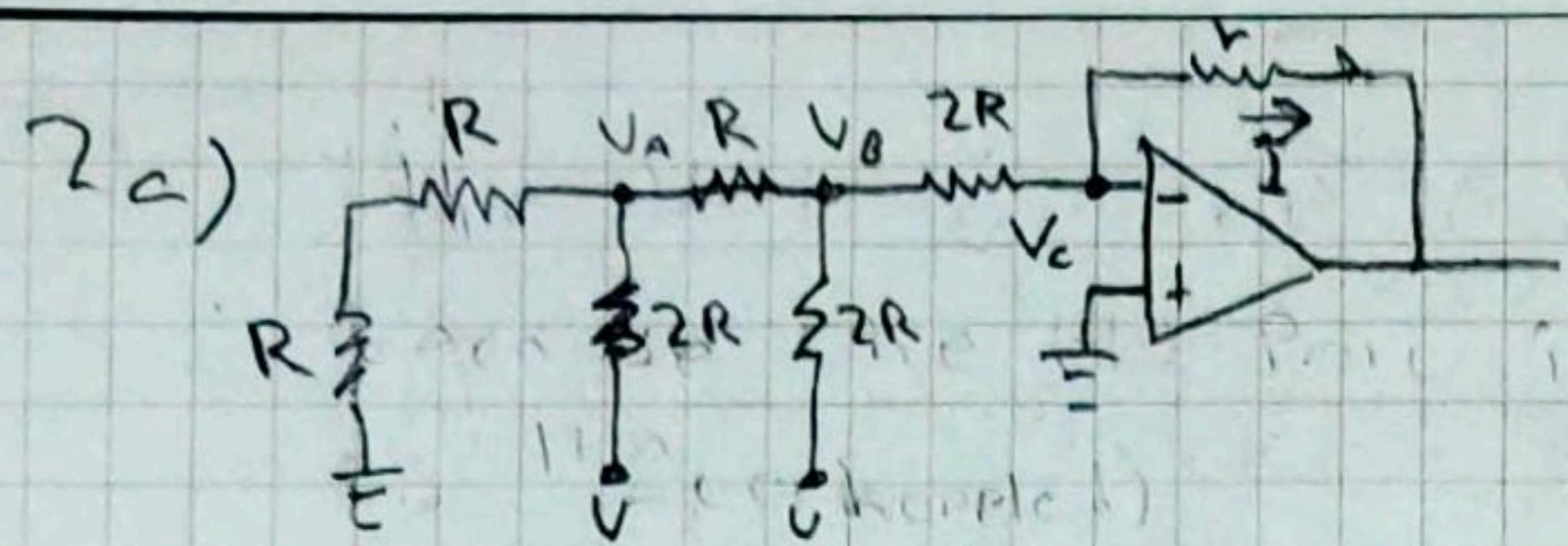

Grounded

and
"across op-amp"

$$\rightarrow V_C = 0$$

19F3D-0084-YUH

Ark 4

Voltage divider at V_A and V_B : $V_A = V \cdot \frac{2R}{4R} = \frac{V}{2}$, $V_B = V \cdot \frac{2R}{4R} = \frac{V}{2}$

$$V_A = V_B$$


Current from V_B to V_C : $I = \frac{V}{R}$ $I = \frac{\frac{V}{2}}{2R} = \frac{V}{4R}$ A

No current enters OP-amp (-) Port C under ideal conditions

\rightarrow Some current through resistor r.

ANSWER: $I = \frac{V}{4R}$ A

5

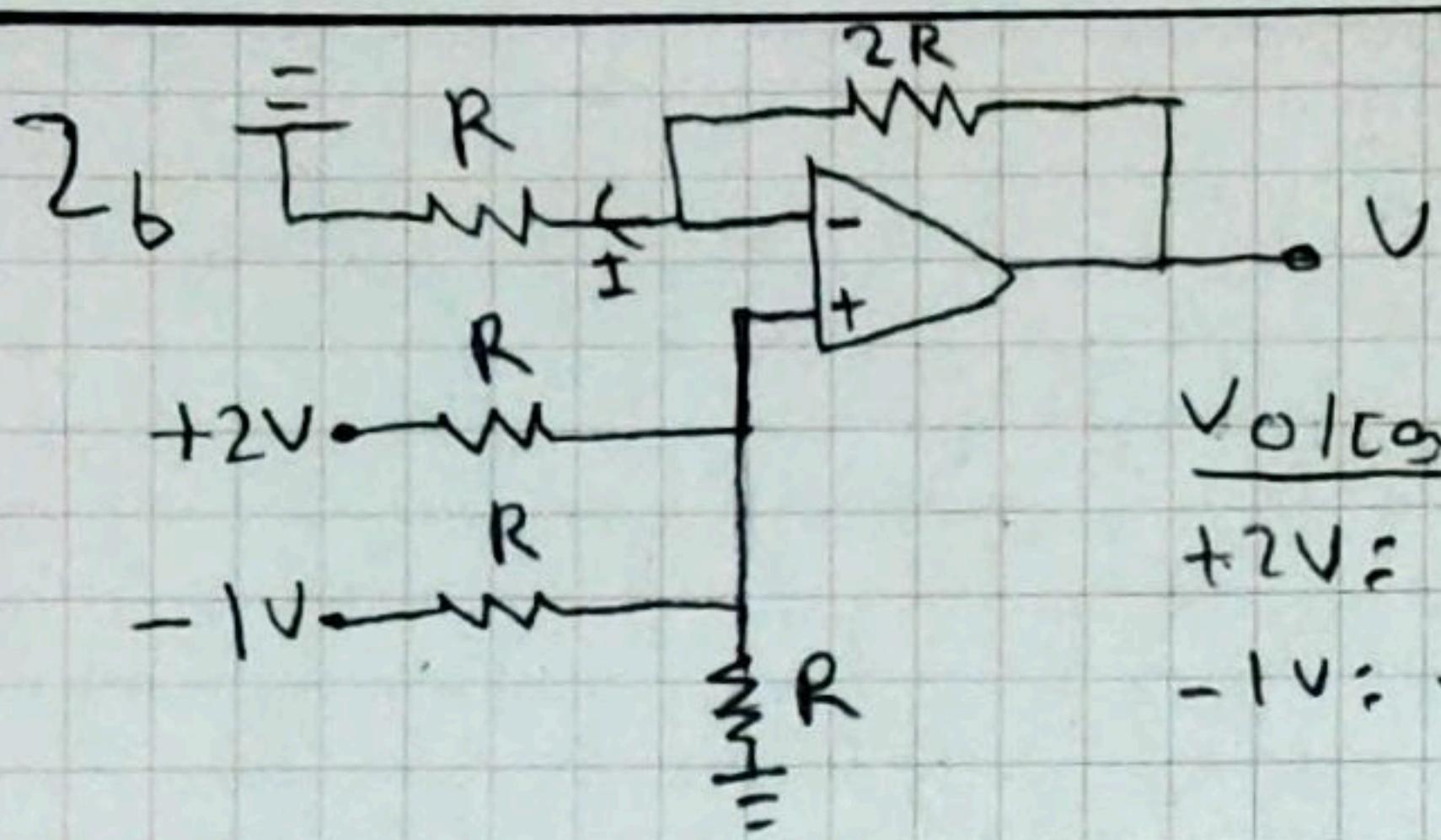

19F3D-0024-YUH

Ark 5

Voltage divider

$$+2V = 2 \cdot \frac{R}{2R} = 1V$$

$$-1V = -1 \cdot \frac{R}{2R} = -\frac{1}{2}V$$

$$\text{sum: } 1V - \frac{1}{2}V = \frac{1}{2}V \quad V_+ = \frac{1}{2}V$$

$V_+ = V_-$ gives current to the left over $R \quad I = \frac{1}{R} = \frac{1}{2R} A$


$$V_o - V_- = 2R \cdot \frac{1}{2R} = 1V \quad V_o = 1V + 0,5V = 1,5V$$

ANSWER: $V_o = 1,5V$ (output voltage)

X'

①

6
62

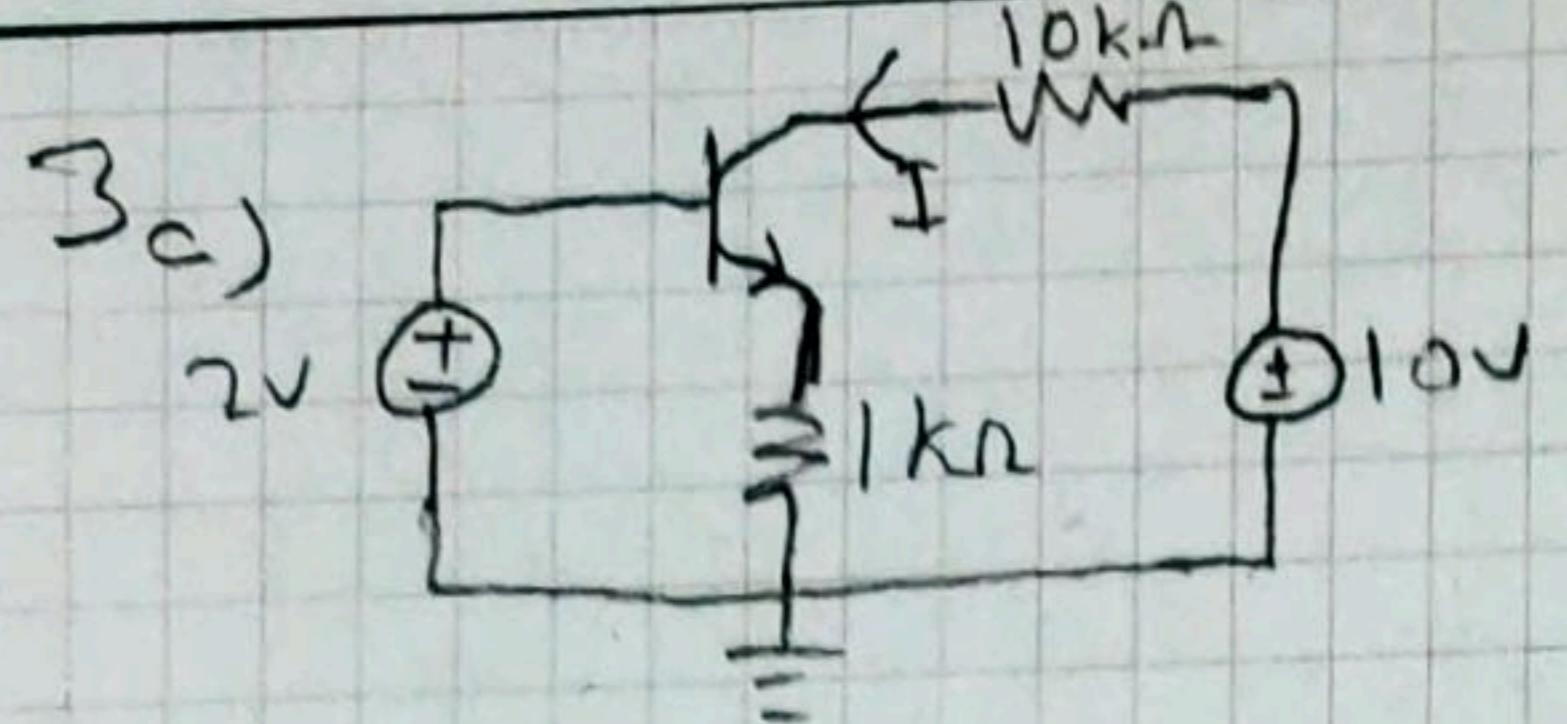

β (very large)
 $V_{BE} = 0.7V$

$V_B = 2V$ and $V_{BE} = 0.7V$ gives $V_E = 2V - 0.7V = 1.3V$


$I = \frac{V}{R}$ $I = \frac{1.3}{1k} = 1.3mA$ assuming large β $I_E \approx I_C$

Voltage over 10kΩ resistor $U = R \cdot I$ $U = 10k \cdot 1.3m = 13V$
 And max I_C for active region is $\frac{U_t}{R_{CK}} = \frac{10}{10k} = 1mA$ not possible

as $1.3mA > 1mA$ The transistor is saturated.

ANSWER: Mode of operation is "saturated"

④ ✓

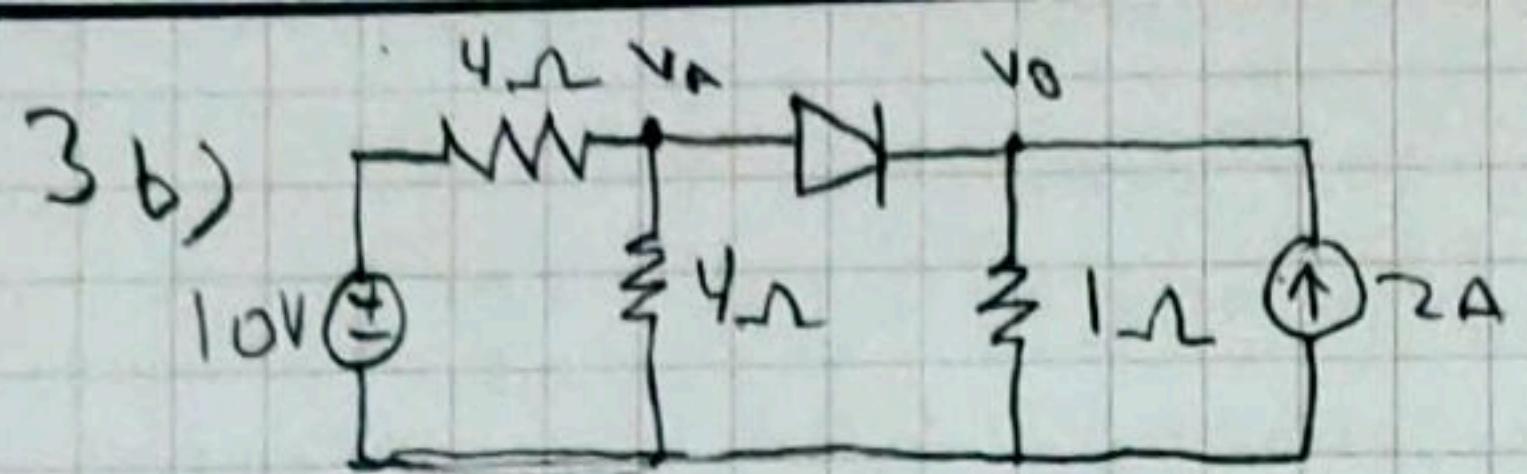

Ideal diode $V_{BE}=0V$

19F3D-0084-YUH

ARK)

Current through diode if Voltage is 0V or more
from left to right. D

No current through diode: $V_A = 10 \cdot \frac{4}{8} = 5V$ $V_B = 2 - 1 = 2V$

→ The diode will let through current as long as $V_A \geq V_B$

Because the current through the current source


results in a 2V drop across the 10Ω resistor

Those Z_0 will not draw any current from the 10V source

Chlorophyll

3c) Zener diode ideal and breakdown voltage 6V

19 F3D-0084-YUH
Ark 8

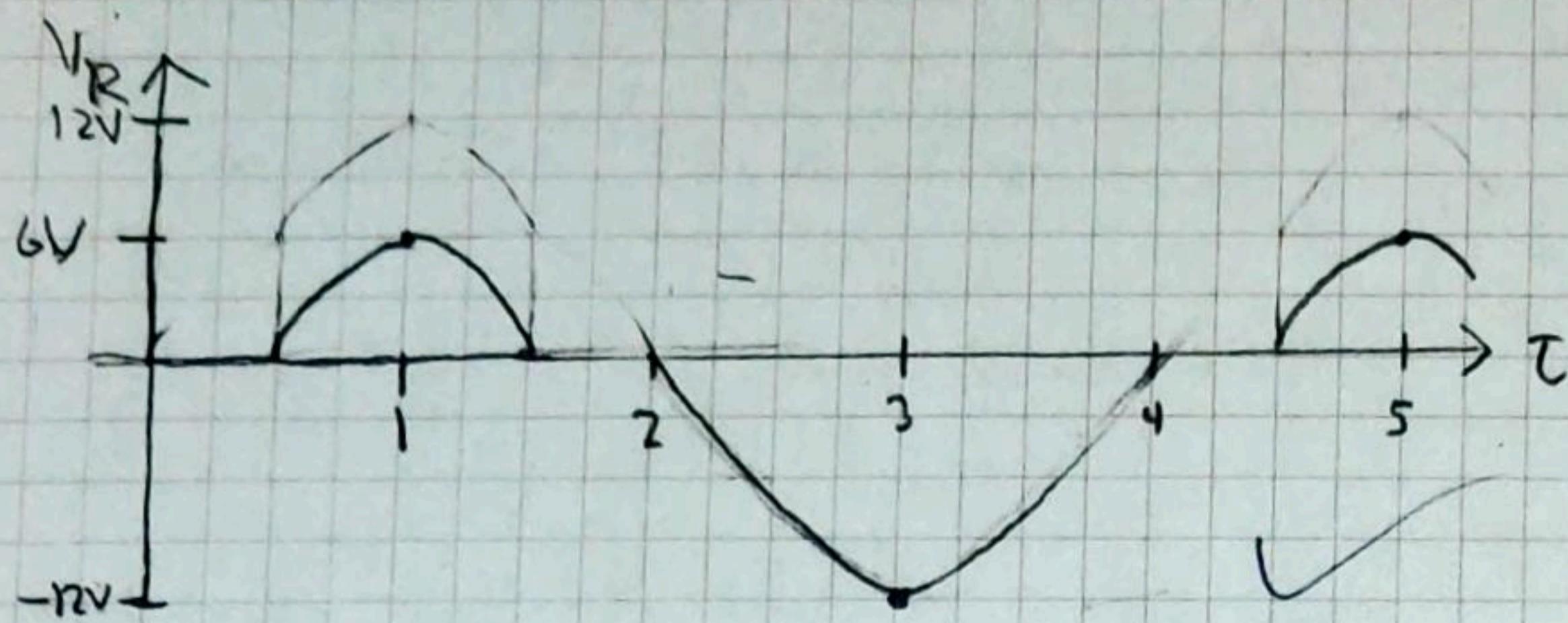

$$12 \cdot \sin \omega t$$

$$\omega = \pi \text{ (for sketching)}$$

②

The voltage over the Zener diode increases, but the voltage over R does not, because no current is flowing. Then at breakdown voltage current is again flowing, but the Zener diode has a voltage drop of 6V so the voltage V_R has its maximum at 6V (half on diode, half on resistor). When the direction is reversed the diode has $V_{BD} = 0V$ and can be neglected.

6
Q3

$$4a) (x + \bar{z}(\bar{Y} + (\bar{z} + x\bar{Y}))) (\bar{x} + \bar{z}(x + Y)) = 1 \quad \boxed{19F3D-0084-YUH} \quad \boxed{\text{Ans 9}}$$

$$x=1 \text{ gives } (1 + \bar{z}(\bar{Y} + (\bar{z} + 1 \cdot \bar{Y}))) (0 + \bar{z}(1 + Y)) = 1$$

$$\begin{array}{l} 1+b=1 \\ 1 \cdot b=b \end{array} \Rightarrow \bar{z}=1$$

$x=0$ and $\bar{z}=0$ gives: (for ①)

$$(1 + 0(\bar{Y} + (1 + 1 \cdot \bar{Y}))) (0 + 1(1 + Y)) = 1$$

$$\begin{array}{l} 0 \cdot b=0 \\ 1+b=1 \\ 1 \cdot b=b \end{array} \Rightarrow 1+Y=1$$

Y can be
whatever

ANSWER: $x=1$ and $\bar{z}=0$, Y can be both 1 and 0

(2)



19F3D-0084-YUH
Ark 10

$$46) F(w, x, y, z) = \underline{w}y + \underline{x}y + \underline{\underline{w}}\underline{x}yz + \underline{\underline{w}}\underline{\underline{x}}y + xz + xy\bar{z}$$

w, x	Y, z	0001	11	10
- 00	1	0	1	1
- 01	0	1	1	1
- 11	0	1	1	1
- 10	1	1	0	1


3 circled groups of 2ⁿ

1. xz
2. $\bar{x}\bar{z}$
3. y
4. yx

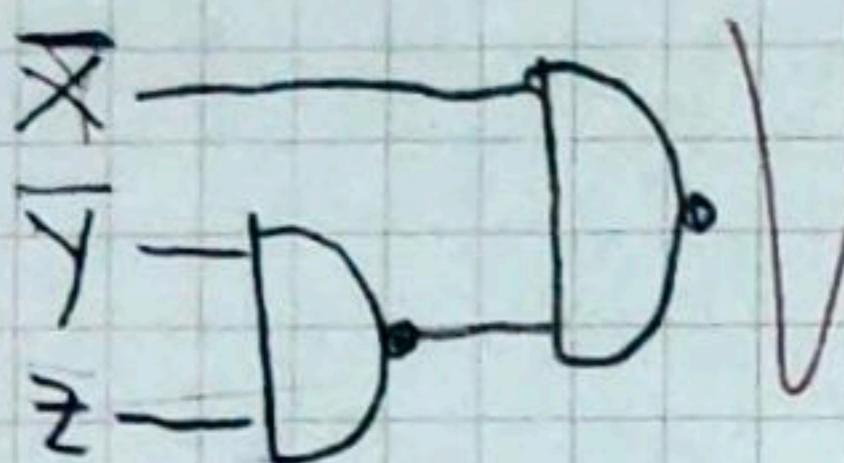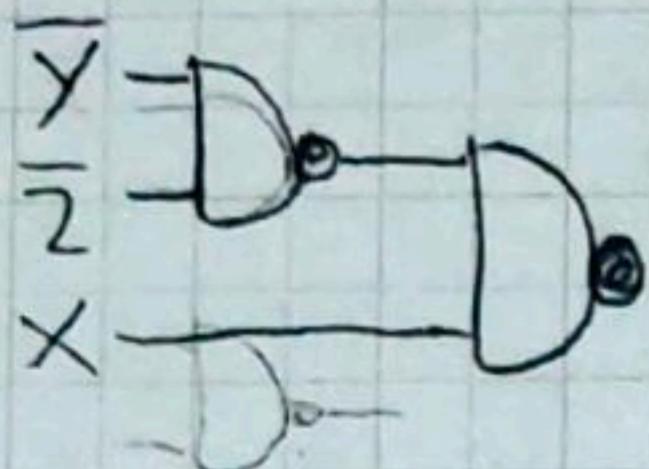

Q

$$4c) Y = AB + \bar{C}\bar{D}$$

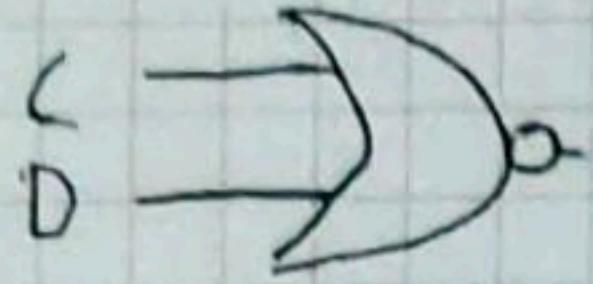

C	B	out
0	0	1
0	1	0
1	0	0
1	1	0

$$\Leftrightarrow \bar{C}\bar{B}$$

$$A \rightarrow D = \bar{A}$$

$$B \rightarrow D = \bar{B}$$

A	B	desired
0	0	1
0	1	0
1	0	0
1	1	0

$$\Rightarrow \text{Gate } G1 = \text{NOR} \Leftrightarrow AB$$


R

$$\text{and then since } G2 = \text{OR} \Leftrightarrow AB + \bar{C}\bar{D}$$

$$\text{ANSWER: } G1 = \text{NOR} \text{ and } G2 = \text{NOR}$$

???

①

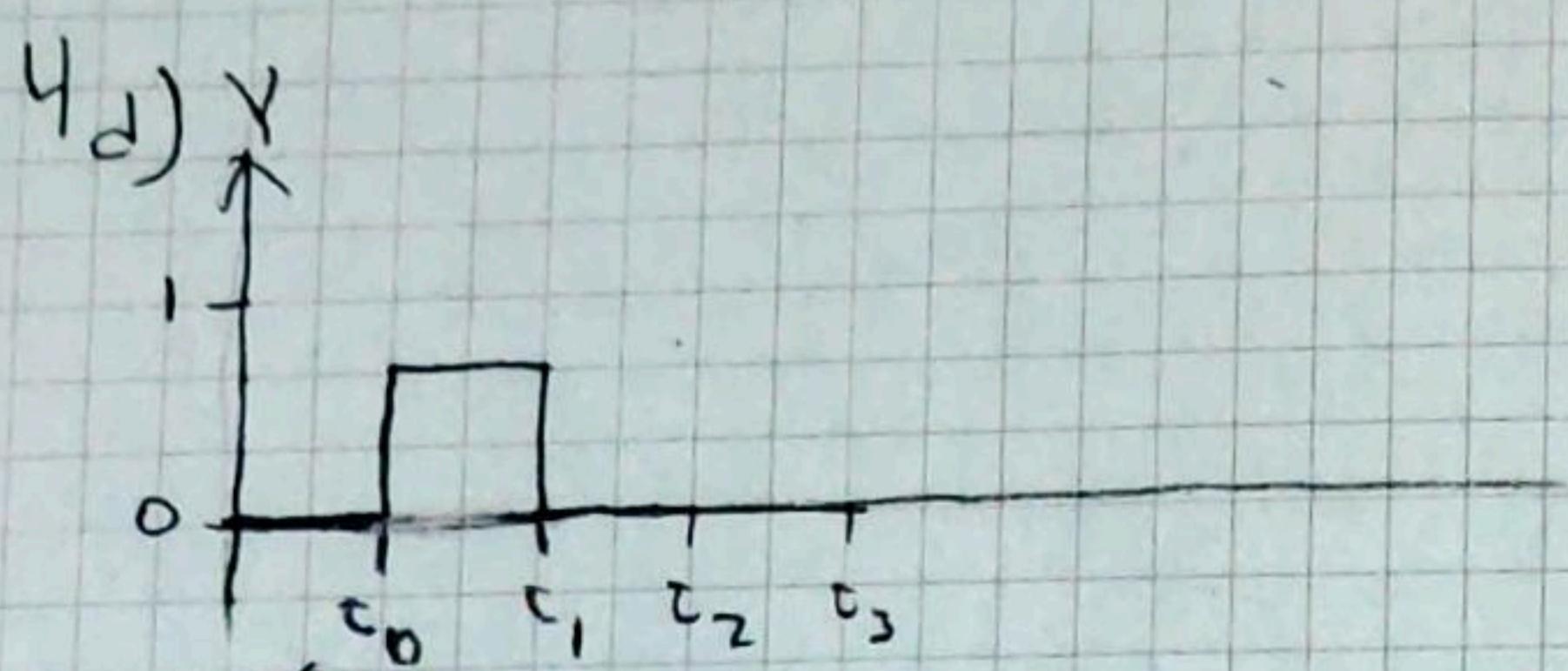

t₀ First CLK $Q_1 = 1$ and $Q_2 = 1$ (\bar{Q}_1 is first on 1)


t₁ Second CLK $Q_1 = 1$ and $Q_2 = 0$ (\bar{Q}_1 changed last CLK)

t₂ Third CLK $Q_1 = 1$ and $Q_2 = 0$ (\bar{Q}_1 still 0)

t₃ Fourth CLK $Q_1 = 1$ and $Q_2 = 0$ (\bar{Q}_1 still 0)

(3)

ES

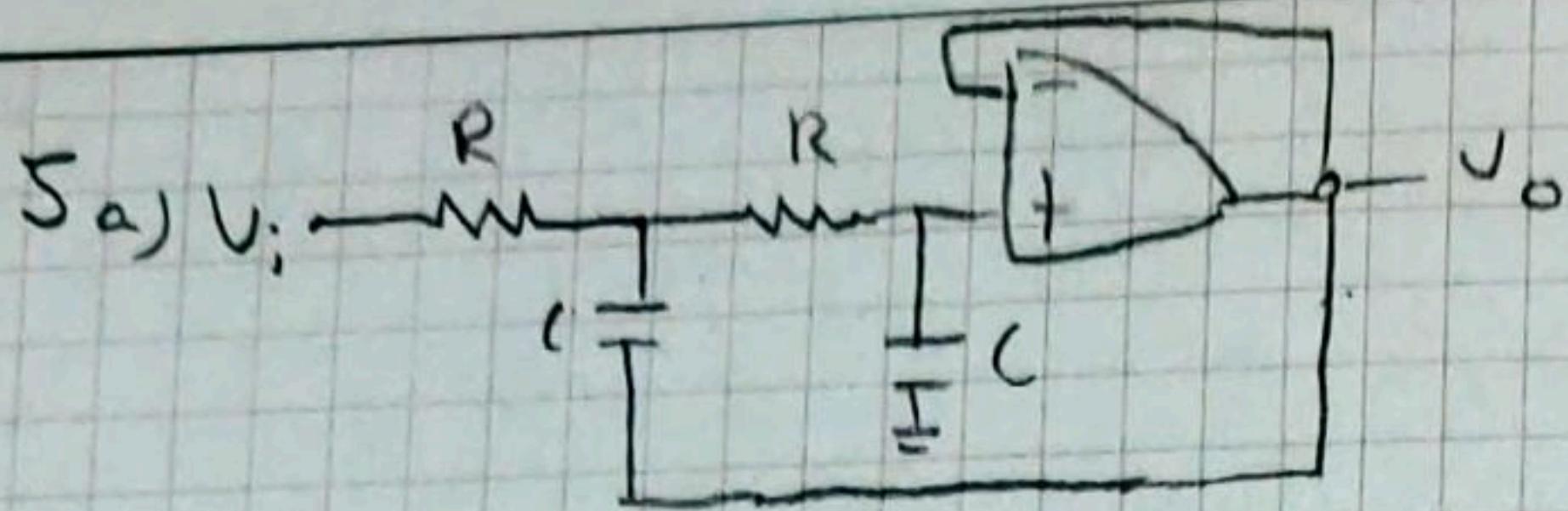

First we determine the transfer function $H(j\omega) = \frac{V_o}{V_i}$

$$V_{in} = Z_R + Z_R + Z_C = 2R + \frac{1}{j\omega C} \text{ series capacitors}$$

$$V_{out} = Z_C + Z_R + Z_L = R + \frac{j\omega C - j\omega C}{j\omega C + j\omega C} = R + \frac{j\omega C}{2}$$

$$H(j\omega) = \frac{R + \frac{j\omega C}{2}}{2R + \frac{1}{j\omega C}} = \frac{R \cdot j\omega C - \frac{1}{2} \omega^2 C^2}{2Rj\omega C + 1}$$

Extreme values $\omega \rightarrow 0$ or $\omega \rightarrow \infty$?

$$\lim_{\omega \rightarrow 0} H(j\omega) = 0 \quad \lim_{\omega \rightarrow \infty} H(j\omega) = -\frac{C^2}{4R^2C} = -\frac{C}{4R^2}$$


\Rightarrow High pass filter

ANSWER: It is a Highpass filter circuit.

5b) $V_i = V_p \cos(\omega t / RC)$ determine V_o

19F3D-0084-YUH

Ark 14

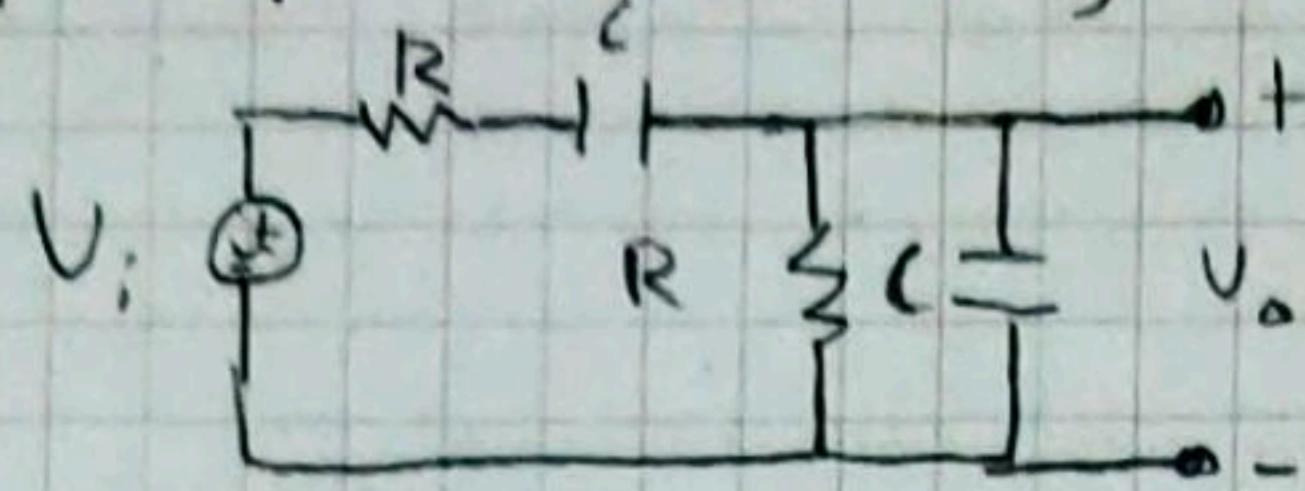

Transfer function: $H(j\omega) = \frac{V_o}{V_i}$

$$V_i \neq (Z_R + Z_C + Z_R || Z_C) I = \left(R + \frac{1}{j\omega C} + \frac{R}{Rj\omega C + 1} \right) I$$

$$V_o = Z_R || Z_C I = R || \frac{1}{j\omega C} = \frac{\frac{R}{j\omega C}}{R + \frac{1}{j\omega C}} = \frac{R}{Rj\omega C + 1} \cdot I$$

$$H(j\omega) = \frac{\frac{R}{Rj\omega C + 1}}{R + \frac{1}{j\omega C} + \frac{R}{Rj\omega C + 1}} = \frac{R}{R(Rj\omega C + 1) + \frac{Rj\omega C + 1}{Rj\omega C} + R} = \frac{R^2 j\omega C}{R^2 j\omega C (Rj\omega C + 1) + Rj\omega C + 1 + R^2 j\omega C}$$
$$= \frac{R^2 j\omega C}{-R^3 \omega^2 C^2 + 2R^2 j\omega C + Rj\omega C + 1}$$

Sugnar redan abragit poäng
för delta i 5a) $\Rightarrow \textcircled{S}$