

1a) Assume C to be discharged at $t \leq 0$.

- $U_C = 1 - R I_C = 1 - RC \frac{dU_C}{dt}$

$$\rightarrow -\frac{1}{RC} dt = \frac{1}{U_C - 1} dU_C$$

$$-\frac{1}{RC} \int dt = \int \frac{1}{U_C - 1} dU_C$$

$$-\frac{t}{RC} = \ln(U_C - 1) + \alpha_0$$

$$e^{-t/RC} = e^{\alpha_0} (U_C - 1)$$

$$U_C = 1 + \alpha_1 e^{-t/RC}$$

Initial cond. $U_C(0) = 0 \rightarrow \alpha_1 = -1$

Answer: $U_C(t) = \begin{cases} 0, & t \leq 0 \\ 1 - e^{-t/RC}, & t > 0 \end{cases} \text{ [Volt]}$

1b) Answer: $-10 \leq U_{out}(t) \leq 10 \text{ [Volt]}$

1c) $\bullet 1 - U_{in}^+ = RC \frac{dU_{in}^+}{dt}$

$\bullet \bar{U}_{in} = RC \frac{d(U_{out} - \bar{U}_{in})}{dt}$

$\bullet U_{in}^+ = \bar{U}_{in} \text{ (Ideal OpAmp + Neg. Feedback)}$

$$\rightarrow 1 - RC \frac{d(U_{out} - \bar{U}_{in})}{dt} = RC \frac{dU_{in}^+}{dt}$$



$$\rightarrow U_{out} = \frac{1}{RC} \int 1 dt$$

$$\text{Answer: } u_{\text{out}}(t) = \begin{cases} 0, & t < 0 \\ t/RC, & 0 \leq t < 10RC \\ 10, & t \geq 10RC \end{cases}$$


[Vole]

1d) Answer; Integration.

2a)

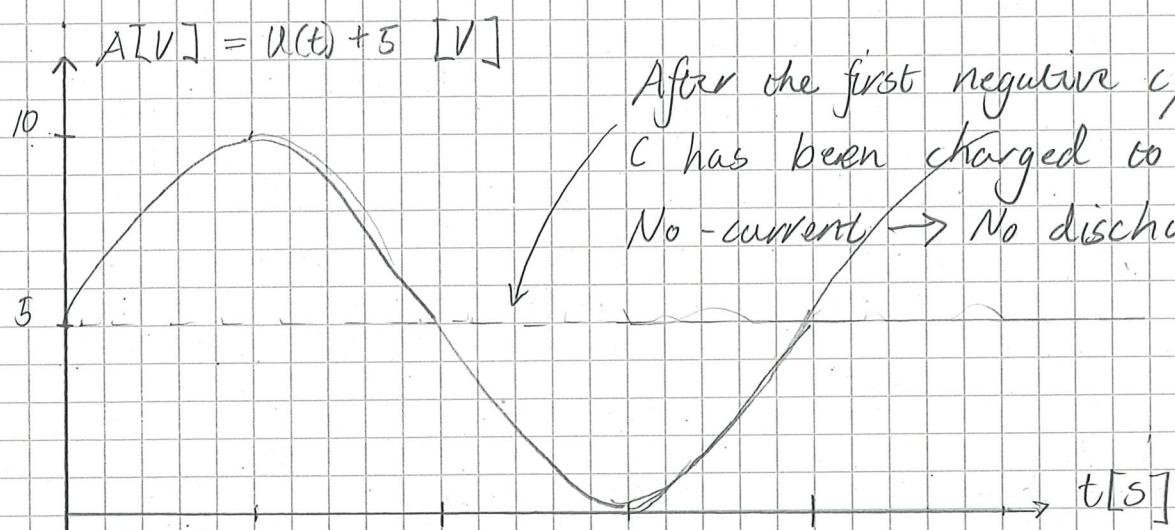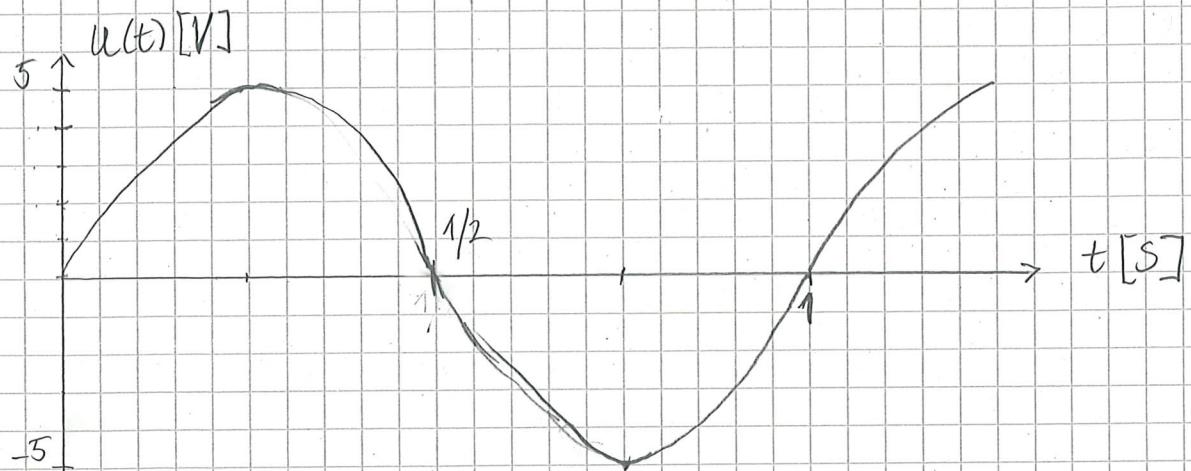


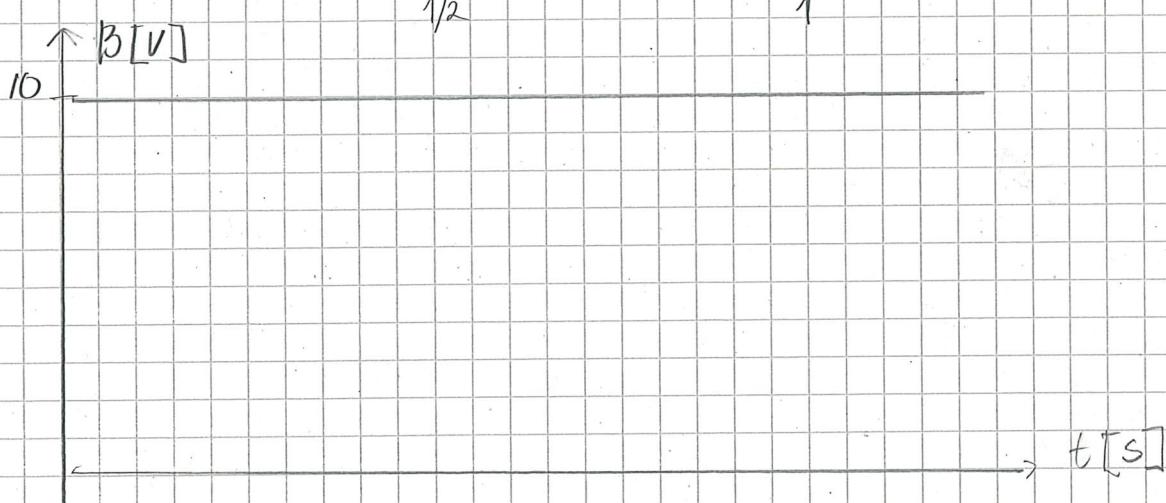After the first negative cycle
C has been charged to 5 V.
No current \rightarrow No discharge.



2b) The circuit rectifies the AC-input and double its peak voltage,

2.b)

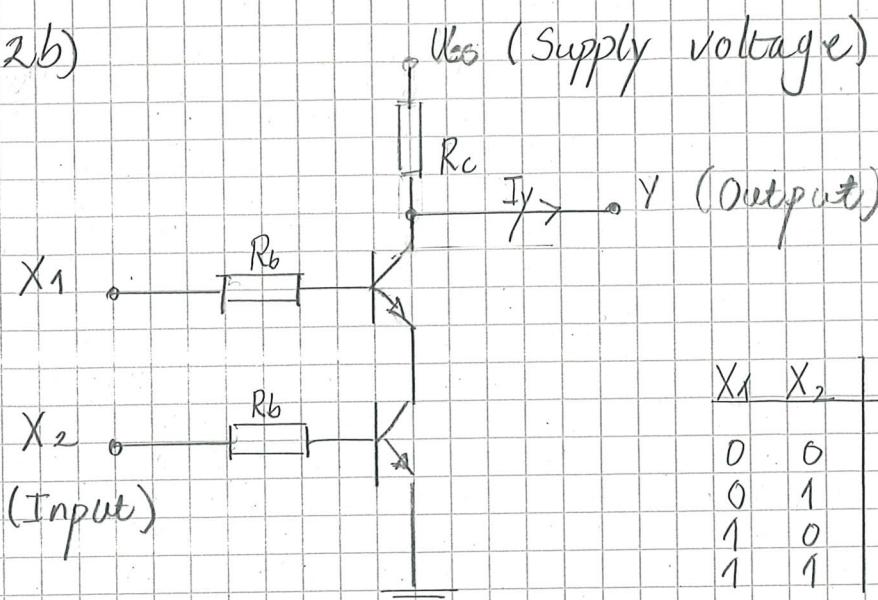


$$U_{high} > 4 \text{ V}$$

$$I_{Cmax} = 10 \text{ mA}$$

$$U_{low} < 1 \text{ V}$$

- Assume X_1 or X_2 is low $\rightarrow I_C \approx 0$
 $\rightarrow Y = U_{ss} - R_C I_Y > U_{high} \quad \& \quad I_Y \leq 1 \text{ mA}$
 $\rightarrow R_C < (5 - 4) / 10^{-3} = 1 \text{ k}\Omega$
 $\rightarrow \text{Select } R_C = 820 \text{ }\Omega. \quad (\text{E12 series of values})$
- Minimum I_C when X_1 & X_2 are high.
 $U_Y = U_{ss} - R_C(I_Y + I_C) \leq U_{ss} + R_C I_C < U_{low}$
 $\rightarrow I_C > (U_{ss} - U_{low}) / R_C \approx 5 \text{ mA}$
- Maximum I_C when X_1 & X_2 are high
 $I_C < U_{ss} / R_C \approx 6 \text{ mA}$
- Minimum bias current $I_B > I_C / h_{FE} = 6 \cdot 10^3 / 100 = 6 \cdot 10^{-5}$
- Maximum $I_B \leq 1 \text{ mA}$
Upper bound: $I_B < (U_{ss} - V_{BE}) / R_B < 1 \text{ mA} \rightarrow R_B > 4,3 \text{ k}\Omega$
Lower bound: $I_B > (U_{low} - V_{BE} - V_{CE}) / R_B > 60 \mu\text{A} \rightarrow R_B < 53 \text{ k}\Omega$
 $\rightarrow \text{Select } R_B = 10 \text{ k}\Omega$

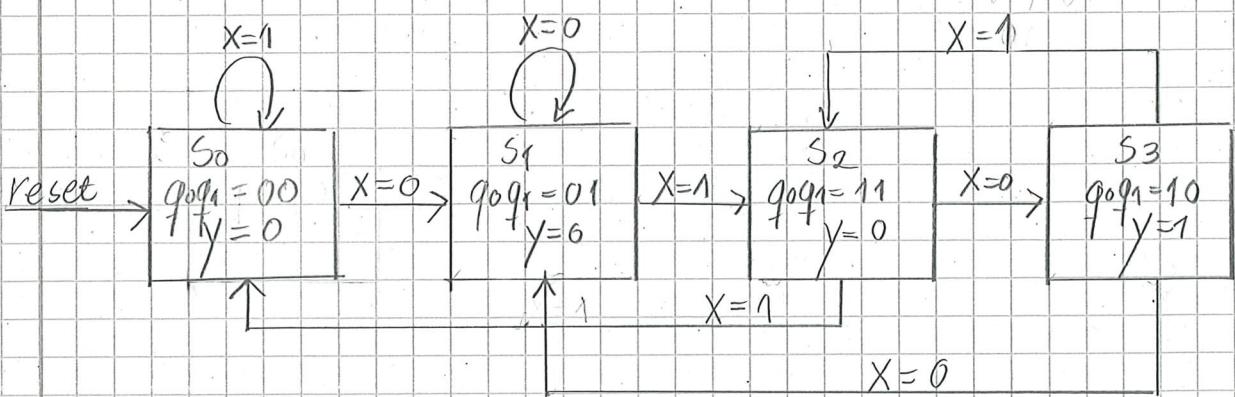3 a) $q_0 q_1$ - state coding, y -output, x -input



Truth tables

X	$q_0 q_1$	$q_0^t q_1^t$
0	00	00
0	01	01
1	11	10
0	10	01
1	00	00
1	01	11
1	11	00
1	10	11

$q_0 q_1$	Y
00	0
01	0
10	1
00	0

K-map q_0^t

X	$q_0 q_1$	00	01	11	10
q_0^t	0	0	0	1	0
q_1^t	1	0	1	0	1

K-map q_1^t


X	$q_0 q_1$	00	01	11	10
q_0^t	0	1	1	0	1
q_1^t	1	0	1	0	1

$$q_0^t = X \bar{q}_0 q_1 + \bar{X} q_0 q_1 + X q_0 \bar{q}_1$$

$$q_1^t = \bar{X} \bar{q}_0 + \bar{q}_0 q_1 + q_0 \bar{q}_1$$

$$Y = q_0 \bar{q}_1$$

3b) NOT-gate from NAND-gate

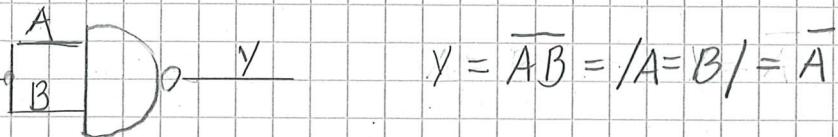


$$Y = \overline{AB} = /A=B/ = \bar{A}$$

AND-gate from NAND-gates



OR-gate from NAND-gates

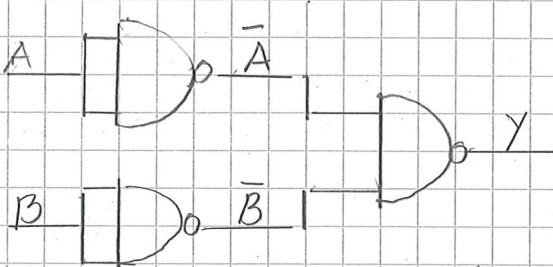

$$\begin{aligned} Y &= \overline{\overline{A}\overline{B}} = /De'Morgons/ \\ &= \overline{\overline{A}+\overline{B}} = A+B \end{aligned}$$

4a) Assume ideal OpAmp.

- Negative feedback $\rightarrow U_{IN} = U_{IIN} = 0$

- $\frac{U_{OUT}}{Z_C // Z_{R1}} = - \frac{U_{IN}}{Z_{R1}} \rightarrow H(j\omega) = - \frac{Z_C // Z_{R2}}{Z_{R1}}$

- $Z_C = 1/j\omega C_1, Z_{R1} = R_1, Z_{R2} = R_2$

$$\Rightarrow H(j\omega) = - \frac{\frac{Z_C + Z_{R1}}{Z_C + Z_{R1}}}{\frac{Z_{R2}}{Z_C + Z_{R1}}} = - \frac{1}{R_1} \cdot \frac{\frac{R_2/j\omega C_1}{1/j\omega C_1 + R_2}}{=}$$

$$= - \frac{R_2}{R_1} \cdot \frac{1}{1 + j\omega R_2 C_1}$$

4b)

- $\lim_{\omega \rightarrow 0} |H(j\omega)| = R_2/R_1$

- $\lim_{\omega \rightarrow \infty} |H(j\omega)| = 0$

- Filter has one pole (one cut-off freq)

$\Rightarrow LP\text{-filter}$

4c) With component values $H(j\omega)$ becomes

$$H(j\omega) = - \frac{-10}{1 + j0.1\omega}$$


- $|H(j\omega)|_{\omega=10} = 10/\sqrt{2}$

- $\angle H(j\omega)|_{\omega=10} = \pi - \angle(1+j) = \pi - \pi/4 = 3\pi/4$

- $SIN-IN \rightarrow SIN OUT$

$$\Rightarrow u_{out}(t) = \frac{10}{\sqrt{2}} \cos(10t + \frac{3\pi}{4}) [Volt]$$

5a)

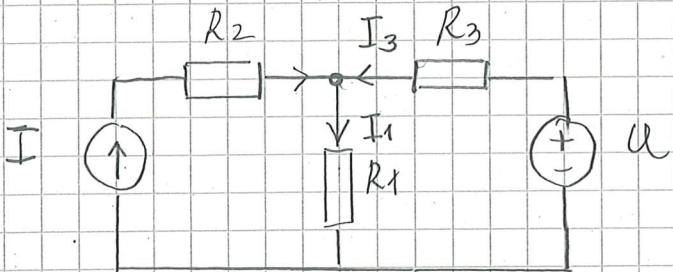

$$I_x = I + I_3$$

$$U_{R1} = R_1 I_1 = u - R_3 I_3$$


$$\rightarrow R_1 I_1 = u - R_3 (I_1 - I)$$

$$(R_1 + R_3) I_1 = u + R_3 I$$

$$I_1 = (u + R_3 I) / (R_1 + R_3)$$

$$\rightarrow u R_1 = R_1 I_1 = \frac{R_1}{R_1 + R_3} u + \frac{R_1 R_3}{R_1 + R_3} \cdot I \quad [\text{Volt}]$$

5b)

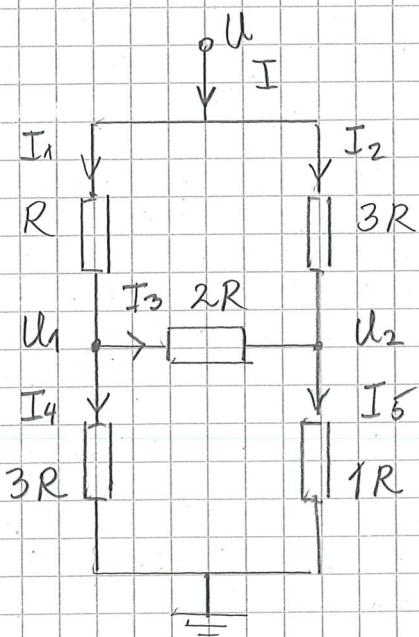

$$I = I_1 + I_2 = I_4 + I_5$$

$$I_1 = I_3 + I_4$$

$$I_5 = I_3 + I_2$$

$$R_{\text{eq}} = u / I \rightarrow \text{Find } I$$

$$u = R I_1 + 3R I_4$$

$$u = 3R I_2 + R I_5$$

$$u = R I_1 + 2R I_3 + R I_5$$

$$U = R I_1 + 3R (I_1 - I_3) = 4R I_1 - 3R I_3 \quad (\text{a})$$

$$U = 3R I_2 + R (I_2 + I_3) = 4R I_2 + R I_3 \quad (\text{b})$$

$$U = R I_1 + 2R I_3 + R (I_2 + I_3) = R I_1 + R I_2 + 3R I_3 \quad (*)$$

$$(*) \rightarrow U = R(I_1 + I_2) + 3R I_3 \rightarrow I_3 = \frac{U - RI}{3R} = I$$

Insert (*) into (a) yields:

$$\rightarrow U = 4R I_1 - 3R I_3 = 4R I_1 - 3R(U - RI)$$

$$\rightarrow 2U = 4R I_1 + RI \rightarrow I_1 = 2U - RI = \frac{U}{2R} - \frac{I}{4}$$

Insert (*) into (b) yields:

$$\rightarrow U = 4R I_2 + R(U - RI) = 4R I_2 + \frac{U}{3} - \frac{RI}{3}$$

$$\rightarrow I_2 = \left(\frac{RI}{3} + \frac{2U}{3} \right) / 4R = \frac{I}{12} + \frac{U}{6R}$$

This yields the equiv. resistance

$$I = I_1 + I_2 = \frac{U}{2R} - \frac{I}{4} + \frac{I}{12} + \frac{U}{6R}$$

$$\frac{7I}{6} = \frac{2U}{3R}$$

$$R_{\text{equiv}} = \frac{U}{I} = \frac{3 \cdot 7R}{6 \cdot 2} = \frac{21R}{12} = \underline{\underline{\frac{7R}{4}}}$$