

Exercise sessions 7 and 8 - AC circuits and filters
1TE717 Digital Technologies and Electronics

Question 1

This question is a short recap and practice of complex numbers.

(a) Rewrite the following complex numbers in polar coordinates.

(1) $z = 10 + j5$.

(2) $z = j3$.

(3) $z = -j5$.

(4) $z = -5 + j2.5$.

(b) Compute the following operations with complex numbers.

(1) $z_1 = 10 + j5$, $z_2 = -4 + j8$. $z = z_1 + z_2$.

(2) $z_1 = 10 + j5$, $z_2 = -4 + j8$. $z = z_1 z_2$.

(3) $z_1 = 10 + j5$, $z_2 = -4 + j8$, $z_3 = 2 - j4$. $z = z_1 z_2 z_3$.

(4) $z_1 = 10 + j5$, $z_2 = -4 + j8$, $z_3 = 2 - j4$. $z = z_1 / (z_2 + z_3)$.

(5) $z = (j4)^2 + j2 - 3$.

(6) $z = \frac{1}{j4} + j5 + 1$.

(c) Compute the magnitude and phase of the following complex numbers.

(1) $z = j3$.

(2) $z = 2 - j6$.

(3) $z = \frac{1+j}{3+j6}$.

(4) $z = \frac{(1-j2)(3-j2)}{(1+j4)(3+j2)}$.

(5) $z = \frac{2+j3+(j4)^2}{1-j3-(j4)^2}$.

Question 2

Determine the time-signal $i(t)$ corresponding to the following complex currents.

Note: Indicate which transformation you have considered to go from complex current to current signals.

(a) $I = 5mA$.

(b) $I = 8e^{j\frac{\pi}{3}}mA$.

(c) $I = j2mA$.

(d) $I = (1 + j)mA$.

Question 3

Determine the complex current corresponding to the current signals:

- (a) $i(t) = 4 \cos(\omega t) \text{ mA}$.
- (b) $i(t) = 2 \cos(\omega t + \frac{\pi}{6}) \text{ mA}$.
- (c) $i(t) = 5 \cos(\omega t - \frac{\pi}{3}) \text{ mA}$.
- (d) $i(t) = 4 \sin(\omega t) \text{ mA}$.

Question 4

A AC voltage source with voltage $v(t) = V_0 \cos(\omega t)$ is connected to a capacitor with capacitance C . Determine $i(t)$ using the $j\omega$ -method and complex voltages.

Question 5


Consider a high-pass filter composed by a capacitor C connected in series with a resistor R . The input voltage $v_{in}(t) = V_0 \cos(\omega t)$ is applied to this series of components, while the output voltage $v_{out}(t)$ is measured as the voltage drop across the resistor. Suppose that R and C are known.

- (a) Determine the expression for the complex voltage V_{out} .
- (b) What is the phase shift (or phase difference) between $v_{out}(t)$ and $v_{in}(t)$?
- (c) Determine the voltage signal $v_{out}(t)$.
- (d) Suppose that $R = 1 \text{ k}\Omega$ and $C = 1 \mu\text{F}$. Determine the frequency f in Hz (or ω in rad/s) for which the peak-amplitude of the output voltage signal is $\frac{1}{\sqrt{2}}$ of peak-amplitude of the input voltage. Determine the phase difference between the output and input voltages at this frequency.


Question 6

For each of the RLC circuits below, derive the transfer function $H(j\omega)$ from the input to the output. Determine what is the gain $|H(j\omega)|$ for frequencies close to $\omega = 0$ and $\omega = \infty$.


a)

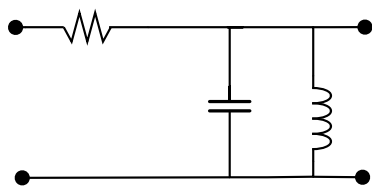


b)

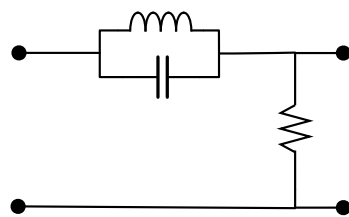


c)

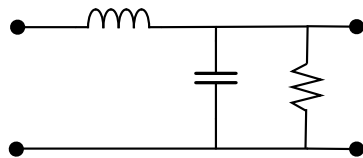


d)

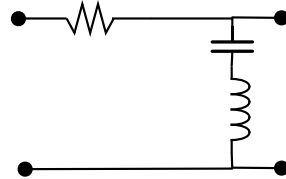

e)

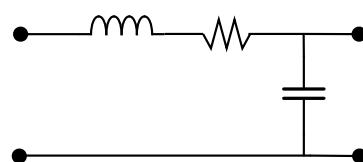

f)

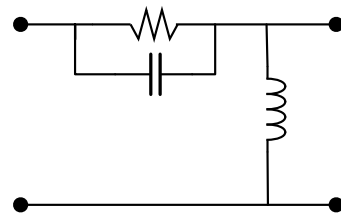

Question 7

For each of the RLC circuits in Question 6, use the respective component values indicated below and compute the amplitude gain $|H(jw)|$ and phase shift $\arg H(jw)$ of the output when a sinusoidal signal with a specific frequency is applied at the input.

Note: match the circuit in Question 6.a) with the parameters in Question 7.a), and so on for the other circuits.

- (a) $R = 1 \text{ k}\Omega$, $C = 1 \text{ }\mu\text{F}$, $L = 1.0134 \text{ mH}$, $f = 5000 \text{ Hz}$.
- (b) $R = 1 \text{ k}\Omega$, $C = 1 \text{ }\mu\text{F}$, $L = 1.0134 \text{ mH}$, $f = 2000 \text{ Hz}$.
- (c) $R = 100 \text{ }\Omega$, $C = 1 \text{ }\mu\text{F}$, $L = 10 \text{ mH}$, $f = 4000 \text{ Hz}$.
- (d) $R = 20 \text{ }\Omega$, $C = 100 \text{ nF}$, $L = 100 \text{ mH}$, $f = 1600 \text{ Hz}$.
- (e) $R = 1000 \text{ }\Omega$, $C = 100 \text{ nF}$, $L = 100 \text{ mH}$, $f = 1000 \text{ Hz}$. (test also with $f = 1590$ and $f = 1580$)
- (f) $R = 1000 \text{ }\Omega$, $C = 1 \text{ }\mu\text{F}$, $L = 1 \text{ mH}$, $f = 2000 \text{ Hz}$.

Question 8

- Derive the transfer functions $H(j\omega)$, i.e. V_o / V_i , of the following circuits. Determine the gain $|H(j\omega)|$ for frequencies close to $\omega = 0$ and $\omega = \infty$.

