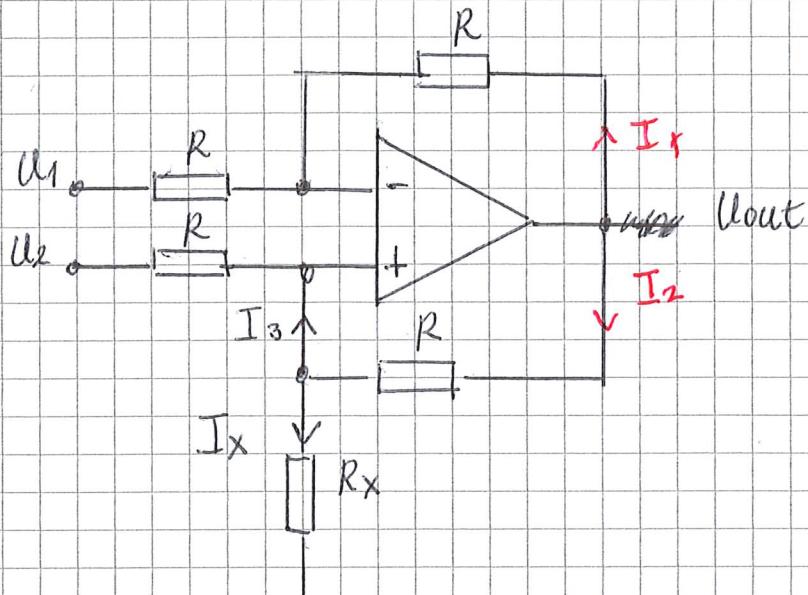


1a)





Negative feedback + Ideal OpAmp $\rightarrow u_1^+ \approx u_1^-$

$$\begin{aligned} u_{1N}^+ &= u_{\text{out}} - R I_1 \\ u_{1N}^- &= u_{\text{out}} - R I_2 \end{aligned} \quad \rightarrow I_1 = I_2 \text{ since } u_{1N}^+ \approx u_{1N}^-$$

$$\begin{aligned} u_1 &= -R I_1 + u_{1N}^- \\ u_2 &= -R I_3 + u_{1N}^+ \end{aligned}$$

$$I_x = I_2 - I_3 = I_1 - I_3$$
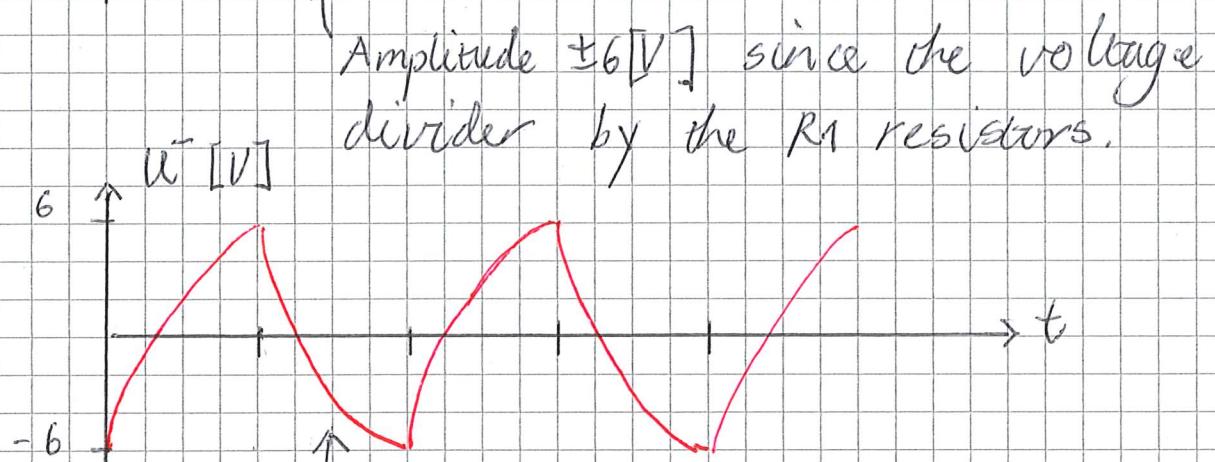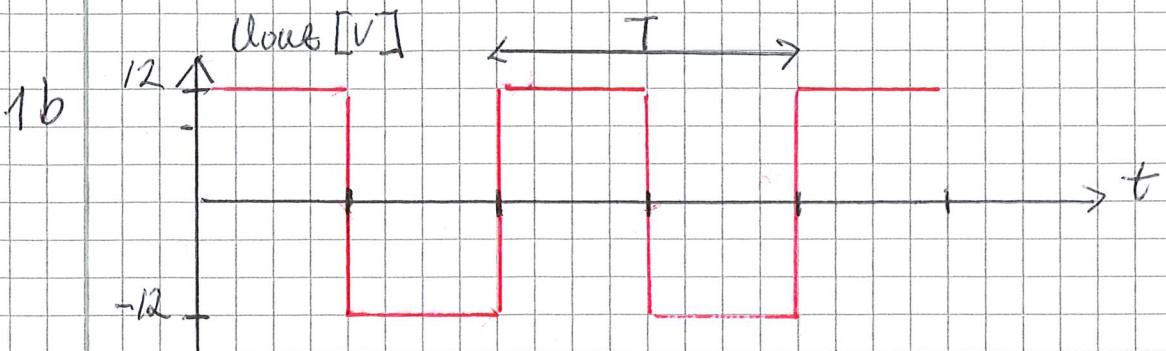
$$I_x = -\frac{u_1 + u_{1N}^-}{R} - \frac{-u_2 + u_{1N}^+}{R} = /u_{1N}^+ = u_{1N}^-/ = \frac{u_2 - u_1}{R} [A]$$



Amplitude $\pm 6[V]$ since the voltage divider by the R_1 resistors.

charge/discharge of RC-circuit.
The comparator (with hysteresis) switch state at $\pm 6[V]$.

RC-circuit: $U_C(t) = U_S - (U_S - U_{init}) e^{-t/RC}$, $t > 0$

\uparrow supply voltage \uparrow initial charge voltage of cap.

Identification

$$U_S = 12[V]$$

$$U_{init} = -6[V]$$



Eq. to solve


$$u_c(\frac{I}{2}) = 12 - (12 - 6) e^{-T/2RC} = 6$$

$$\rightarrow 6 = 18 e^{-T/2RC}$$

$$\rightarrow T/(2RC) = \ln(3)$$

$$\rightarrow T = 2RC \ln(3)$$
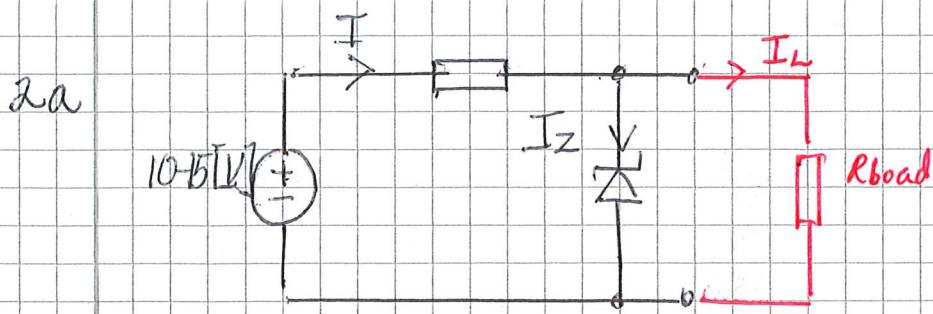
$$\rightarrow T = \underline{RC \ln(9)} \quad [s]$$



$$U_Z = 4,7 \text{ [V]}$$

$I_{Z\min} = 10 \text{ [mA]}$ (Minimum backward bias current for zener diode to work)

$$P_Z = U_Z \cdot I_Z < 0,5 \text{ [W]}$$

$$I_L = 10 - I_{\max} \text{ [mA]}$$

* Maximum current through diode

$$P_Z = U_Z \cdot I_Z < 0,5 \rightarrow I_{Z\max} \leq P_Z/U_Z = 0,5/4,7 \approx 106 \text{ [mA]}$$

* Minimum allowable resistance

- I_Z is max if $I_L = 10 \text{ [mA]}$

$$I = I_{Z\max} + I_L$$

$$I = \frac{U_s - U_Z}{R} \leq \frac{15 - 4,7}{R}$$

$$\rightarrow R \geq \frac{15 - 4,7}{I_{Z\max} + I_L} \geq \frac{15 - 4,7}{0,106 + 0,01} \approx 113 \text{ [Ohm}] \quad 88,8 \text{ Ohm}$$

* Maximum allowable load


$$U_Z = U_s - RI = U_s - R(I_Z + I_{load}) \quad (\text{Most hold for voltage reg.})$$

$$\rightarrow I_{load} = \frac{U_s - U_Z}{R} - I_Z$$

$$\rightarrow I_{Z\min} = 10 \text{ mA} \quad \& \quad U_{s\min} = 10 \text{ [V]}$$

$$\rightarrow I_{\max} < \frac{10 - 4,7}{88,8 \text{ Ohm}} = 10^{-2} \approx 45 \text{ [mA]} \quad 50 \text{ [mA]}$$

2b

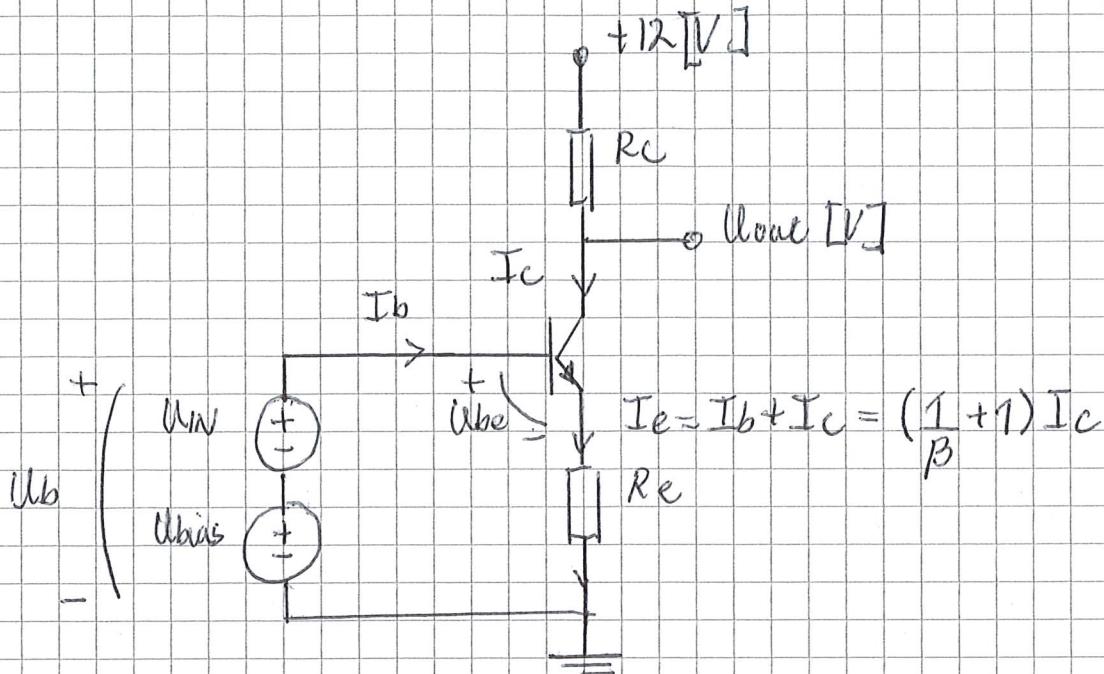

$$U_{out} = 12 - R_C \cdot I_C$$

$$I_B = (U_b - U_{be}) / R_E$$

$$I_C = \beta I_B$$

$$I_E = \left(\frac{1}{\beta} + 1 \right) I_C$$

$$\rightarrow U_{out} = 12 - R_C \cdot \left(U_b - U_{be} \right) = 12 - \frac{R_C}{R_E} \left(U_N + U_{bias} - U_{be} \right)$$

$$\frac{R_C}{R_E} \left(\frac{1}{\beta} + 1 \right) \quad \frac{R_C}{R_E} \left(1 + \frac{1}{\beta} \right)$$

- $U_{be} = 0.6 \text{ V}$, $\beta > 1$, $U_N = 0.1 \sin(t) \text{ V}$

- We want $U_{out} = 6 - 5 \sin(t)$

- 2 unknowns: R_C/R_E & U_{bias} \rightarrow 2 eqv. needed

$$t=0 \rightarrow U_N(t)=0 \rightarrow U_{out} = 12 - \frac{R_C}{R_E} (+U_{bias} - 0.6) = 6$$

$$t=\pi/2 \rightarrow U_N(t)=0.1 \rightarrow U_{out} = 12 - \frac{R_C}{R_E} (0.1 + U_{bias} - 0.6) = 1$$

$$\rightarrow R_C/R_E = 50 \text{ [-]} , U_{bias} = 0.19 \text{ V}$$

0.72 [V]

3a)

Truth table

Digit	X_0	X_1	X_2	D_1	D_2	D_3	D_4	D_5	D_6	D_7
1	0	0	0	0	0	0	1	0	0	0
2	0	1	0	1	0	0	0	0	0	1
3	1	1	0	1	0	0	1	0	0	1
4	0	0	1	1	0	1	0	1	0	1
5	1	0	1	1	0	1	1	1	0	1
6	0	1	1	1	1	1	0	1	1	1
7	1	1	1	-	-	-	-	-	-	-
0	0	0	0	-	-	-	-	-	-	-
7	1	1	1	-	-	-	-	-	-	-

) Doesn't
matterK-map
Truth table $D_1 \& D_7$

X_0	X_1	X_2	D_1	D_7
0	0	0	1	1
0	1	1	1	1
1	0	1	-	-
1	1	0	-	-

$$D_7 = D_1 = \bar{X}_0 + X_1 + X_2$$

Red circle is
wrong. x_0 not
need

K-map
Truth table $D_2 \& D_6$

X_0	X_1	X_2	D_2	D_6
0	0	0	0	0
0	1	1	1	0
1	0	0	0	0
1	1	0	-	-

$$D_6 = D_2 = X_1 X_2$$

K-map
Truth table $D_3 \& D_5$

X_0	X_1	X_2	D_3	D_5
0	0	0	1	0
0	1	1	1	0
1	0	1	-	-
1	1	0	-	-

$$D_3 = D_5 = X_2$$


K-map
Truth table D₄

X ₀	X ₁	X ₂	0	0	1	1	1	0
0	-	0	0	0	0	0	0	0
1	1	1	-	1	1	-	1	0

$$D_4 = X_0$$

3b)

jump on clock pulse

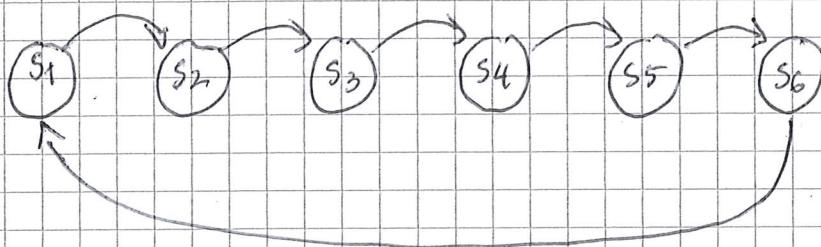

6 states \rightarrow 3 flip-flops (memory states)

State coding			state ⁺ coding ⁺				
s _i	X ₀	X ₁	X ₂	s _i	X ₀ ⁺	X ₁ ⁺	X ₂ ⁺
1	1	0	0	2	0	1	0
2	0	1	0	3	1	1	0
3	1	1	0	4	0	0	1
4	0	0	1	5	1	0	1
5	1	0	1	6	0	1	1
6	0	1	1	1	1	0	0

K-map X₀⁺

X ₀	X ₁	X ₂	0	0	1	1	1	0
0	-	0	1	1	1	1	1	0
1	0	0	-	0	0	0	0	0

$$X_0^+ = \overline{X}_0$$

K-map X_1^+

	X_1	X_2			
X_0	0 0	0 1	1 1	1 0	
0	1	0	0	1	
1	1	1	-	0	


$$X_1^+ = \bar{X}_0 \bar{X}_2 + X_0 \bar{X}_1$$


K-map X_2^+

	X_1	X_2			
X_0	0 0	0 1	1 1	1 0	
0	-	1	0	0	
1	0	1	-	1	


$$X_2^+ = \bar{X}_1 X_2 + X_0 X_1$$

See next page

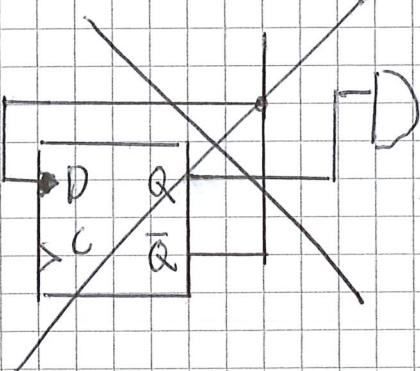

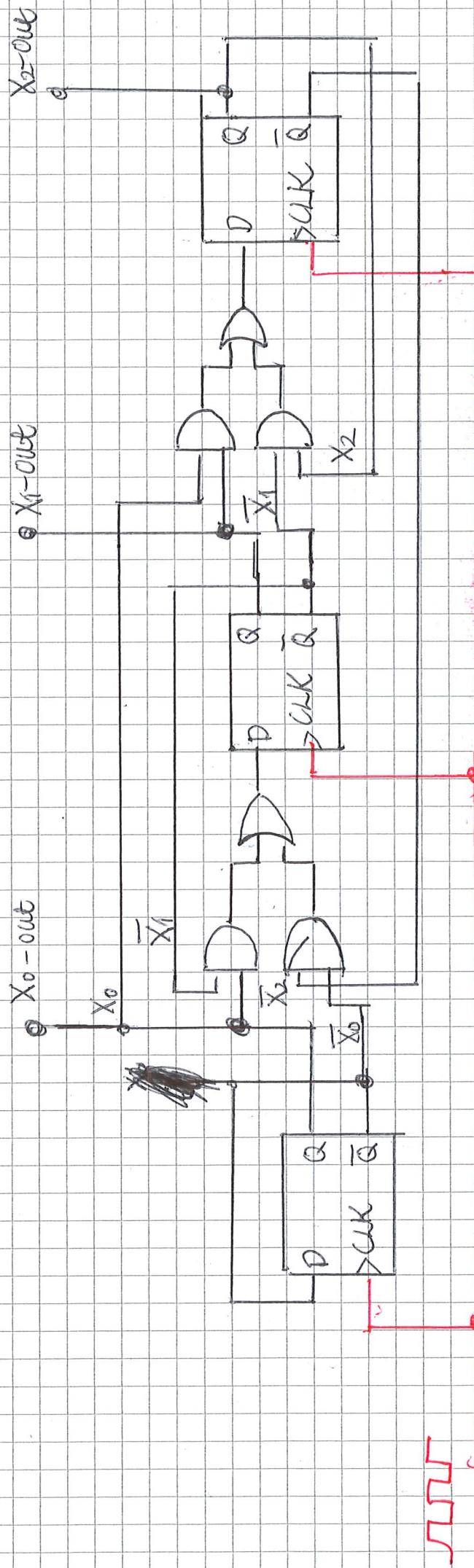

4a

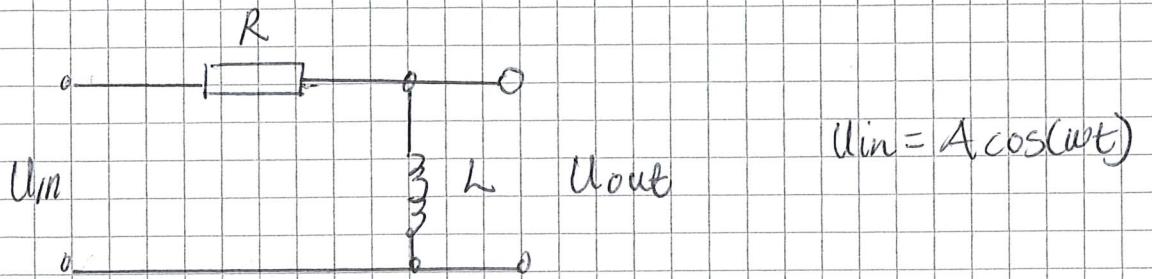

$$H(j\omega) = \frac{U_{out}^c}{U_{in}^c} = \frac{\frac{Z_L}{Z_L + Z_R} \cdot U_{in}^c}{U_{in}^c} = \frac{Z_L}{Z_L + Z_R} =$$

$$= \frac{j\omega L}{j\omega L + R} = |H(j\omega)| e^{j\angle H(j\omega)}$$

$$|H(j\omega)|^2 = H(j\omega) \cdot H(j\omega)^* = \frac{j\omega L}{j\omega L + R} \cdot \frac{-j\omega L}{-j\omega L + R} = \frac{\omega^2 L^2}{\omega^2 L^2 + R^2}$$


$$\angle H(j\omega) = \angle j\omega L - \angle j\omega L + R = \frac{\pi}{2} - \arctan(\omega L / R)$$

$$\rightarrow H(j\omega) = \frac{\omega L}{\sqrt{\omega^2 L^2 + R^2}} \cdot e^{j(\frac{\pi}{2} - \arctan(\omega L / R))}$$

4b

$$|H(0)| = 0$$

$$\lim_{\omega \rightarrow \infty} |H(\omega)| = 1$$

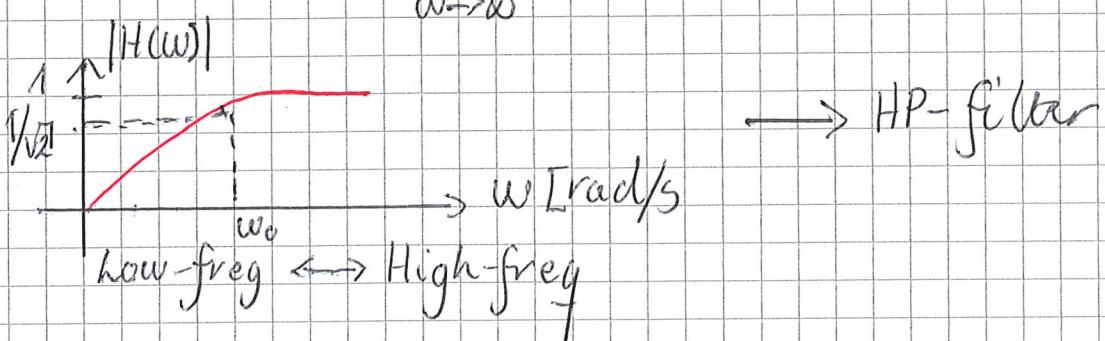

4c

$$|H(\omega_0)| = \frac{1}{\sqrt{2}} \lim_{\omega \rightarrow \infty} |H(\omega)| \rightarrow \frac{\omega_0^2 L^2}{\omega_0^2 L^2 + R^2} = \frac{1}{2}$$

$$\rightarrow 2\omega_0^2 L^2 = \omega_0^2 L^2 + R^2 \rightarrow \omega_0^2 = R^2 / L^2$$

$$\rightarrow \omega_0 = R/L \text{ [rad/s]}$$

LTI-system (passive RLC components)

4d)

sin-in \rightarrow sin-out


$aX_1 + bX_2 \rightarrow aY_1 + bY_2$ (linear sys)

$$\rightarrow U_{\text{out}}(t) = |H(j\omega_0)| \cdot A \cos(\omega_0 t + \angle H(j\omega_0))$$

$$+ |H(j\omega_0)| \cdot B \sin(\omega_0 t + \angle H(j\omega_0)) =$$

$$= \frac{A}{\sqrt{2}} \cos\left(\omega_0 t + \frac{3\pi}{4}\right) + \frac{B}{\sqrt{2}} \sin\left(\omega_0 t + \frac{3\pi}{4}\right) [V]$$

5a)

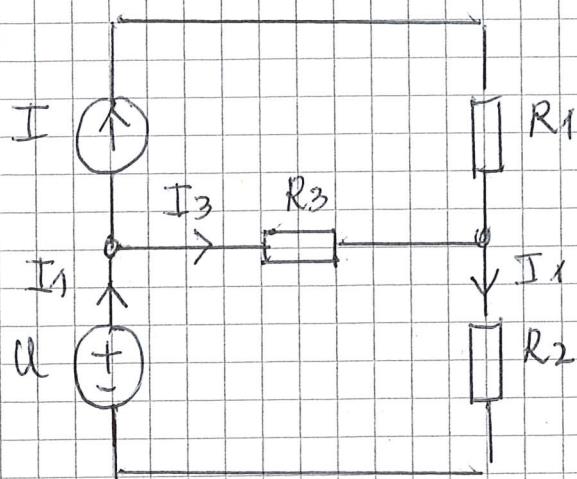

$$I_1 = I + I_3 \quad (\text{KCL})$$

$$U - R_3 I_3 - I_1 R_2 = 0 \quad (\text{KVH})$$

$$\rightarrow U - R_3 I_3 - (I + I_3) R_2 = 0$$


$$\rightarrow I_3 (R_2 - R_3) = -U + IR_2$$

$$\rightarrow I_3 = \frac{U - IR_2}{R_3 + R_2} \quad [\text{A}]$$

$$R_{\text{eqv}} = U / I_1 =$$

$$= \frac{U(R_2 + R_3)}{U + I(R_3)}$$

5b)

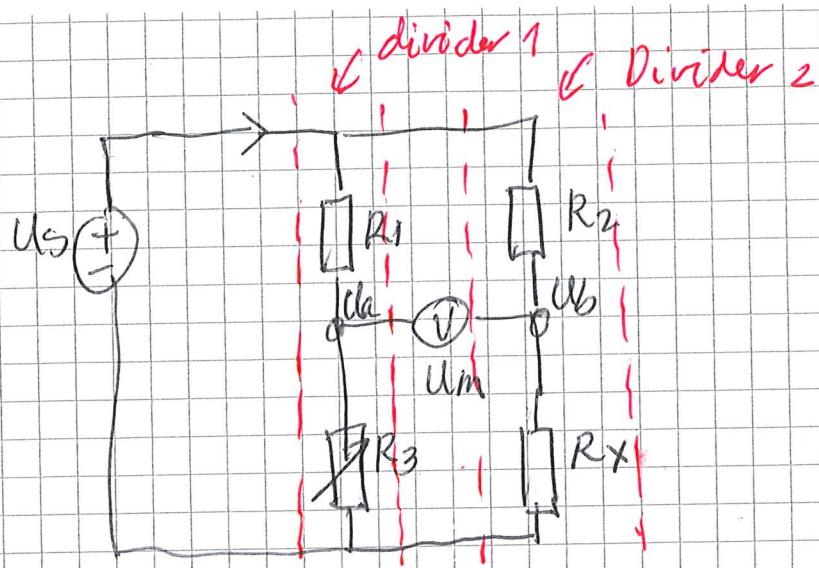

If $U_m = 0 \text{ [V]}$ then $I_m = 0 \text{ [A]}$. \rightarrow

The 2 voltage dividers can be treated separately.

$$U_a = \frac{R_3}{R_1 + R_3} \cdot U_s$$

$$U_b = \frac{R_x}{R_x + R_2} \cdot U_s$$

$$U_a = U_b \rightarrow \frac{R_3}{R_1 + R_3} = \frac{R_x}{R_x + R_2}$$

$$\rightarrow \frac{1}{1 + \frac{R_1}{R_3}} = \frac{1}{1 + \frac{R_2}{R_x}}$$

$$\rightarrow \frac{R_1}{R_3} = \frac{R_2}{R_x}$$

$$\rightarrow R_x = \frac{R_2 \cdot R_3}{R_1} \text{ [V]} \quad \text{Please}$$