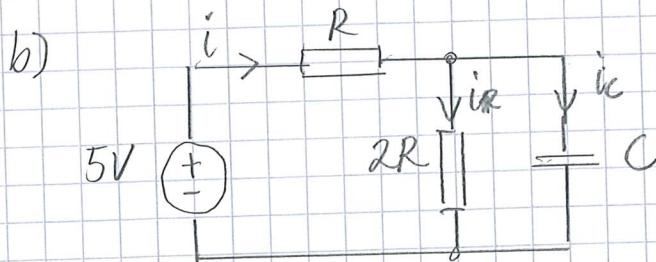


$$1 \text{ a) } U_a = \frac{R}{R+R} \cdot U_N = \underline{\underline{5/2 = 2,5[V]}}$$



$$i_C = C \cdot \frac{dU_c}{dt}$$

$$\begin{aligned} U_c &= 5 - R \cdot i = 5 - R(i_R + i_C) = \\ &= 5 - R \cdot \frac{U_c}{2R} - RC \frac{dU_c}{dt} \end{aligned}$$

$$\frac{3U_c}{2} = 5 - RC \frac{dU_c}{dt}$$

$$RC \frac{dU_c}{dt} = 5 - \frac{3U_c}{2}$$

$$\frac{1}{\frac{5-3U_c}{2}} dU_c = \frac{1}{RC} dt$$

$$\frac{\frac{2}{3}}{\frac{10}{3} - U_c} dU_c = \frac{1}{RC} dt$$

$$-\frac{2}{3} \int \frac{1}{U_c - \frac{10}{3}} dU_c = \frac{1}{RC} \int dt + \beta$$

$$-\frac{2}{3} \ln(U_c - \frac{10}{3}) = t/RC + \beta$$

$$\ln(U_c - \frac{10}{3}) = -3t/2RC + \beta'$$

$$U_c - \frac{10}{3} = e^{-3t/2RC} \cdot \beta''$$

$$* \quad t = 0 \rightarrow U_c = 0 \rightarrow \beta'' = -10/3$$

$$U_c = \frac{10}{3} (1 - e^{-3t/2RC})$$

Next, solve for C given  $t=10$  &  $U_C = 5/2$ .

$$\frac{5}{2} = \frac{10}{3} (1 - e^{-30/2RC})$$

$$\frac{3}{4} = 1 - e^{-30/2RC}$$

$$e^{-30/2RC} = 1/4$$

$$-\frac{30}{2RC} = -\ln(4)$$

$$C = \frac{175}{R \cdot \ln(4)} [F]$$

c)  $R_{led} = \frac{5-1.2}{10-21} = 380 [\Omega]$

- 2a) From the datasheets it is given that
- $U_Z \approx 5,1 \text{ [V]}$  at  $50 \text{ [mA]}$  (Zener-diode)
- $U_{fD} \approx 0,85 \text{ [V]}$  at  $50 \text{ [mA]}$  (Diode)

$$\rightarrow U_a \approx 5,95 \text{ [V]}$$

- b) Assuming that  $U_{BE} \approx 0,7 \text{ [V]}$ , then


$$I \approx \frac{U_a - U_{BE}}{25} \approx \frac{5}{25} = \frac{1}{5} \text{ [A]}$$

- c) From the datasheet it is given at collector current of approx.  $1/5 \text{ [A]}$  then  $h_{FE} \approx 50$ .

$$\rightarrow I_B = \frac{1}{1+h_{FE}} \cdot I_E \approx \frac{1}{50 \cdot 5} = \frac{1}{250} \text{ [A]} = 4 \text{ [mA]}$$

- d) The dissipated power is  $P = UI \approx (U_a - U_{BR}) \cdot I =$   
 $\approx 5 \cdot \frac{1}{5} = 1 \text{ [W]}$ .

### 3a) State-diagram

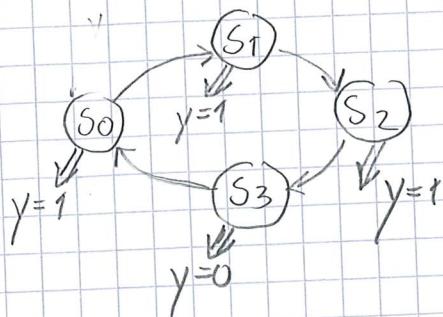

$y = \text{output}$


4 states  $\rightarrow$  2 flip-flops.

Old state	$q_0$	$q_1$	New state	$q_0^+$	$q_1^+$
$S_0$	0	0	$S_1$	0	1
$S_1$	0	1	$S_2$	1	0
$S_2$	1	0	$S_3$	1	1
$S_3$	1	1	$S_0$	0	0


$$\rightarrow q_0^+ = \bar{q}_0 q_1 + q_0 \bar{q}_1 \quad (\text{XOR})$$

$$\rightarrow q_1^+ = \bar{q}_1 \quad (\text{Inverter})$$
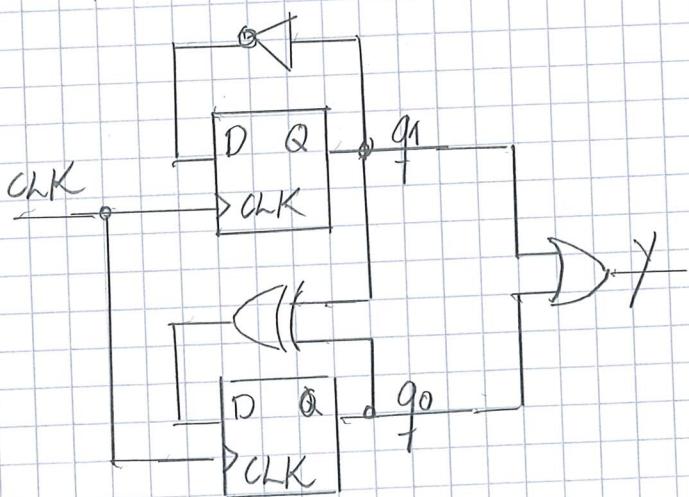
$$\rightarrow y = q_0 + q_1 \quad (\text{OR})$$



3b) One possible circuit is

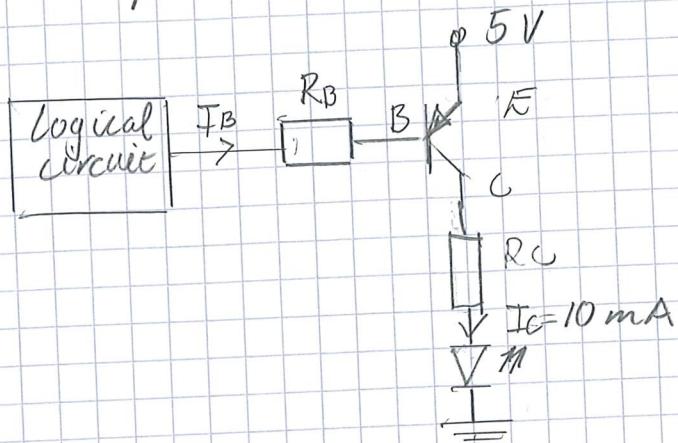

Assume:  $U_{EC} = 0,2 \text{ [V]}$  at saturation

$$h_{FE} = 100$$


$$\rightarrow R_C = \frac{5 - U_{EC} - 1,2}{I_C} = \frac{3,6}{10^2} = 360 \text{ [\mu V]}$$

$\rightarrow$  For saturation  $I_B > I_C/h_{FE} = 10/100 = 10^{-2} \text{ [A]}$


$$I_B = \frac{5 - U_{EB}}{R_B} \approx \frac{5 - 0,7}{R_B} > 10^{-4}$$


$$R_B < \frac{5 - 0,7}{10^{-4}} \approx 43 \text{ [k\mu V]}$$

3c)

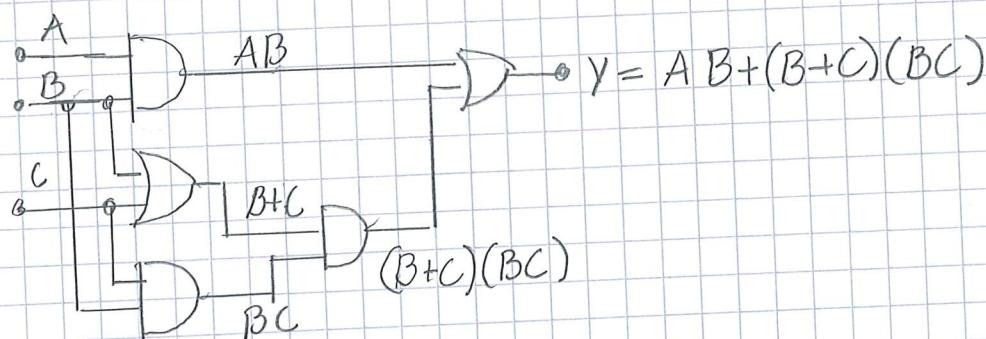
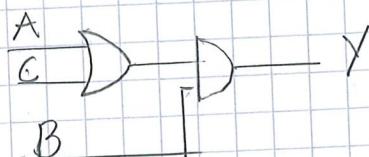
$$Y = AB + BBC + CBC = AB + BC = (A+C)B$$



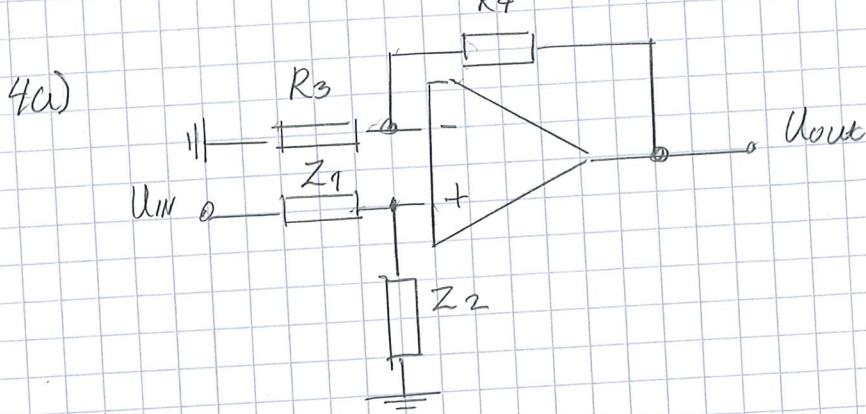

$$\text{Ideal OpAmp} \rightarrow U^- \approx U^+ \rightarrow \frac{Z_2}{Z_1 + Z_2} U_{IN} = \frac{R_3}{R_3 + R_4} U_{out}$$

$$\Rightarrow H(j\omega) = \frac{\frac{Z_2}{R_3}}{\frac{Z_1 + Z_2}{R_3 + R_4}} = \left(1 + \frac{R_4}{R_3}\right) \left(\frac{1}{1 + \frac{Z_1}{Z_2}}\right)$$

Case  $U_{IN}$

$$Z_1 = 1/j\omega C_1, Z_2 = R_1$$

$$H_{U_1, U_2}(j\omega) = \left(1 + \frac{R_4}{R_3}\right) \cdot \frac{1}{1 + \frac{1}{j\omega R_1 C_1}} = \left(1 + \frac{R_4}{R_3}\right) \cdot \frac{j\omega R_1 C_1}{1 + j\omega R_1 C_1}$$

Case  $U_{IN}, U_3$

$$Z_1 = R_2, Z_2 = 1/j\omega C_2$$

$$H_{U_2, U_3}(j\omega) = \left(1 + \frac{R_4}{R_3}\right) \cdot \frac{1}{1 + j\omega R_2 C_2}$$

4b)  $R_1 = 10k\Omega, C_1 = 100\mu F \rightarrow |H_{U_1, U_2}(0)| = 0 \rightarrow \text{HP-filter}$

$$\lim_{\omega \rightarrow \infty} |H_{U_1, U_2}(j\omega)| = 11$$


$$\omega_c = 1/R_1 C_1 = 1/(10^4 \cdot 10^{-4}) = 1 \text{ rad/s}$$

$R_2 = 1k\Omega, C_2 = 100\mu F \rightarrow |H_{U_2, U_3}(0)| = 11 \rightarrow \text{LP-filter}$


$$\lim_{\omega \rightarrow \infty} |H_{U_2, U_3}(j\omega)| = 0$$

$$|\omega_c| = 1/R_2 C_2 = 1/(10^3 \cdot 10^{-4}) = 10 \text{ rad/s}$$

4c) Band-pass filter

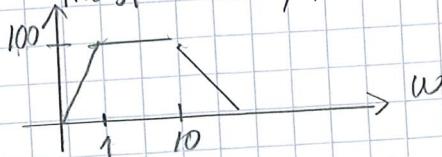

5a)

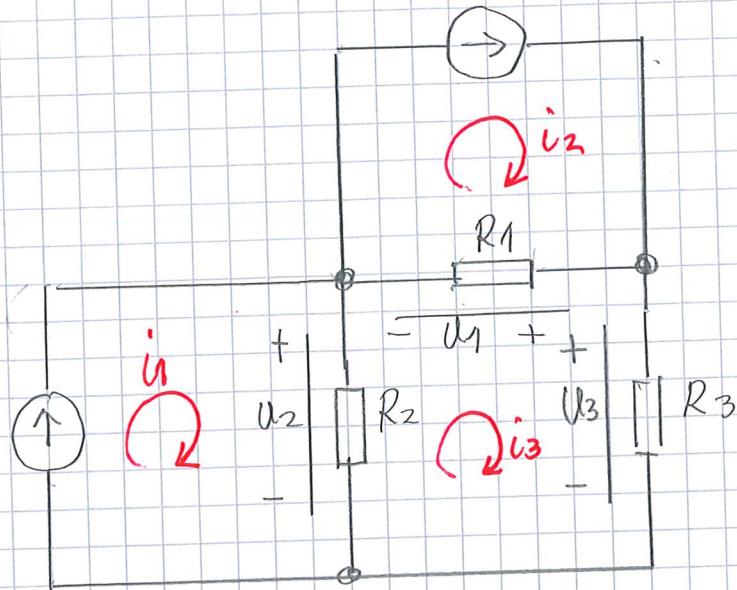

$$U_2 = R_2(i_1 - i_3)$$

$$U_1 = R_1(i_2 - i_3)$$

$$U_1 + U_2 = U_3 = R_3 i_3$$

$$R_3 i_3 = R_2(i_1 - i_3) + R_1(i_2 - i_3)$$


$$(R_1 + R_2 + R_3)i_3 = R_2i_1 + R_1i_2$$

$$i_3 = \frac{R_2 i_1 + R_1 i_2}{R_1 + R_2 + R_3} = \frac{3 \cdot 0,7 + 7 \cdot 1,2}{15} = \frac{10,5}{15} = 0,7 \text{ [A]}$$

$$\rightarrow U_2 = R_2(i_1 - i_3) = 3 \cdot (0,7 - 0,7) = 0 \text{ [V]}$$

$$U_3 = 5 \cdot 0,7 = 3,5 \text{ [V]}$$

5b)

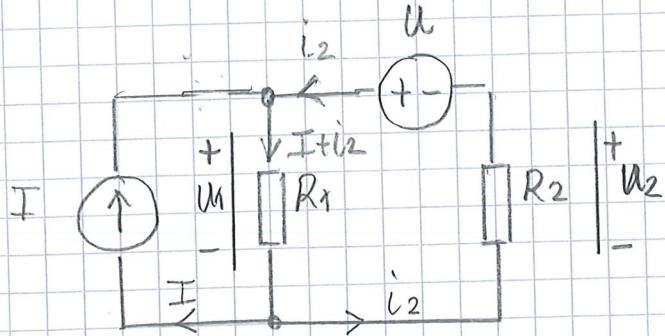

Equivalent resistance:  $R_{eqv} = |U/i_2|$

$$U_1 = R_1(I + i_2)$$

$$U_1 = U + U_2 = U - R_2 i_2$$

$$R_1(I + i_2) = U - R_2 i_2$$

$$(R_1 + R_2)i_2 = U - R_1 I$$

$$i_2 = \frac{U - R_1 I}{R_1 + R_2}$$

$$\rightarrow R_{eqv} = \left| \frac{U}{i_2} \right| = \left| \frac{(R_1 + R_2)U}{U - R_1 I} \right| = \frac{(R_1 + R_2)}{\frac{R_1}{U - I}} \cdot \left| \frac{U}{\frac{U - I}{R_1}} \right| \quad [V]$$