
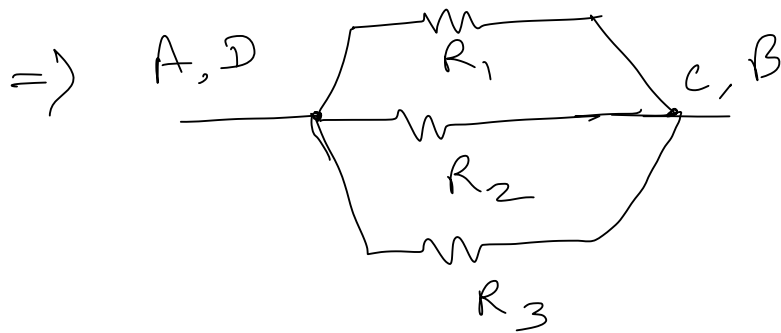


1. a. pts: 2

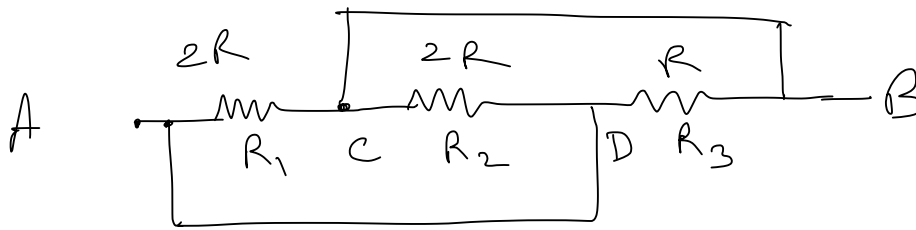


$$\therefore R_{AB} = R_1 \parallel R_2 \parallel R_3$$

$$= (2R \parallel 2R) \parallel R$$

$$= R \parallel R = \boxed{\frac{R}{2} \text{ (Ans)}}$$


1. b. Points 3

For $t < 0$

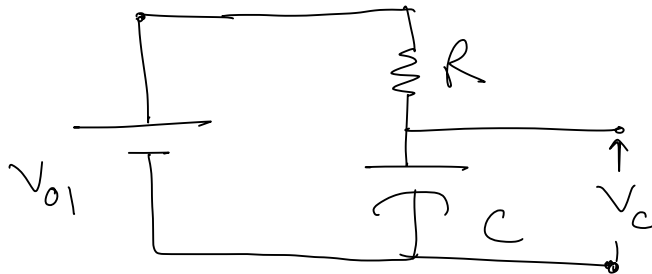


\therefore At $t = 0^+$, $V_c(t) = V_{01}$

For $t \geq 0^+$

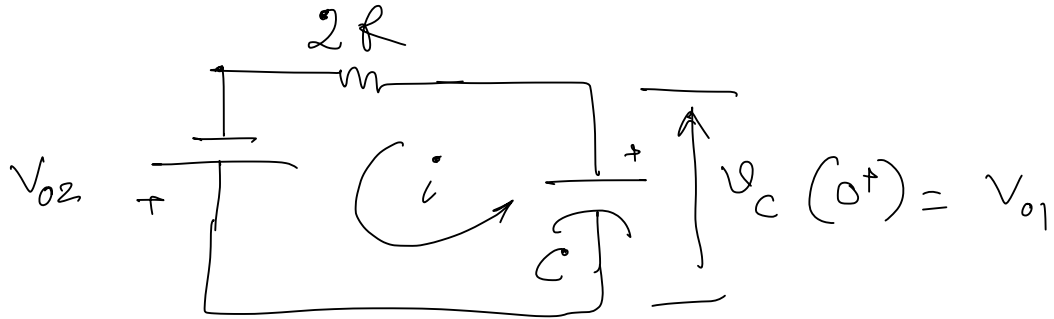


\therefore Initial value of voltage across $C \Rightarrow V_{01}$

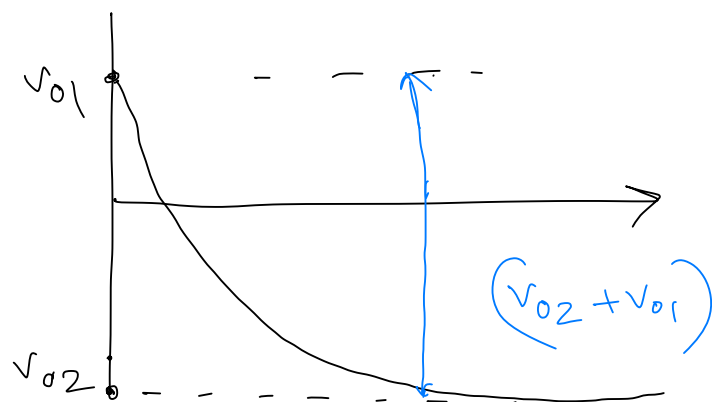final value of the vol across $C \Rightarrow -V_{02}$




$$v_c(t) = (V_{02} - V_{01}) (1 - e^{-t/2Rc}) + V_{01}$$

1. c. points 3

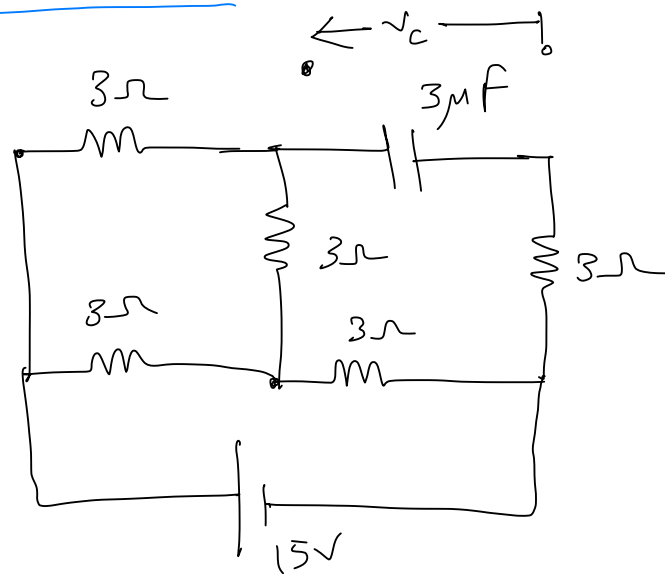

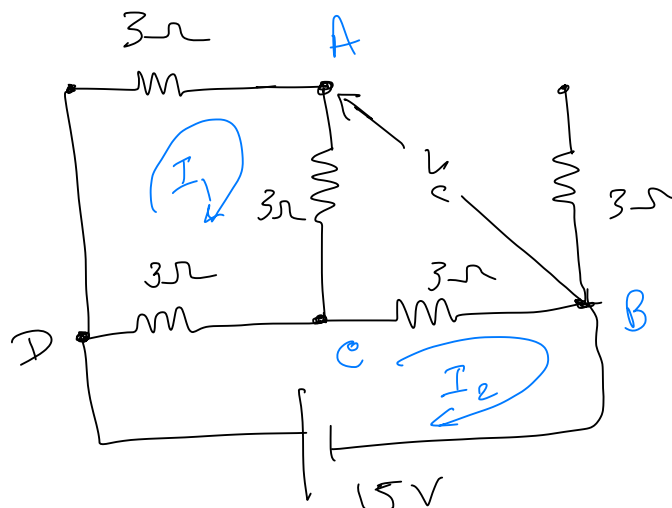At steady state, no current will flow through the capacitor, ∴ the ckt becomes,



$$\underline{\text{Loop-1}} \quad -3I_1 - 3I_1 - 3(I_1 - I_2) = 0$$

$$\Rightarrow -9I_1 + 3I_2 = 0$$

$$\Rightarrow -3I_1 + I_2 = 0 \quad \text{--- (1)}$$

$$\underline{\text{Loop-2}}$$

$$15 - 3I_2 - 3(I_2 - I_1) = 0$$

$$\Rightarrow 15 - 6I_2 + 3I_1 = 0$$

$$\Rightarrow 15 - 6I_2 + I_2 = 0 \quad \left[\text{using (1)} \right]$$

$$\Rightarrow I_2 = 3 \text{ A.}$$


$$I_1 = 1 \text{ A.}$$

$$V_c = V_{AB} = V_{Ac} + V_{cB}$$

$$= 3I_1 + 3I_2$$

$$= 3 + 9 = 12 \text{ V} \quad \text{Ans.}$$

1.d. points 2

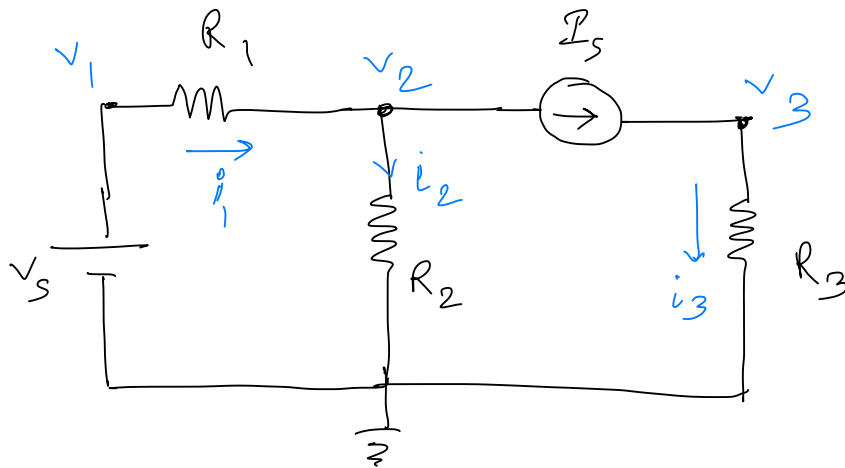

$$v_1 = V_s. \quad \text{Ans.}$$

Node 2

$$i_1 = i_2 + i_3$$

$$\frac{v_1 - v_2}{R_1} = \frac{v_2}{R_2} + I_s \quad (\textcircled{i_3 = I_s})$$


$$\Rightarrow \frac{V_s}{R_1} - \frac{v_2}{R_1} = \frac{v_2}{R_2} + I_s$$

$$\Rightarrow v_2 \left(\frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{V_s}{R_1} - I_s$$

$$\Rightarrow v_2 = \left(\frac{V_s}{R_1} - I_s \right) \frac{R_1 R_2}{R_1 + R_2} \quad \text{Ans.}$$

$$v_3 = I_s R_3 \quad \text{Ans.}$$

2.a. points 7

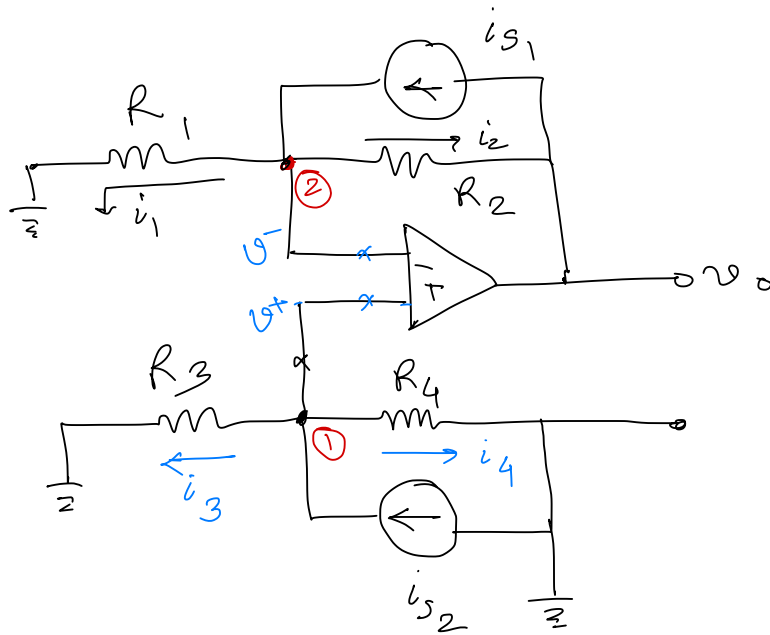

At Node (1)

$$i_{s2} = i_3 + i_4$$

$$\Rightarrow i_{s2} = \frac{v^+}{R_3} + \frac{v^+}{R_4}$$

$$\Rightarrow v^+ = \left(\frac{R_3 R_4}{R_3 + R_4} \right) i_{s2} = v^- \quad \text{--- (1)}$$

At Node (2)

$$i_{s1} = i_1 + i_2$$

$$\Rightarrow i_{s1} = \frac{v^-}{R_1} + \frac{v^- - v_o}{R_2}$$

$$\Rightarrow i_{s1} = v^- \left(\frac{1}{R_1} + \frac{1}{R_2} \right) - \frac{v_o}{R_2}$$

$$\Rightarrow \frac{v_o}{R_2} = \frac{R_1 + R_2}{R_1 R_2} \cdot v^- - i_{s1}$$


$$\Rightarrow v_o = \frac{R_1 + R_2}{R_1} \cdot v^- - i_{s2}$$

$$\Rightarrow v_o = \left(\frac{R_1 + R_2}{R_1} \right) \left(\frac{R_3 R_4}{R_3 + R_4} \right) i_{s2} - R_2 i_{s1}$$

Ans.

E2 ① used.

2.b. points 3

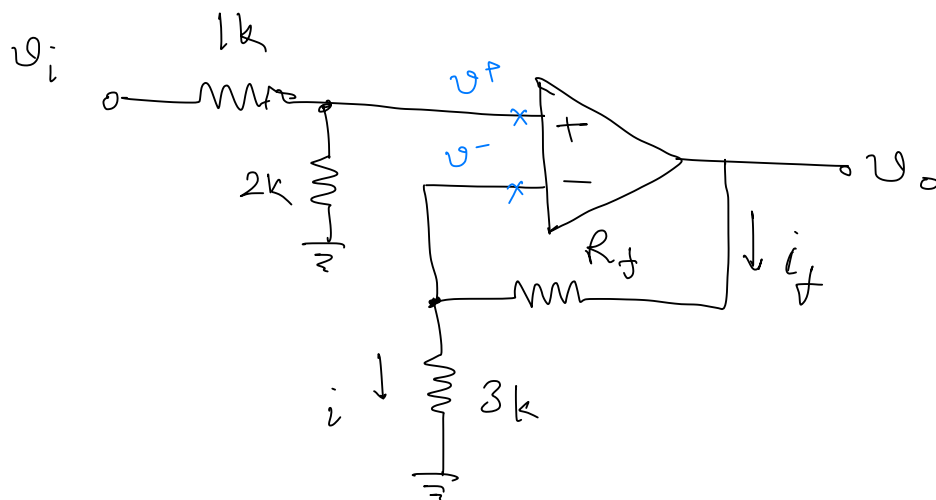

$$v^+ = \frac{2}{2+1} \cdot v_i = \frac{2}{3} v_i = v^- \quad \dots \quad \textcircled{1}$$

$$i_f = i$$

$$\Rightarrow \frac{v_o - v^-}{R_f} = \frac{v^-}{3}$$

$$\Rightarrow \frac{V_o}{R_f} = V^- \left(\frac{1}{R_f} + \frac{1}{3} \right)$$

$$\Rightarrow V_o = V^- \left(1 + \frac{R_f}{3} \right)$$

$$= \frac{2}{3} \cdot V_i \left(1 + \frac{R_f}{3} \right) \leftarrow$$

① used

$$\frac{V_o}{V_i} = 5 \quad (\text{given})$$


$$\therefore \frac{2}{3} \left(1 + \frac{R_f}{3} \right) = 5$$

$$\Rightarrow 1 + \frac{R_f}{3} = \frac{15}{2}$$


$$\Rightarrow R_f = 3 \left(\frac{15}{2} - 1 \right) = \frac{39}{2} = 19.5 \text{ k}\Omega$$

Ans.

3. a point 3

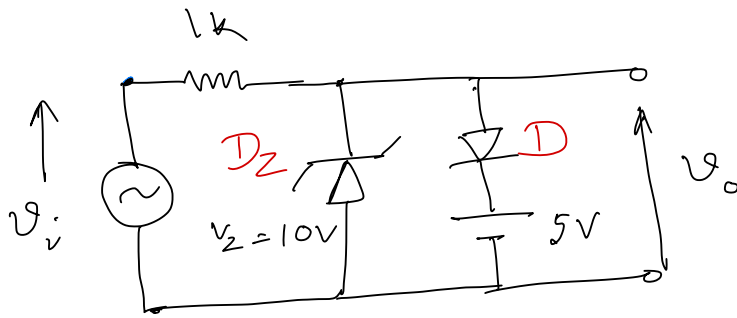
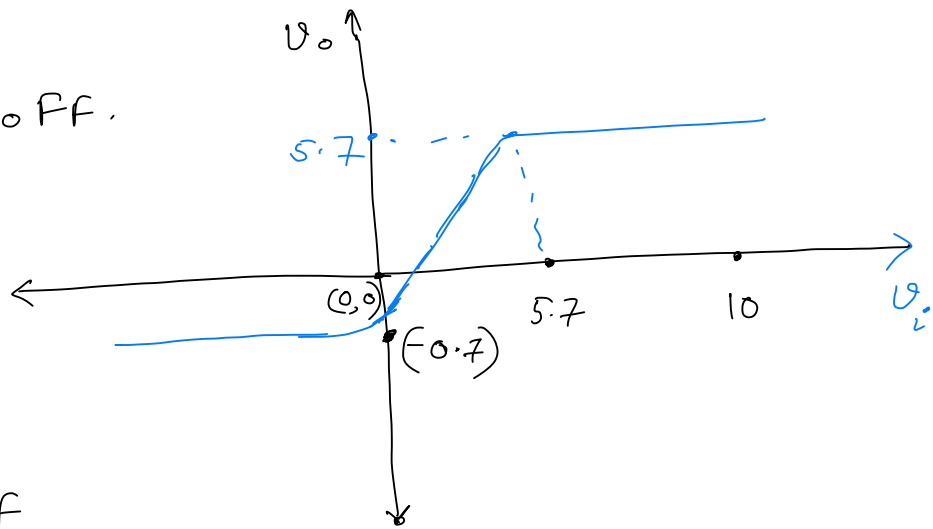
$$\left\{ \begin{array}{l} v_i < 0V \\ D_Z \text{ ON, } D \text{ OFF.} \\ v_o = -0.7V \end{array} \right.$$




$$\left\{ \begin{array}{l} 5.7 > v_i \geq 0 \\ D_Z \text{ OFF, } D \text{ OFF} \\ v_o = v_i \end{array} \right.$$

$$\left\{ \begin{array}{l} 10 > v_i \geq 5.7 \\ D_Z \text{ OFF, } D \text{ ON} \\ v_o = 5.7V \end{array} \right.$$

$$\left\{ \begin{array}{l} v_i \geq 10 \\ D \text{ ON, } D_Z \text{ OFF.} \\ v_o = 5.7V \end{array} \right.$$

3.6. point 3

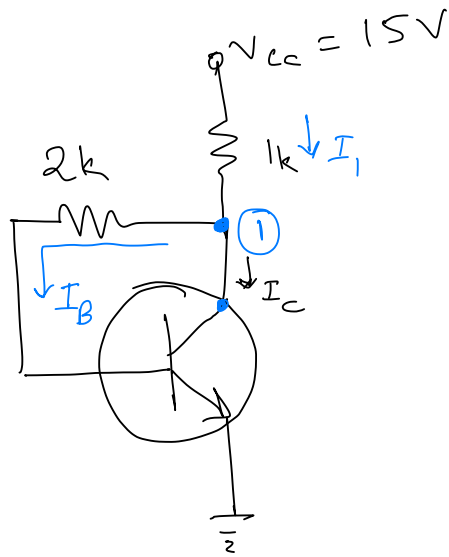

path $V_{CC} \rightarrow 1k \rightarrow 2k \rightarrow B \rightarrow E \rightarrow \text{Ground}$.

$$15 - 1 \frac{I_1}{k} - 2 \frac{I_B}{k} - 0.7 = 0 \quad \text{--- (1)}$$

Assume Active region,

$$I_1 = I_B + I_C$$

$$I_1 = I_B + \beta I_B$$

$$15 - I_B - \beta I_B - 2 I_B - 0.7 = 0$$

$$\Rightarrow 83 I_B = 14.3$$


$$\Rightarrow I_B = 0.1723 \text{ mA}$$

$$I_C = \beta I_B = 13.78 \text{ mA.} \quad \text{Ans}$$

$$\frac{15 - 0.7}{2 + 80 \times 1} \times 80 = \frac{14.3}{82} \times 80$$

$$= 13.95 \text{ Ams}$$

3. C. point 4

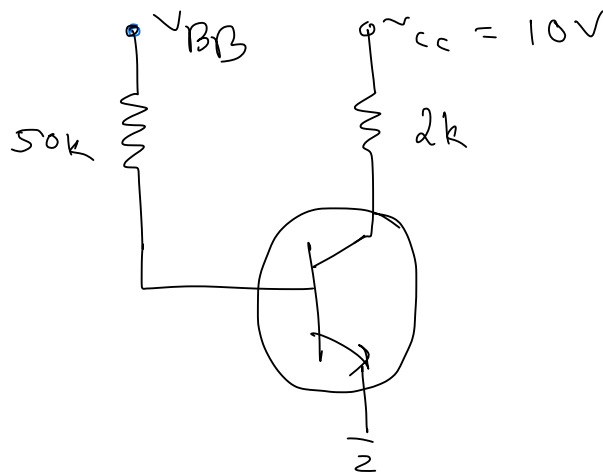

In saturation, $V_{CE} = 0.2V$ or $0V$, (assume)

& $I_C < \beta I_B$, just $I_C \rightarrow \beta I_B$.

$$I_C = \frac{V_{CC} - V_{CE}}{2} = \frac{10 - 0.2}{2} \approx 5 \text{ mA}$$

$$I_B = \frac{5}{\beta} = 0.025 \text{ mA}$$


$$V_{BB} - 50 I_B - 0.7 = 0$$

$$V_{BB} = 0.7 + 50 \times 0.025$$

$$= 1.95 \text{ V}$$

$$\therefore V_{BB} \geq 1.95 \text{ V} \quad \text{Ans.}$$

4.a. point 2

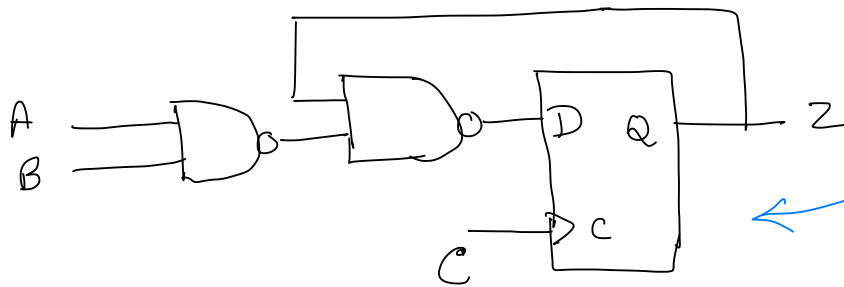


↑ +ve edge triggered
 $\therefore Z = D$ at +ve edge.

$$D = \overline{A \cdot B \cdot Z}$$

$$= \overline{A \cdot B} + \overline{Z}$$

$$= A \cdot B + \overline{Z}$$

A	B	Z	D
0	0	0	1
0	1	0	1
1	0	0	1
1	1	0	1
0	0	1	0
0	1	1	0
1	0	1	0
1	1	1	0

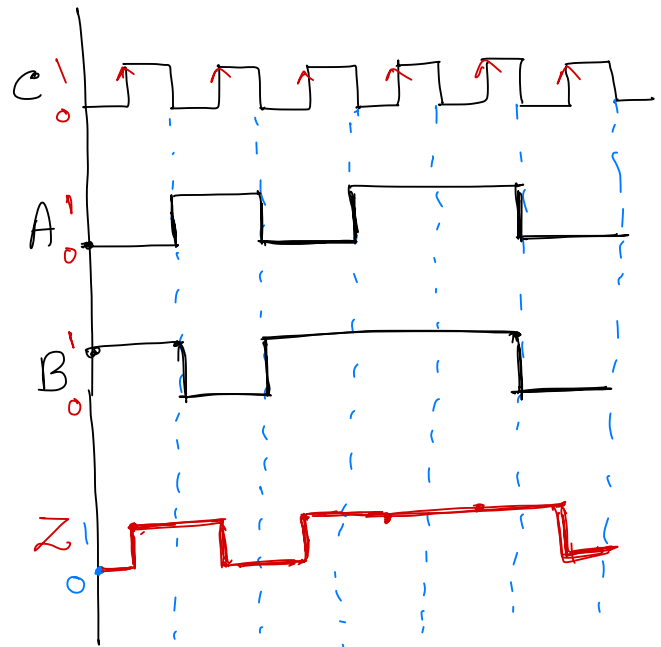

4.b. point 1

$$Y = A + \overline{B}C + A(B + \overline{C})$$


$$= A + AB + \overline{B}C + A\overline{C}$$

$$= A(1+B) + A\overline{C} + \overline{B}C$$

$$= A + A\overline{C} + \overline{B}C$$

$$= A(1+\overline{C}) + \overline{B}C$$

$$Y = A + \overline{B}C$$

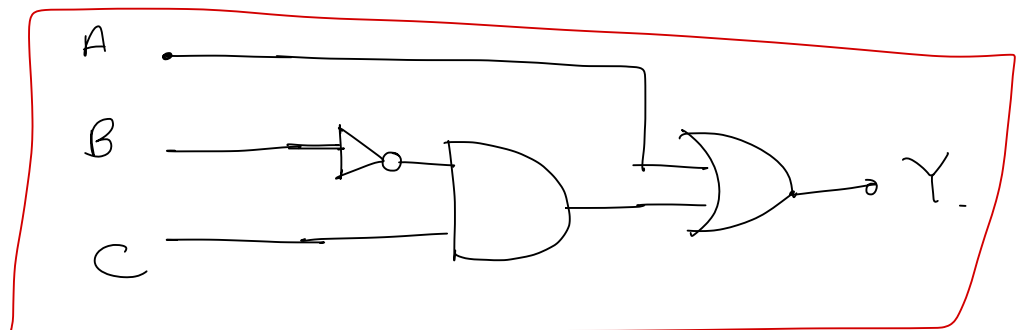

4.C. point 3

AB \ CD	00	01	11	10
00	1	1	1	
01			1	
11				
10			1	


Blue numbers in boxes (minterms):

- Row 00: 10, 11, 13, 12
- Row 01: 14, 15, 17, 16
- Row 11: 12, 13, 15, 14
- Row 10: 18, 19, 11, 10

$$Y = \bar{A}\bar{B}\bar{C} + \bar{A}CD + \bar{B}CD$$

$$Y = (\bar{B} + C)(\bar{A} + C)(\bar{A} + \bar{B})(\bar{C} + D)$$

4.2 point 4

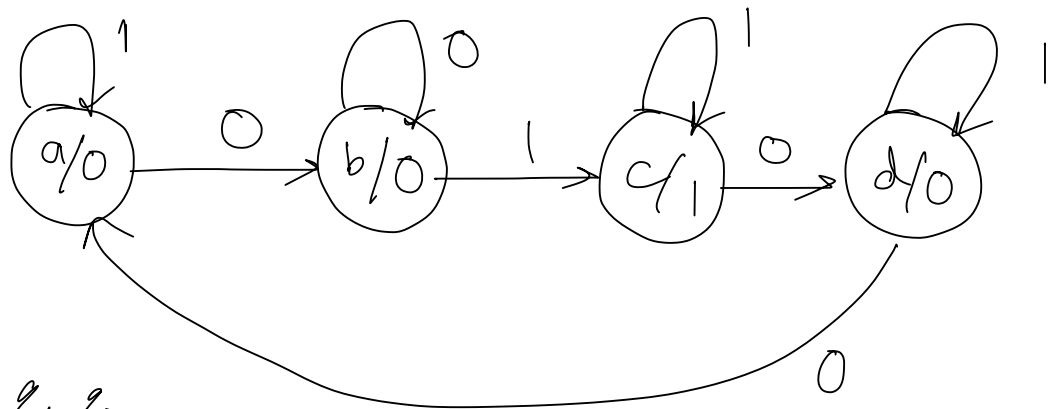

	z_1	z_0
a	0	0
b	0	1
c	1	0
d	1	1

$i/p \Rightarrow x$

$o/p \Rightarrow y$

	z_1	z_0	x	z_1^+	z_0^+	
a	0	0	0	0	1	b
b	0	1	0	0	1	b
c	1	0	0	1	1	d
d	1	1	0	0	0	a
a	0	0	1	0	0	a
b	0	1	1	1	0	c
c	1	0	1	1	0	c
d	1	1	1	1	1	d

	z_1	z_0	y
a	0	0	0
b	0	1	0
c	1	0	1
d	1	1	0

z_1^+

$z_1 z_0$	00	01	11	10
0	0	1	3	2
1	4	5	7	6

Annotations: A red dashed box encloses cells (1,0), (1,1), (1,2), and (1,3). A blue dashed box encloses cells (0,1), (0,2), (1,1), and (1,2). A blue arrow points from cell (0,3) to cell (1,2).

$$z_1^+ = x z_0 + z_1 \bar{z}_0$$

z_0^+


$z_1 z_0$	00	01	11	10
0	1	1		1
1			1	

Annotations: Red circles highlight the 1s in cells (0,0), (0,1), (0,3), and (1,2). A red line connects the 1s in (0,0) and (0,1). A red line connects the 1s in (0,3) and (1,2).

$$z_0^+ = \bar{x} \bar{z}_1 + \bar{x} \bar{z}_0 + x z_1 z_0$$

$$y = z_1 \cdot \bar{z}_0$$

5. a. points 3

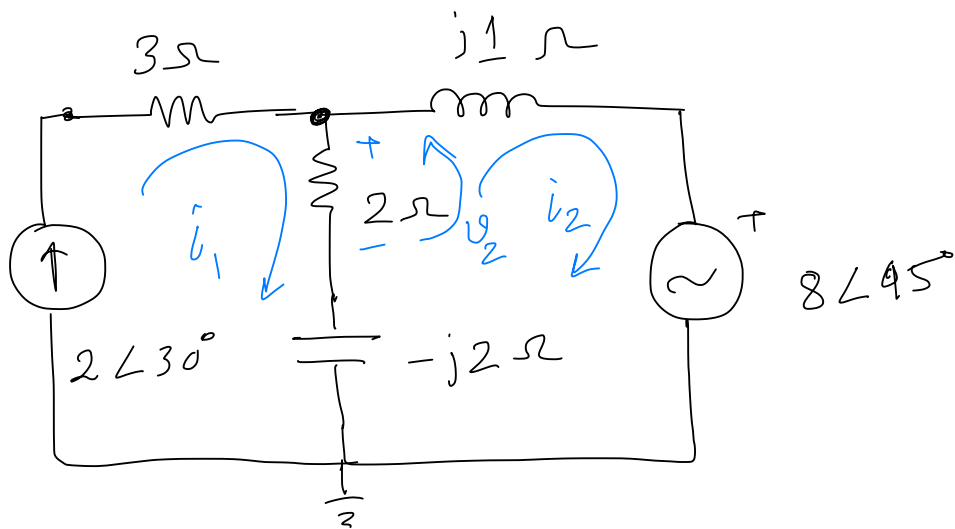

Loop 2

$$j1 \cdot I_2 + (2 - j2)(I_2 - I_1) + 8\angle 45^\circ = 0$$

$$\& \quad I_1 = 2\angle 30^\circ$$


$$\therefore jI_2 + (2 - 2j)I_2 - 2\angle 30^\circ(2 - 2j) = -8\angle 45^\circ$$

$$\therefore I_2 = 3.18\angle -65^\circ \text{ A.}$$

$$\therefore V_2 = 2(I_1 - I_2) = 2(2\angle 30^\circ - 3.18\angle -65^\circ)$$

$$V_2 = 7.8\angle 84.41^\circ \text{ Ans.}$$


5.b point : 2

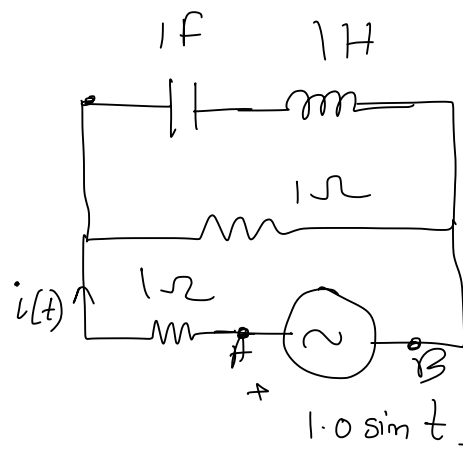

$$\omega = 1 \text{ rad/sec.}$$

$$\frac{1}{j\omega C} = -j1$$

$$j\omega L = j1$$

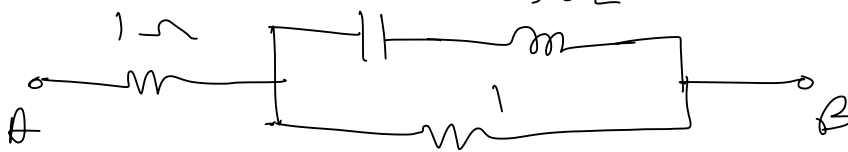


$$Z_{AB} = 1 + 1 \parallel (-j + j)$$

$$= 1 \Omega$$

$$\therefore \text{peak of } i(t) \Rightarrow \frac{1}{1} = 1 \text{ A. Ans.}$$

5.C. point 5

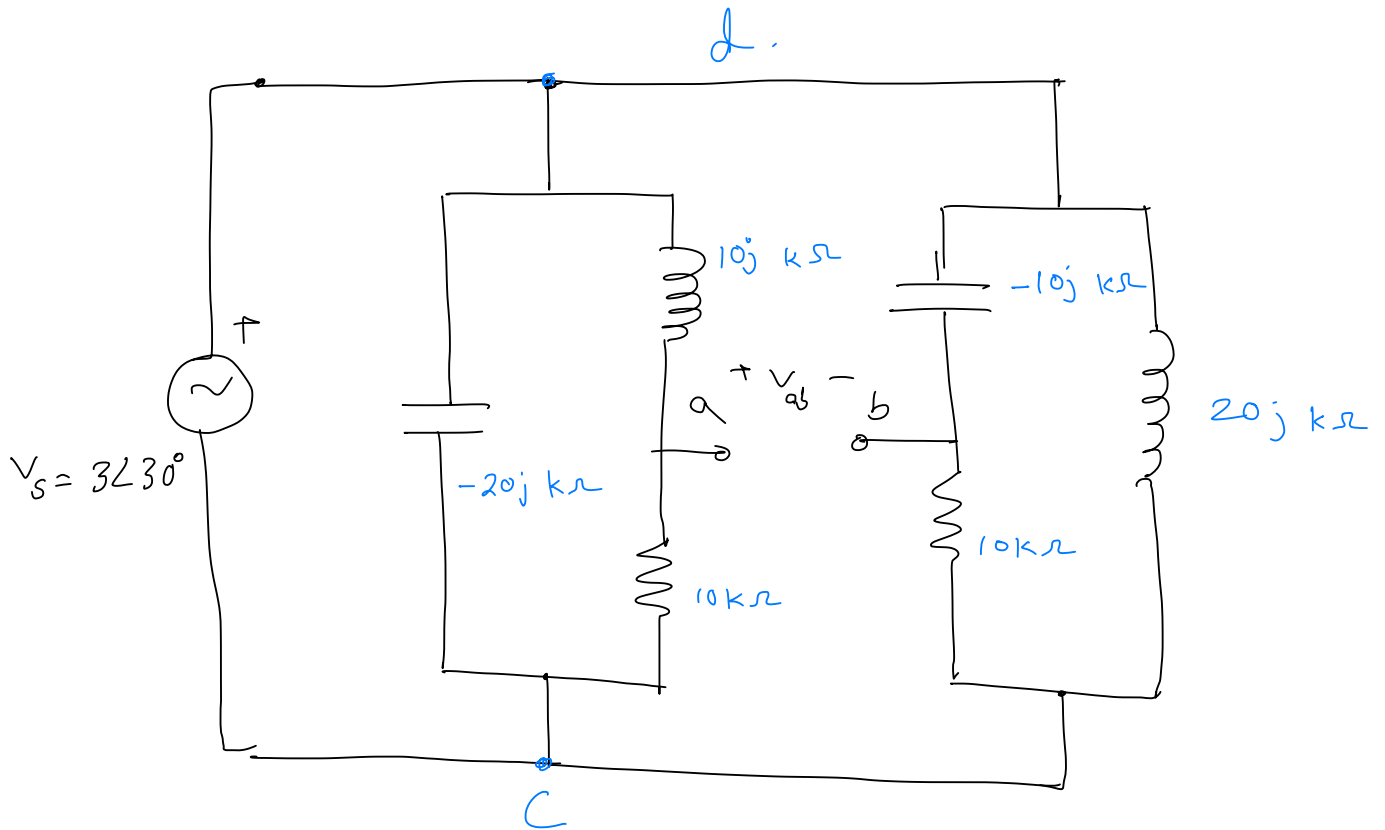

$$V_{dc} = V_s = 3\angle 30^\circ$$

Applying voltage divider rule,

$$V_{ac} = V_s \cdot \frac{10}{10 + 10j}$$

$$V_{bc} = V_s \cdot \frac{10}{10 - 10j}$$

$$V_{ab} = V_{ac} - V_{bc}$$

$$= 10V_s \left(\frac{1}{10 + 10j} - \frac{1}{10 - 10j} \right)$$

$$= 10V_s \frac{10 - 10j - 10 - 10j}{(10 + 10j)(10 - 10j)}$$

$$= 10V_s \cdot \frac{-20j}{10^2 + 10^2}$$

$$= \frac{200}{200} (3 \angle 30^\circ) (1 \angle -90^\circ)$$

$$V_{ab} = 3 \angle -60^\circ \cdot \text{volt.} \quad \text{Ans.}$$