

EXAM

1TE717 Digital Technologies and Electronics

Faculty of Electrical Engineering

2020–10–22, 14:00–19:00

Take-home Exam - Studium

- Aids:**
- Mathematics and / or Physics handbook,
 - a small graphical calculator (e.g. TI-83 and similar),
 - one A4 paper (two sides) with handwritten formulas or notes.

Note that exercise materials (exercise tasks, old exams, and solutions) are **NOT** allowed.

- Observe:**
- Do not treat more than one problem on each page.
Each step in your solutions must be motivated.
Lacking motivation will result in point deductions.
Write a clear answer to each question and clearly indicate which formulas are used.
Mark the total number of pages on the cover or first page

The exam consists of Part A and Part B, for a total of 50 points. The points for each problem are also indicated.

- Passing Grade:** To pass the course, you need to successfully attain the learning goals of the course. This means that you would pass the exam if you obtain **at least 50%** of the points at **each question of part A**.

Part A has a total of 5 questions.

- Exam Grade:** Passing the exam would grant the grade 3. Grades 4 and 5 are obtained based on the **total score** obtained in the exam (Parts A and B).

- Responsible:** André Teixeira (see Studium for contact information)

Good Luck!

Part A

A.1

Consider the network in Fig. 1, where $R_1 = R_2 = R_3 = 40\ \Omega$, $R_4 = R_5 = 20\ \Omega$, $V_1 = 6\text{ V}$ and $V_2 = 3\text{ V}$. Determine the current passing through R_3 (magnitude and direction).

 


Figure 1: Circuit for Question A.1.

(Sub-Total A.1: 5 pt)

A.2

Consider the amplifier circuit in Fig. 2, where $R_1 = 200\ \Omega$, $R_2 = 400\ \Omega$, $R_3 = 100\ \Omega$, $V_r = 1\text{ V}$, and $V_{in} = 5\text{ V}$.

Assume that the OpAmp is ideal and that the supply voltages are sufficiently large. **Using Ohm's and Kirchoff's laws** (possibly through the Nodal or Mesh method), **derive the expression** for the output voltage V_o as a function of V_{in} and V_r and determine the current passing through R_3 (magnitude and direction).

Note: merely identifying and writing down the correct formula, without including the supporting derivations based on circuit analysis, will give no points.

(Sub-Total A.2: 5 pt)

 


Figure 2: Circuit for Question A.2.

A.3

Consider the circuit in Fig. 3, where the bipolar transistor has the following characteristics: $\beta = h_{FE} = 300$, $V_{CEsat} = 0.2\text{ V}$, and $V_{BE} = 0.6\text{ V}$. Suppose that $V_s = 12\text{ V}$, and $V_{in} = 5\text{ V}$. The diode shown in the circuit is an LED with $V_D = 1.5\text{ V}$ and internal resistance $R_D = 20\Omega$.

Design R and R_B so that the BJT works as a switch, no more than 20 mA pass through the LED, and the current provided by the voltage source V_{in} is smaller than 1 mA .

(Sub-Total A.3: 5pt)

 


Figure 3: Circuit for Question A.3.

A.4

This question is about designing a sequential machine that detects a given sequence within a stream of bits x_i . The circuit normally gives $y = 0$ as the output, until the sequence 0110 is detected. Every time that the sequence is detected, the output y should be set to 1 for one clock cycle, and then return to zero when a new input bit x_i is read and continue to detect possible sequences (i.e., **possibly with overlapping** a previous sequence).

- A.4.a) Perform the first steps of the design of the sequential network: i) derive the state-diagram, ii) choose the state-coding, and iii) write the truth tables determining the behavior of the sequential network and its outputs.

Given your design choice, indicate whether it is a Mealy or Moore type, and how many D flip-flops would be needed to implement your circuit. Motivate your answer!

*Note: you need **not** derive the minimal SP-form Boolean expressions, nor to draw the final circuit diagrams with gates and flip-flops.*

- A.4.b) Suppose that one of the D flip-flops has the following Boolean function for determining its next state:

$$q_0^+ = f(q_2, q_1, q_0, x_i) = \Sigma(2, 3, 4, 10, 12) + d(0, 6, 11).$$

Design a combinatorial network that implements the logical function f in minimal SP-form using only NAND gates. Draw the logical circuit with the corresponding D flip-flop.

(Sub-Total A.4: 5pt)

A.5

Consider the filter in Fig. 4. Suppose that $V_{in}(t)$ is a sinusoidal voltage signal with $v_{in}(t) = 2 \sin(100000\pi t - \frac{\pi}{3})$. Using the methods of AC circuit analysis and complex impedances, derive the expression of the output voltage signal $v_{out}(t)$ for $R_1 = R_2 = 50 \Omega$, $C = 0.1 \mu F$, and $L = 1 mH$, and classify this circuit as either a low-pass, high-pass, band-pass, or a band-stop filter.

(Sub-Total A.5: 5pt)

 


Figure 4: Circuit for Question A.5.

Part B

B.1

Consider the amplifier circuit in Fig. 5, where D_1 has $V_d = 0.5\text{ V}$, and $V_{out}(t)$ is the voltage measured across the terminals of the capacitor. Let $V_{in}(t)$ be a sinusoidal voltage with amplitude $V_p = 6\text{ V}$. Describe the behavior of the circuit, motivated by the operation of its components, and sketch the shape of the output voltage. Supposing that the OpAmp is supplied with $+15\text{ V}$ and -15 V , what is the maximum reverse voltage that the diode must be able to withstand?

(Sub-Total B.1: 8pt)

 


Figure 5: Circuit for Question B.1.b).

B.2

Consider the AC amplifier circuit in Fig. 6, where $R_1 = R_2 = 10\text{ k}\Omega$, $C_1 = 2C_2$, and $C_2 = 10\text{ nF}$. Assume that the OpAmp is ideal and that the supply voltages are sufficiently large. **Using AC circuit analysis, derive the transfer function** of the circuit. Based on the transfer function, determine the gain at $\omega = 14000\text{ rad/s}$, and state whether the circuit is a low-pass, high-pass, band-pass, or band-stop filter.

Note: merely identifying and writing down the correct formula, without including the supporting derivations based on circuit analysis, will give no points.

 


Figure 6: Circuit for Question A.3.b).

(Sub-Total B.2: 9pt)

B.3

In this question, you are asked to design a generator of a given sequence of two bits, (x_1, x_2) . The desired sequence is composed of binary numbers, in the following order: $(0, 0)$, $(1, 1)$,

$(0, 1), (1, 0), (0, 0), (1, 1), \dots$ (the sequence repeats itself) ...

The circuit shall be designed based on 1 D flip-flop and a 4-bit counter. The counter has the output (z_3, z_2, z_1, z_0) corresponding to the current number in the counter. It also has an enable bit E and an asynchronous reset bit R . When $E = 1$, the counter continues to count in the positive direction. When $E = 0$, the counter freezes its operation. When R is set to 1, the counter immediately sets its current number to 0 and resumes counting from that number when $E = 1$.

The 4-bit output of the counter is translated onto the respective elements of the sequence.

The purpose of the D flip-flop is to control the operation of the counter.

Design the behavior of the D flip-flop, by drawing the state diagram of a sequential network that controls the counter as desired. Given your design choice, indicate whether it is a Mealy or Moore type.

Briefly describe how the 4-bit output of the counter could be translated onto the elements of the sequence. Motivate your answer (e.g., by using a truth table)!

(**Note:** *Karnaugh diagrams are not needed for this answer.*)

(Sub-Total B.3: 8pt)